
 


TASK 1 C

 


TASK 1 D



$$\begin{aligned} (2 \cdot U_{\max})^2 &= (2 \cdot 3 \cdot r_a)^2 \cdot 2 \\ 4 \cdot U_{\max}^2 &= (6 \cdot r_a)^2 \cdot 2 \quad | :2 \\ 2 \cdot U_{\max}^2 &= 6^2 \cdot r_a^2 \\ 2 \cdot 72V^2 &= 36 \cdot r_a^2 \quad | :36 \\ 2 \cdot 2V^2 &= r_a^2 \quad | \sqrt{} \\ \underline{2V} &= r_a \end{aligned}$$


We want U_{\max} as the distance to the outermost points (0011, 0000, 1100, 1111) because this allows us to send data with the highest possible voltage, resulting in a better SNR.

TASK 2 A

 


$$U_X(0) = \frac{Z_0}{R_I + Z_0} \cdot U_S(0) = \frac{75\Omega}{75\Omega + 50\Omega} \cdot 5V = \underline{\underline{3V}}$$

TASK 2 B

 


$$U_X(\infty) = \frac{R_T}{R_I + R_T} \cdot U_S(\infty) = \frac{175\Omega}{50\Omega + 175\Omega} \cdot 5V = \underline{\underline{3.9V}}$$

TASK 2 C

 

 The value of $U_X(t)$ and $U_Y(t)$ stays constant between changes, because the reflection over the line takes t_d amount of time. See diagram of lecture:



$$V_e = \frac{R_T - Z_0}{R_T + Z_0} = \frac{175\Omega - 75\Omega}{175\Omega + 75\Omega} = 0.4$$

$$V_b = \frac{R_I - Z_0}{R_I + Z_0} = \frac{50\Omega - 75\Omega}{50\Omega + 75\Omega} = -0.2$$

$$U_X(t) = U_Y(t-1) + V_b \cdot [U_Y(t-1) - U_X(t-2)]$$

$$U_Y(t) = U_X(t-1) + V_e \cdot [U_X(t-1) - U_Y(t-2)]$$

$$U_X(0) = 3V \quad (\text{see Task 3 A})$$

$$U_Y(1 \cdot t_d) = 3V + 0.4 [3V - 0V] = 4.2V$$

$$U_X(2 \cdot t_d) = 4.2V + (-0.2) [4.2V - 3V] = 3.96V$$

$$U_Y(3 \cdot t_d) = 3.96V + 0.4 [3.96V - 4.2V] = 3.896V$$

$$U_X(4 \cdot t_d) = 3.8932V$$

$$U_Y(5 \cdot t_d) = 3.89088V$$

TASK 3 A

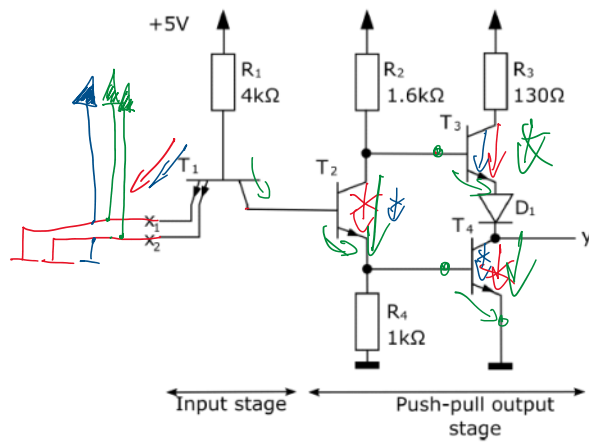


Figure 3.1: standard TTL output driver

x_1	x_2	T_1	T_2	T_3	T_4	y
Low	Low	con.	non-con.	con.	non-con.	H
Low	High	con.	non-con.	con.	non-con.	H
High	Low	con.	non-con.	con.	non-con.	H
High	High	non-con.	con.	non-con.	con.	L

Table 3.1: Logic Level

con. $\hat{=}$ conducting
non-con. $\hat{=}$ non-conducting

TASK 3 B

Advantages are e.g. 1. High currents are possible; 2. Little energy is consumed while static

These advantages hold true in comparison to other types e.g. RTL logic. CMOS for example consumes lower power.