

Example: VHDL model of a state machine

This example will show how a clock-flank-triggered automat with an asynchronous reset can be modelled. Figure 1 shows the interface of an abstract Moore-Automat with two input signals, three output signals, clock and an asynchronous reset signal.

 


Fig. 1: Interface signals of a Moore-Example-Automat

The automat graph for this example is shown below in figure 2. It is a synchronous, front-flank-triggered Moore-Automat with four states. The single input combinations `in_1` and `in_2` are marked on the arrows. The output variables `out_1`, `out_2` and `out_3` are defined within the states. An asynchronous, low-active reset signal (`reset = '0'`) initiates an instantaneous change to the state `init`. This is also the starting state.

 


Fig..2: Automat graph of the example automat

To model such a behavior in VHDL, you have to consider the following:

- ❑ An own counter-type can be declared for an internal "state-signal" for the four possible states, that receives the single states as possible signal values.
- ❑ The flank-triggering of the state changes is done within a process, activated through `clk` and `reset`. The query of the active signal flank is done using the signal attributes. It is important that the reset signal has priority!
- ❑ Because the automat is a Moore-Type automat, the output variables are assigned according to the state. This can be done in the same process or separately as a process or quasi-parallel signal allocation.

This is the described automat behavior realized in VHDL code:

```

-----
-- filename:          fsm.vhd
-- title:             Behavioural Model of a simple state machine
-- author:            B. Wunder, ITIV
-----

ENTITY fsm IS
    PORT (clk, reset : IN bit ;
          in_1, in_2 : IN bit ;
          out_1, out_2, out_3 : OUT bit) ;
    TYPE fsm_state IS (init, state_1, state_2, state_3) ;
END fsm ;

-----

ARCHITECTURE behavioural OF fsm IS
    SIGNAL state : fsm_state := init ;

BEGIN
    new_state : PROCESS (clk, reset)
    BEGIN
        IF (reset = '0') THEN
            state <= init ;
        ELSIF (clk = '1' AND clk'EVENT) THEN
            CASE state IS
                WHEN init =>
                    IF in_1 = '0' AND in_2 = '1' THEN
                        state <= state_1 ;
                    ELSIF in_1 = '1' AND in_2 = '1' THEN
                        state <= state_2 ;
                    END IF ;
                WHEN state_1 =>
                    IF in_1 = '1' THEN
                        state <= init ;
                    ELSIF in_1 = '0' AND in_2 = '1' THEN
                        state <= state_2 ;
                    END IF ;
                WHEN state_2 =>
                    IF in_1 = '1' AND in_2 = '1' THEN
                        state <= init ;
                    ELSIF (in_1 = '0' AND in_2 = '1')
                    OR (in_1 = '1' AND in_2 = '0') THEN
                        state <= state_3 ;
                    END IF ;
                WHEN state_3 =>
                    IF in_1 = '1' AND in_2 = '1' THEN
                        state <= init ;
                    END IF ;
            END CASE ;
        END IF ;
    END PROCESS ;

    output_assignment : PROCESS (state)
    BEGIN
        CASE state IS
            WHEN init =>
                out_1 <= '0' ;
                out_2 <= '0' ;
                out_3 <= '0' ;
            WHEN state_1 =>
                out_1 <= '0' ;

```

```
        out_2 <= '0' ;
        out_3 <= '1' ;
    WHEN state_2 =>
        out_1 <= '0' ;
        out_2 <= '1' ;
        out_3 <= '1' ;
    WHEN state_3 =>
        out_1 <= '1' ;
        out_2 <= '0' ;
        out_3 <= '0' ;
    END CASE ;
END PROCESS ;
END behavioural ;
```