

Design and Modelling of Superconducting FCL

Wescley T. B. de Sousa, Mathias Noe



INSTITUTE FOR TECHNICAL PHYSICS (ITEP)



- The integration of a superconducting fault current limiter (FCL) in power systems appears as a powerful solution against increasing short-circuit currents levels that endanger the safety of electrical equipment
- Simulation methods are part of the development of all new electrical equipment
- Standard network analysis software does not include suitable models for FCLs
 - DigiSILENT PowerFactory, MATLAB Simulink, EMTP-ATP, PSCAD, ANAREDE, etc...



Basic concept of superconducting fault current limiter

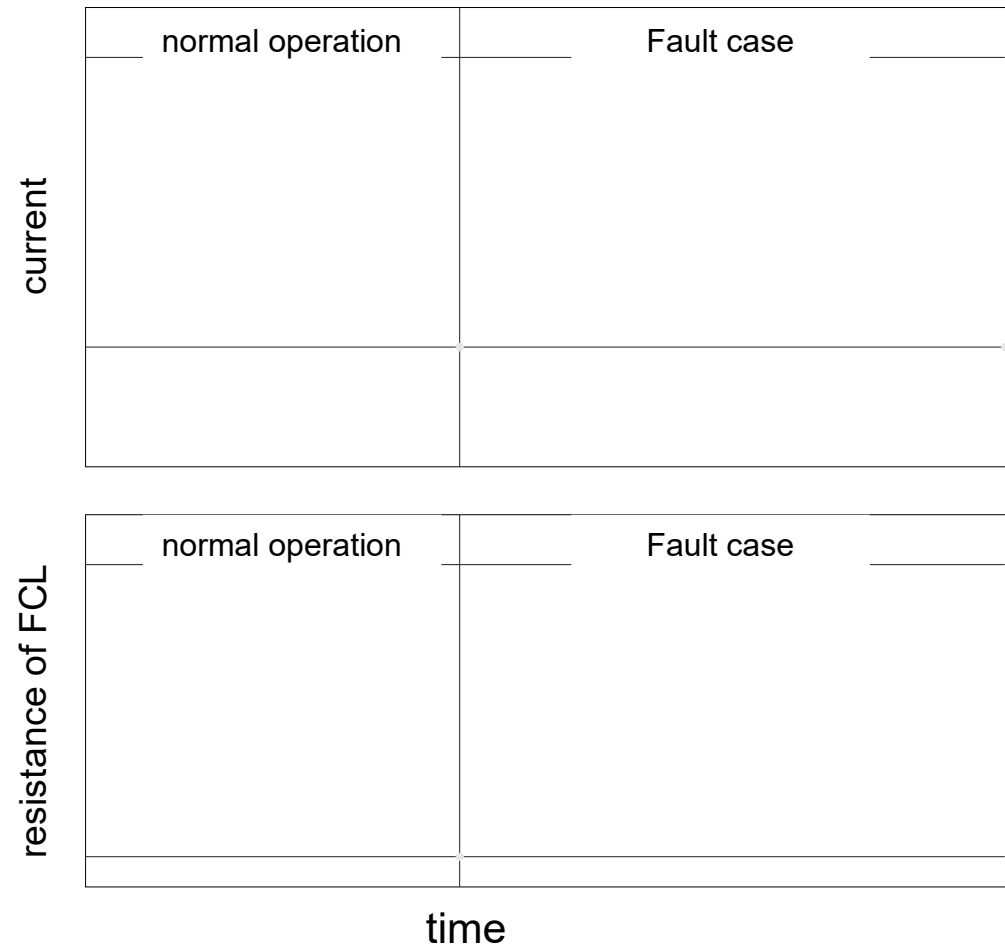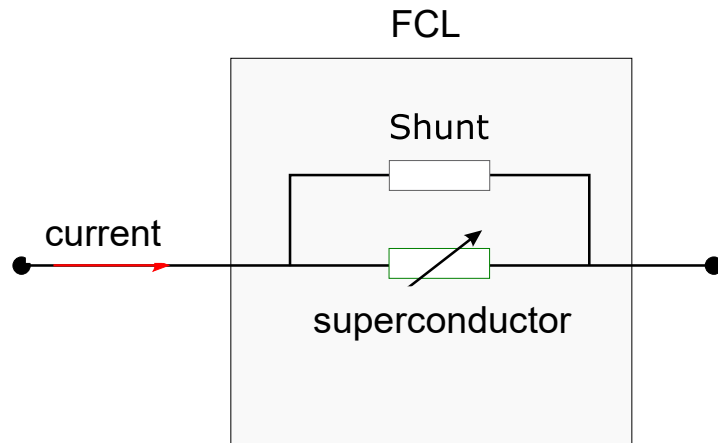- Superconducting fault current limiter are a safety measure that can quickly and efficiently reduce the fault current in an electrical power supply





Basic concept of superconducting fault current limiter

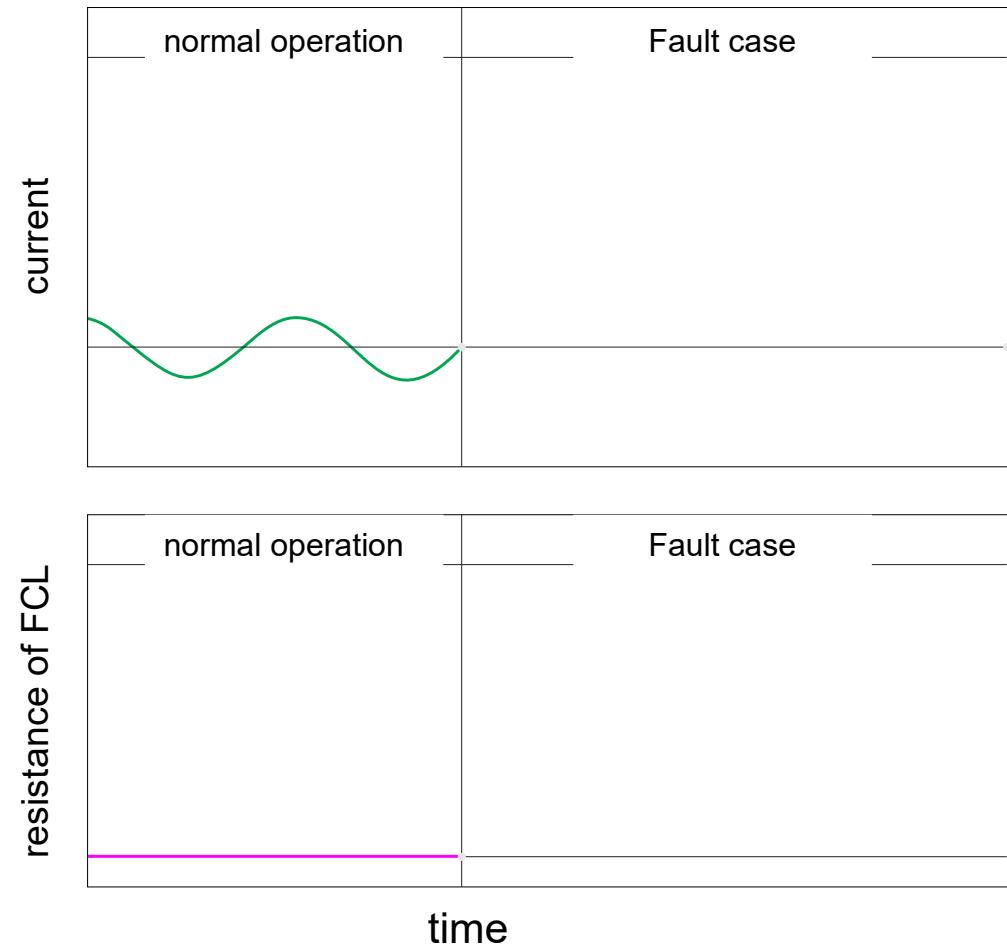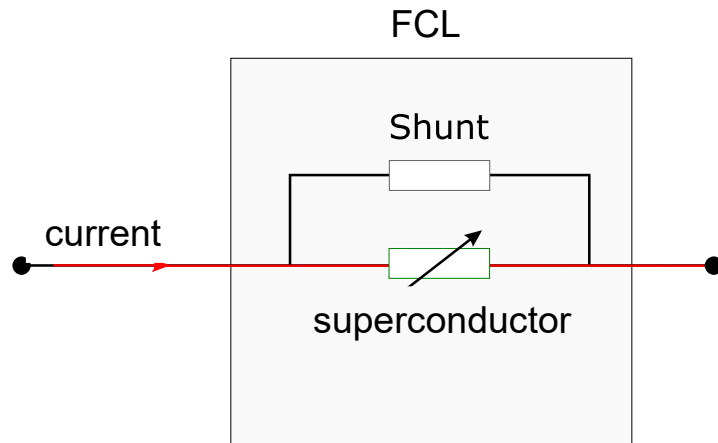- Superconducting fault current limiter are a safety measure that can quickly and efficiently reduce the fault current in an electrical power supply





Basic concept of superconducting fault current limiter

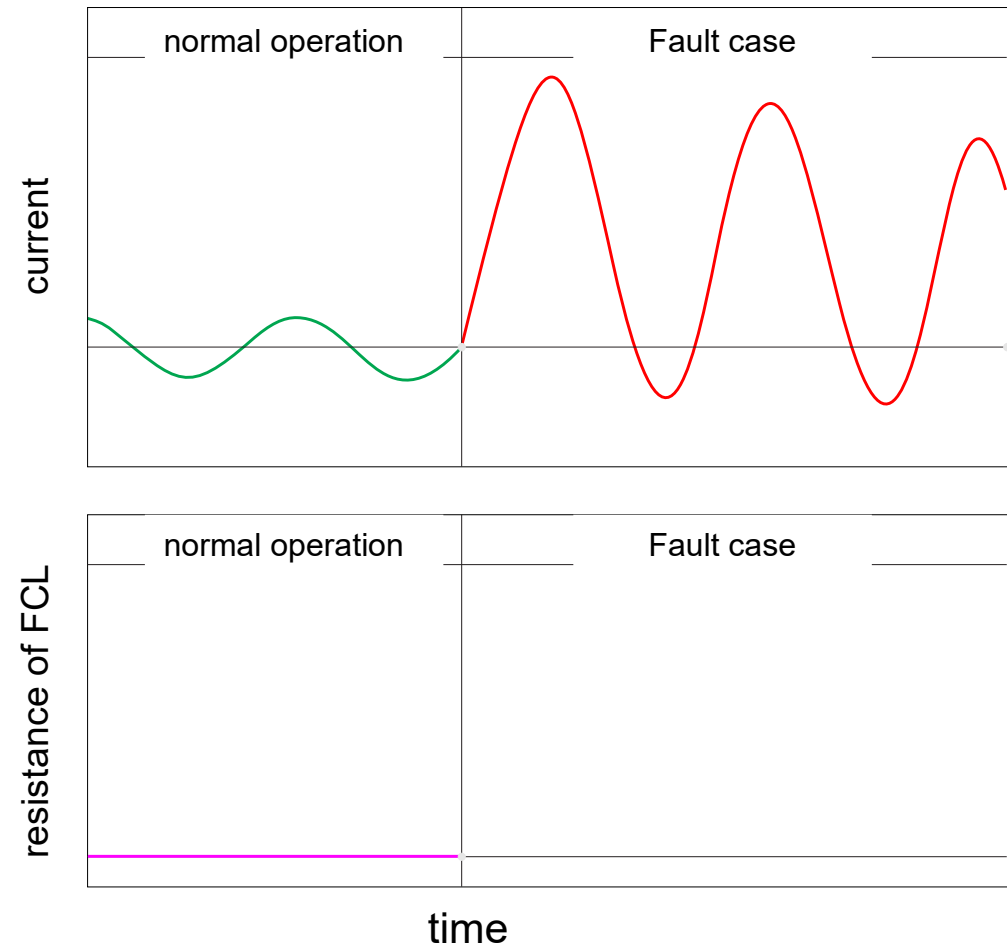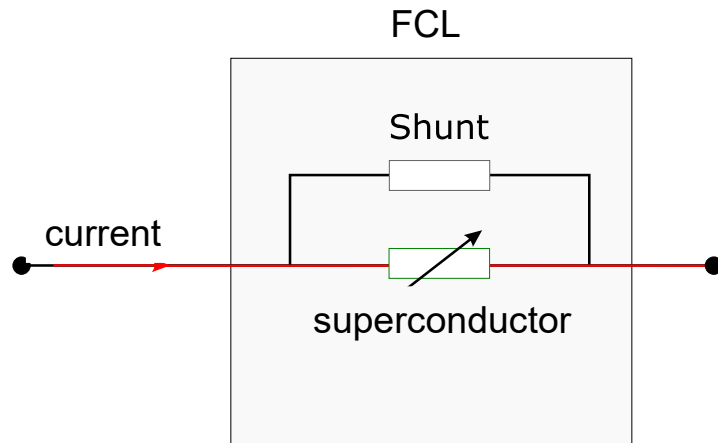- Superconducting fault current limiter are a safety measure that can quickly and efficiently reduce the fault current in an electrical power supply





Basic concept of superconducting fault current limiter

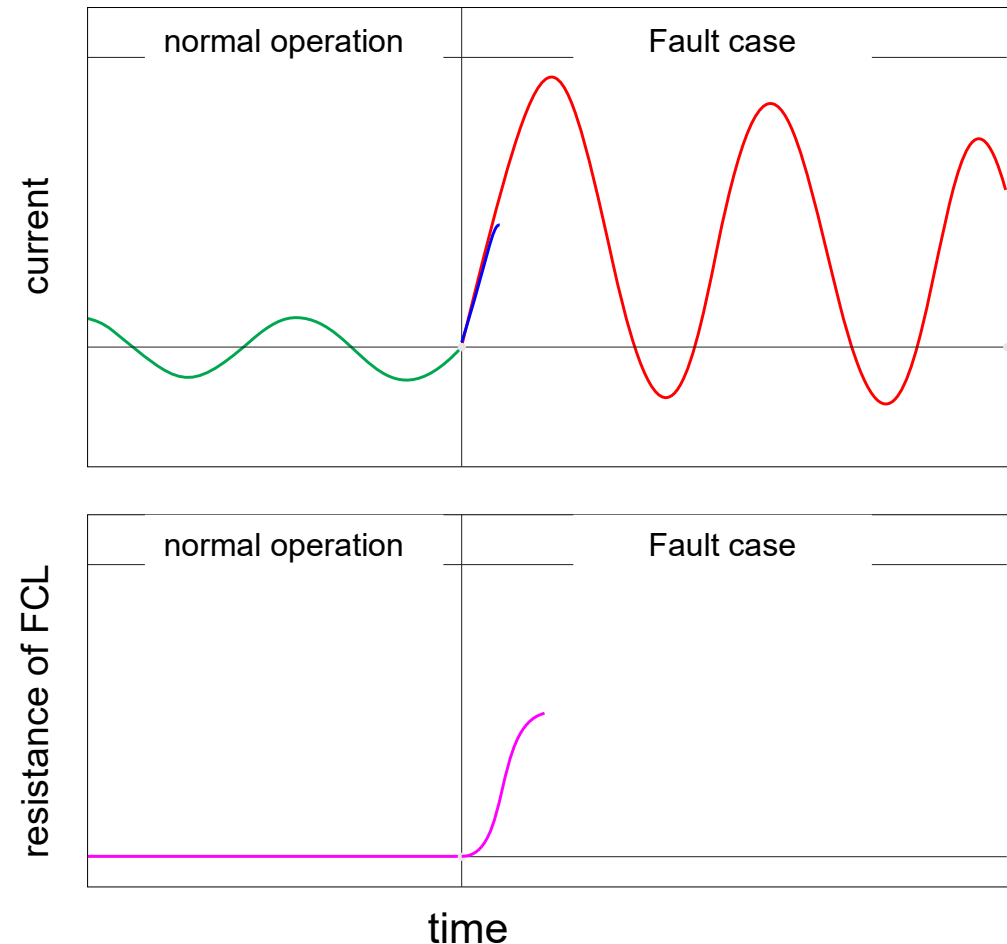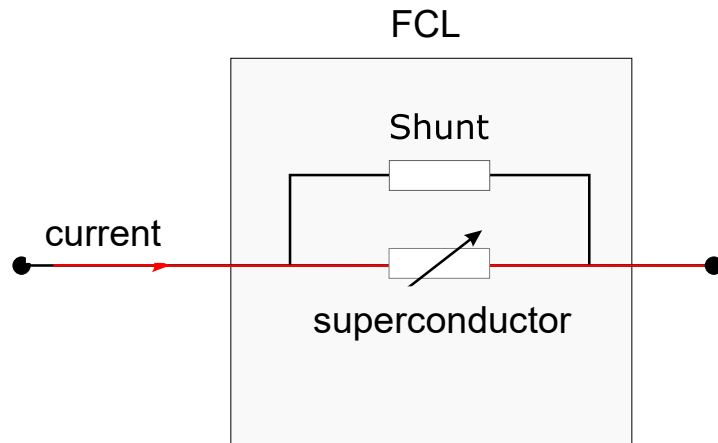- Superconducting fault current limiter are a safety measure that can quickly and efficiently reduce the fault current in an electrical power supply



Basic concept of superconducting fault current limiter

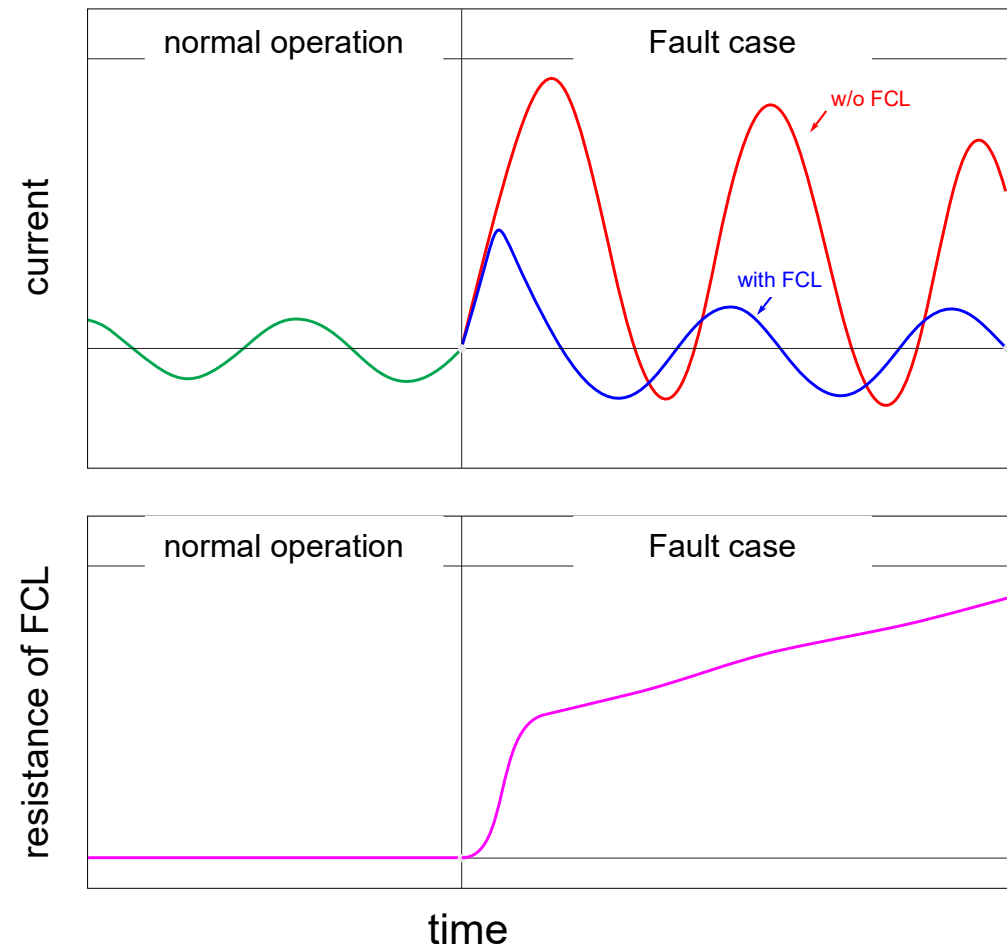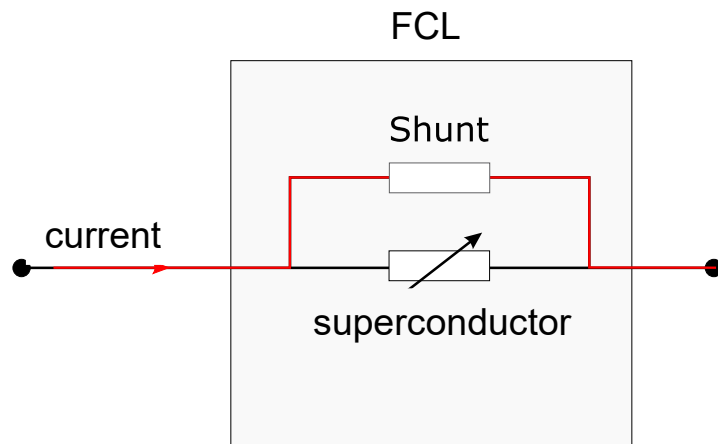- Superconducting fault current limiter are a safety measure that can quickly and efficiently reduce the fault current in an electrical power supply




Basic Designing Concepts

- Voltage Drop along the SFCL during fault period:

$$U_{SFCL} = \frac{U_N}{\sqrt{3}} - I_F \cdot Z_{Grid}$$

- Total length of one single HTS tape:
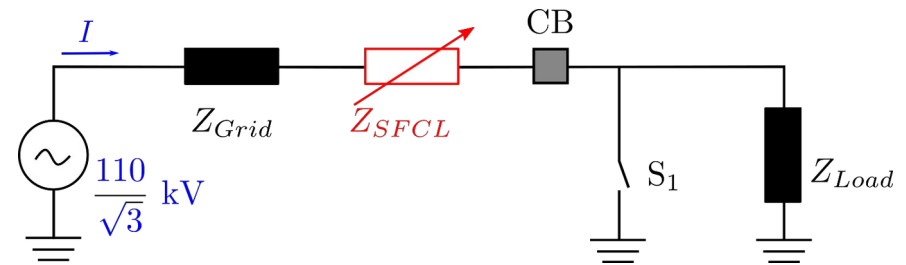
$$\ell_{tape} = \frac{U_{SFCL}}{E_{hts}}$$



- Total length of tapes in the SFCL (per phase):

$$\ell_{Tot} = \ell_{tape} \cdot n_p$$

$$E_{hts} = 0.2 \dots 0.5 \text{ V/cm}$$


$$k = 0.9 \dots 1.0$$

$$n_p = \frac{\sqrt{2} \cdot I_N}{k \cdot I_c}$$

- $T_{MAX} = 360 \text{ K}$

Determination of the network parameters

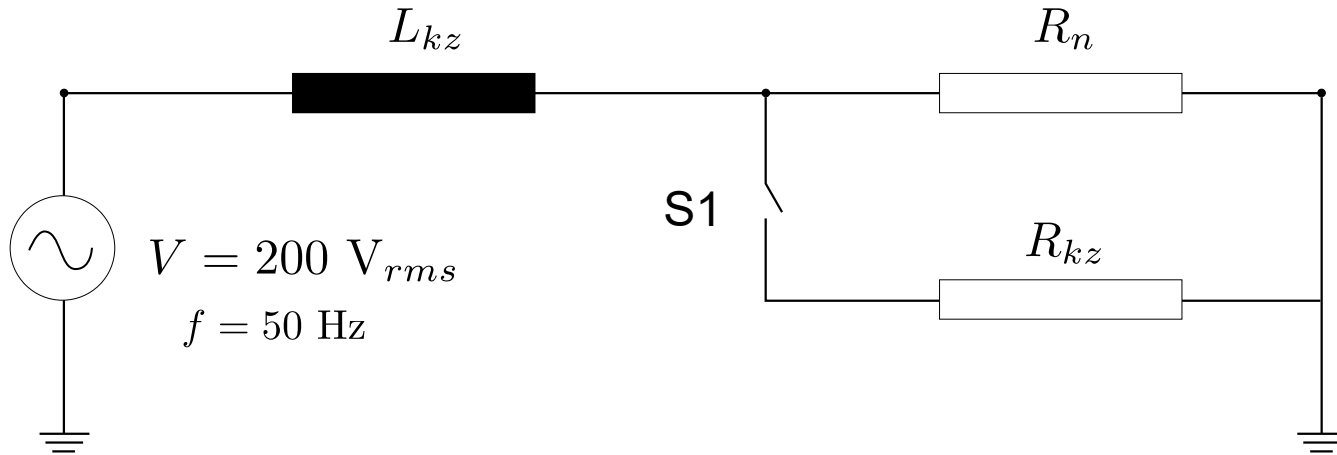- The first step is to set the network parameters. For example, take the following electrical circuit



- Without current limiter

$$L_{kz} \frac{di}{dt} = V - R_{kz} i$$

State Equation

$$R_n = 2.0 \, \Omega$$

$$I_n = 100 \text{ A}_{rms}$$


$$L_{kz} = 0.02 \text{ mH}$$

$$R_{kz} = 0.6 \text{ m}\Omega$$

$$R_n = 2.0 \, \Omega$$

$$I_{kz} = 40 \text{ kA}_{rms}$$

Runge-Kutta method

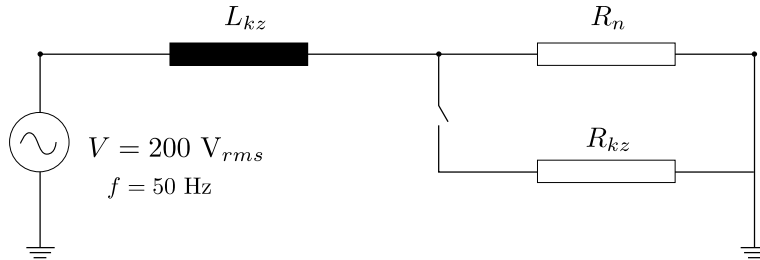

$$L_{kz} \frac{di}{dt} = V - R_{kz} i$$

- The Runge-Kutta method is an explicit iterative method to solve initial value problems (ordinary differential equation) numerically.


$$k_1 = \frac{1}{L_{kz}} A \sin(\omega t) - R_{kz} i_o$$

$$k_2 = \frac{1}{L_{kz}} A \sin \left[\omega \left(t + \frac{h}{2} \right) \right] - R_{kz} \left[i_o + k_1 \frac{h}{2} \right]$$

$$k_3 = \frac{1}{L_{kz}} A \sin \left[\omega \left(t + \frac{h}{2} \right) \right] - R_{kz} \left[i_o + k_2 \frac{h}{2} \right]$$

$$k_4 = \frac{1}{L_{kz}} A \sin [\omega (t + h)] - R_{kz} [i_o + k_3 h]$$

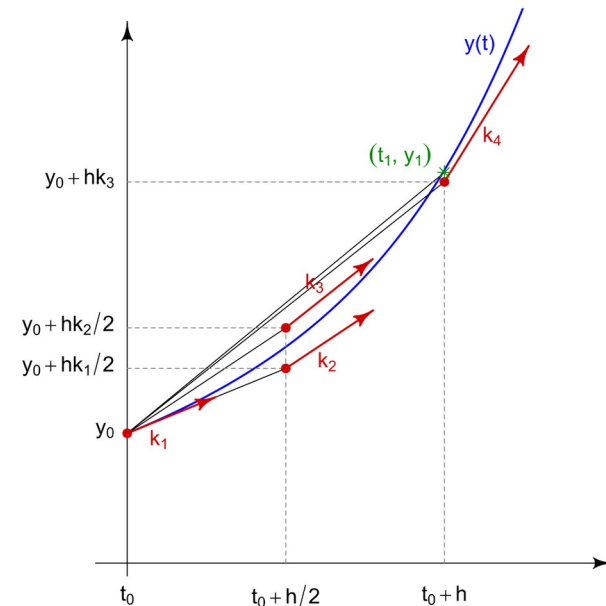
$$i_{u+1} = i_u + \frac{h}{6} (k_1 + 2k_2 + 2k_3 + k_4)$$







Picture: Wikipedia

Simulation sequence – short-circuit current

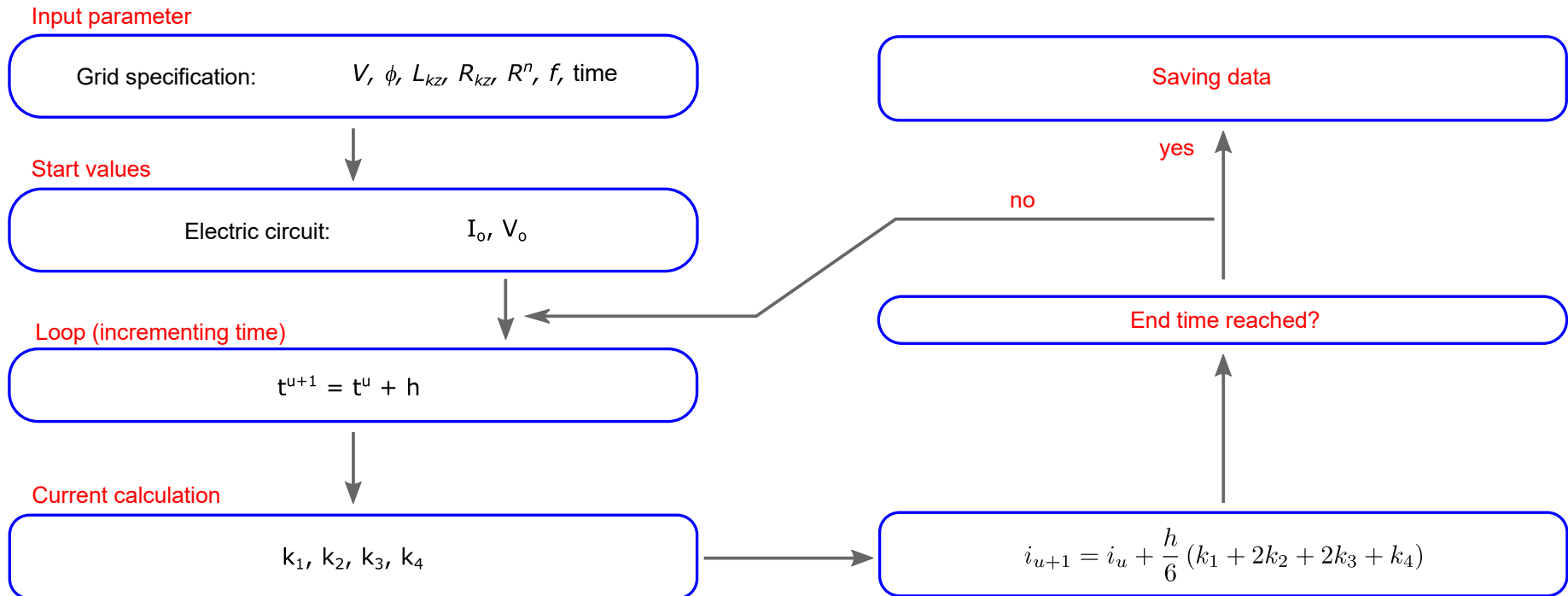■ Flowchart for the simulation of the transient behaviour of short-circuit current




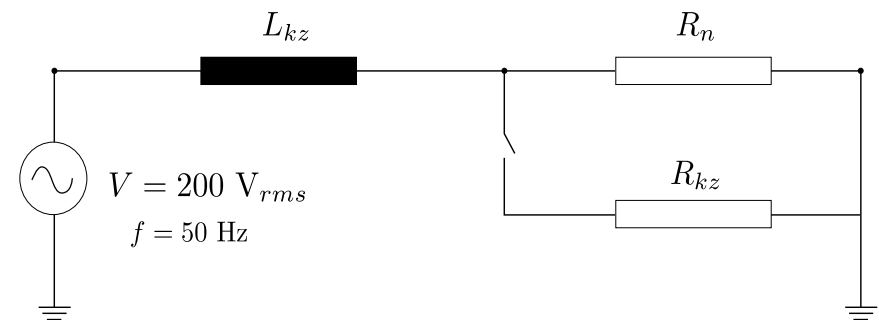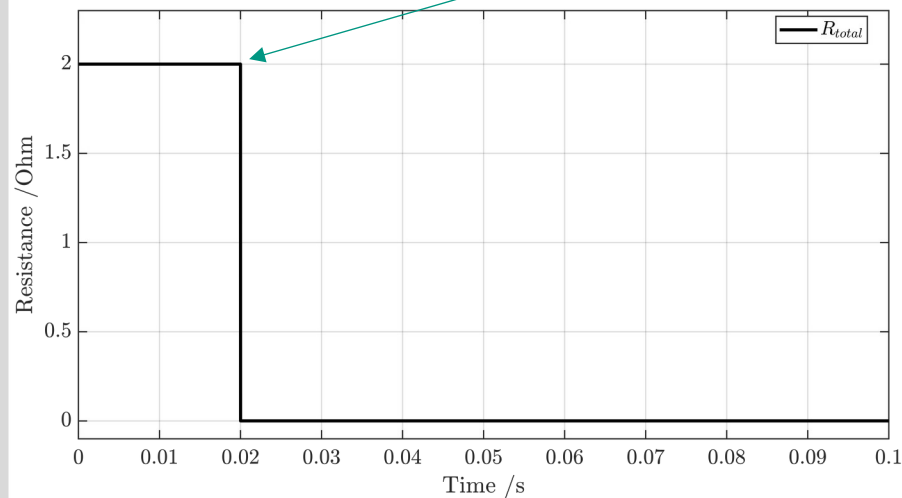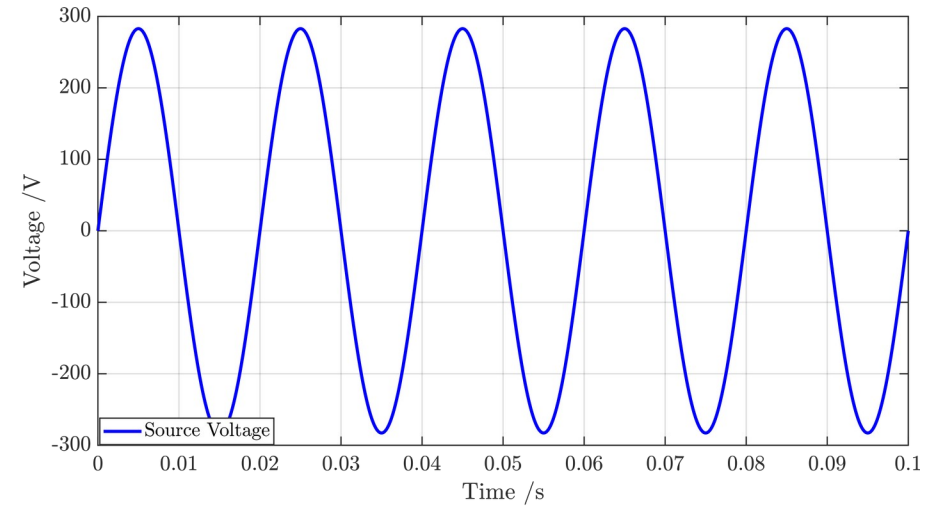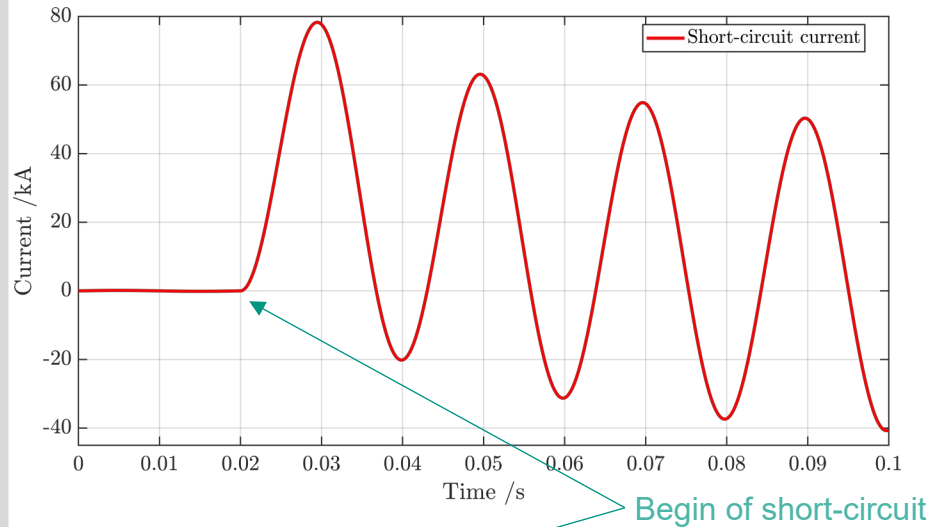Results – Short-circuit current – Example 01



Determination of network parameter

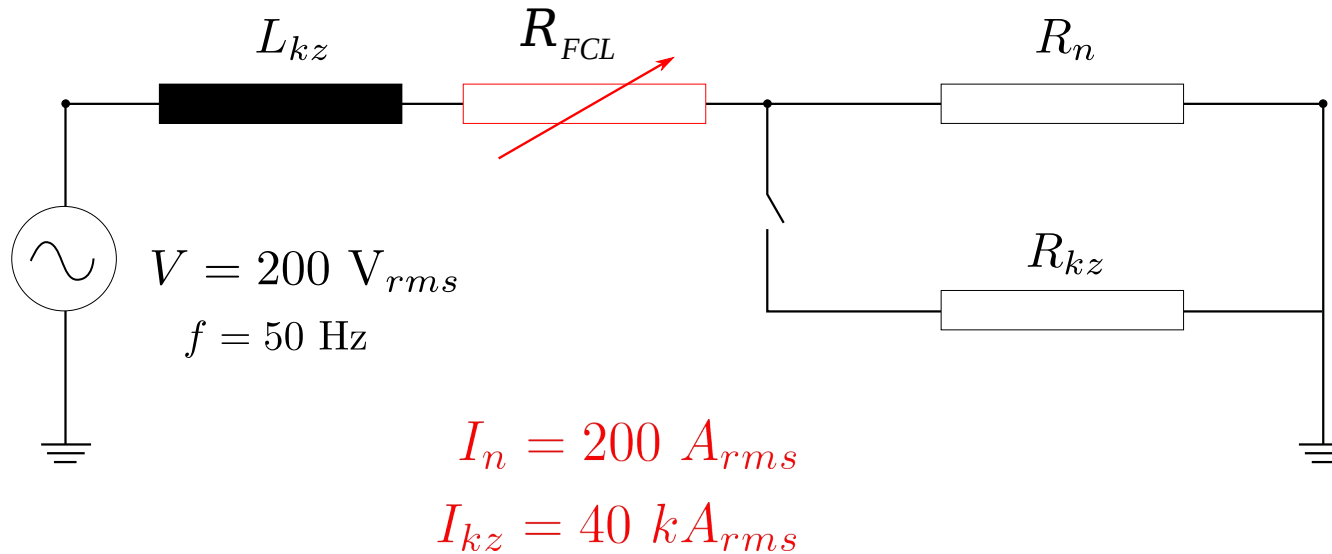- Simulation of the network with FCL (temperature dependent)




- With fault current limiter

$$L_{kz} \frac{di}{dt} = V - [R_{kz} + R_{FCL}(T)]i$$

- In this model, the resistance of the FCL no longer depends on time, but on the temperature of the materials involved.

■ Electrical Model
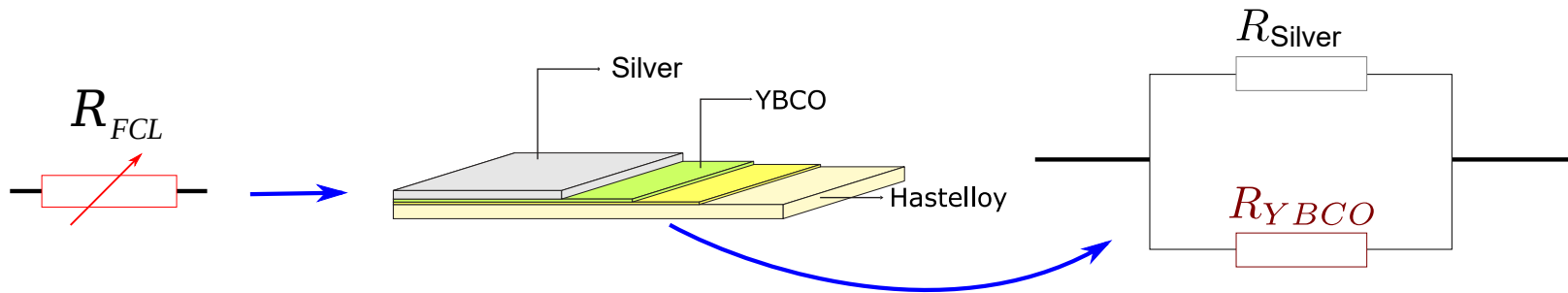
$$\frac{1}{R_{FCL}} = \frac{1}{R_{YBCO}} + \frac{1}{R_{Silver}}$$



■ Thermal Model

$$C_v \frac{\partial T}{\partial t} = R_{FCL} i^2 \xrightarrow{\text{Euler-method}} T_{(u+1)} = T_{(u)} + h \left[\frac{R_{FCL} i_{(u)}^2}{C_v} \right]$$

$$C_v = C_{Silver} + C_{Hastelloy} + C_{YBCO}$$


Temperature dependance of specific resistance

- Resistivity ρ of Silver and YBCO over T_c :

$$\rho = mT + z$$


- Below T_c :
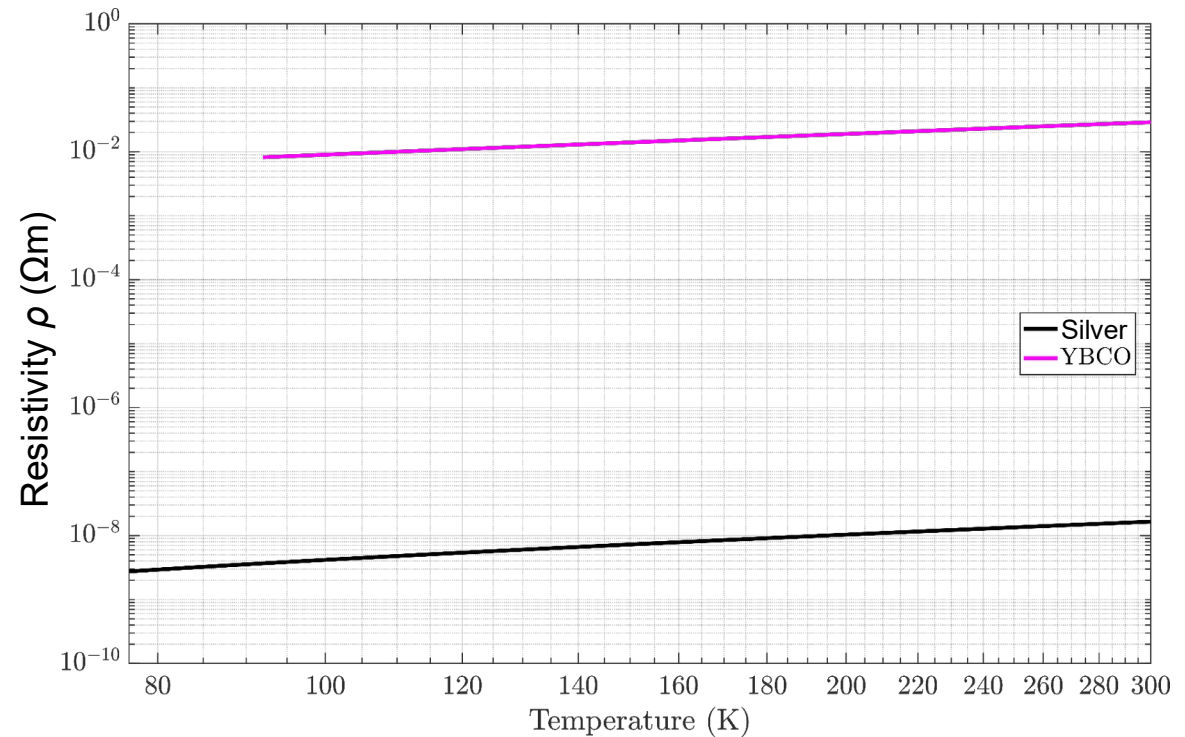
$$\rho_{YBCO} = \rho(T_c) \left[\frac{T}{T_c} \right]^n$$







Simulation Sequence - FCL

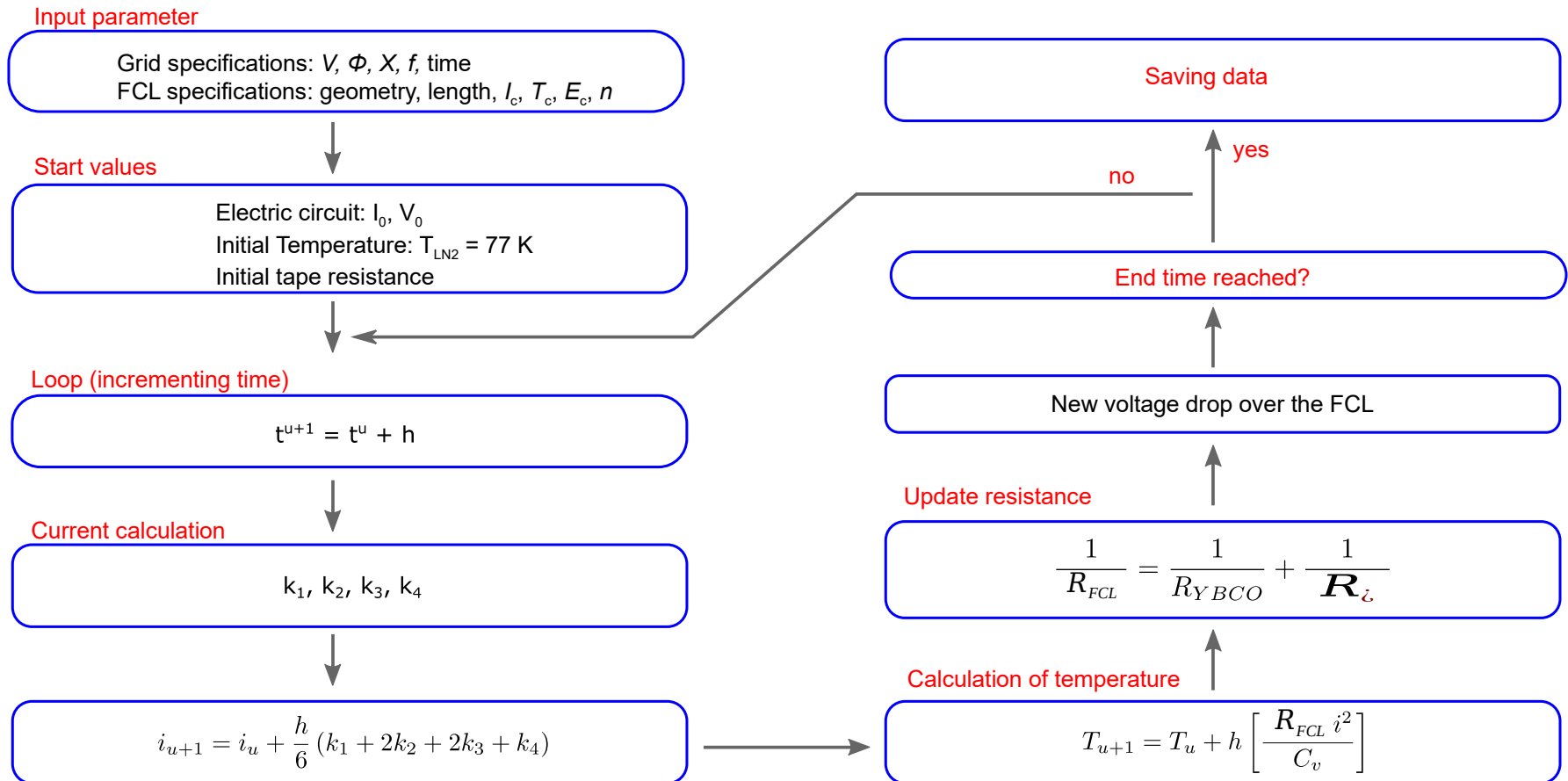- Flowchart for the simulation of the limiting behavior of a temperature-dependent FCL.



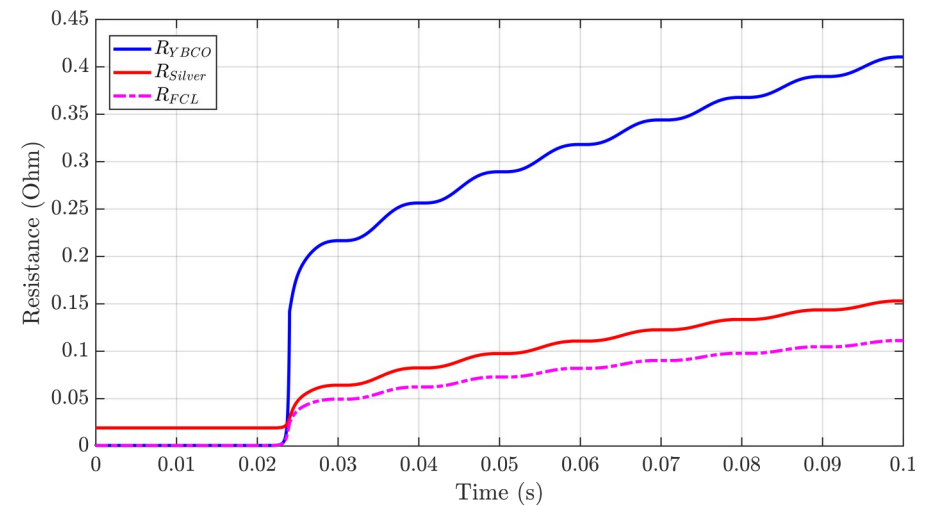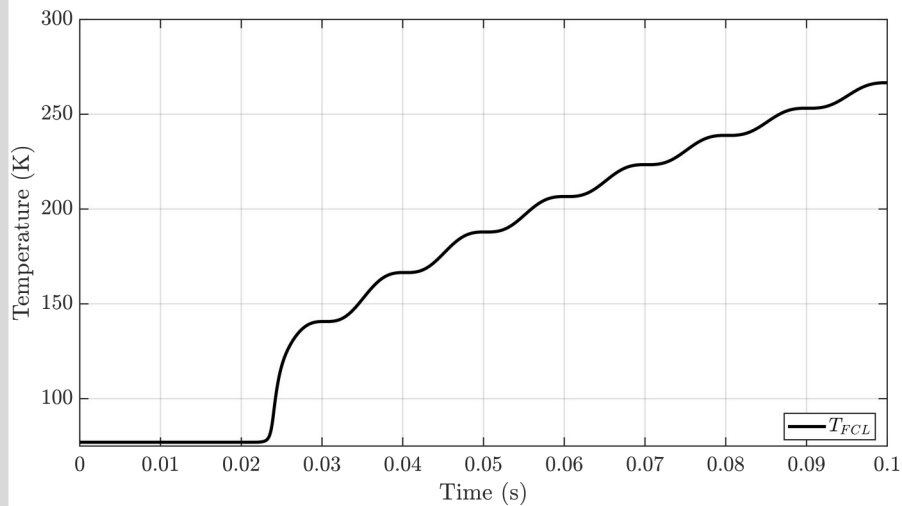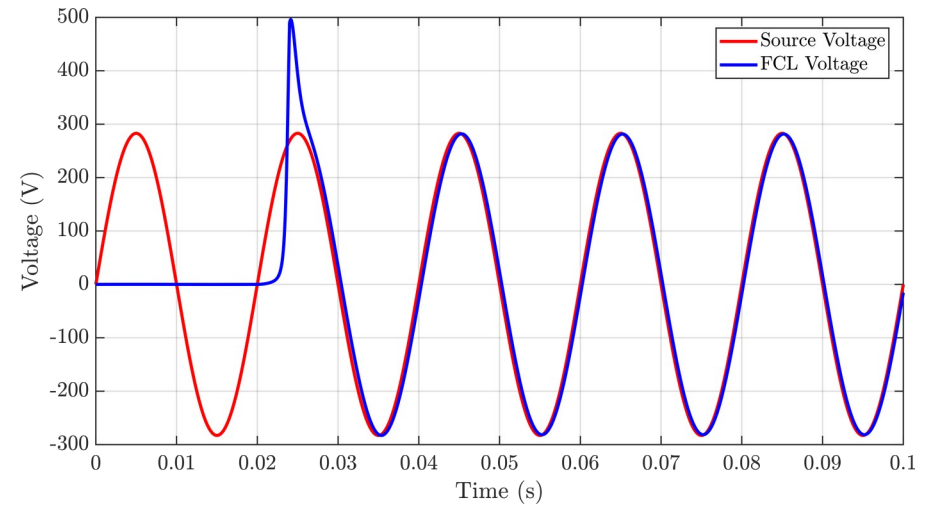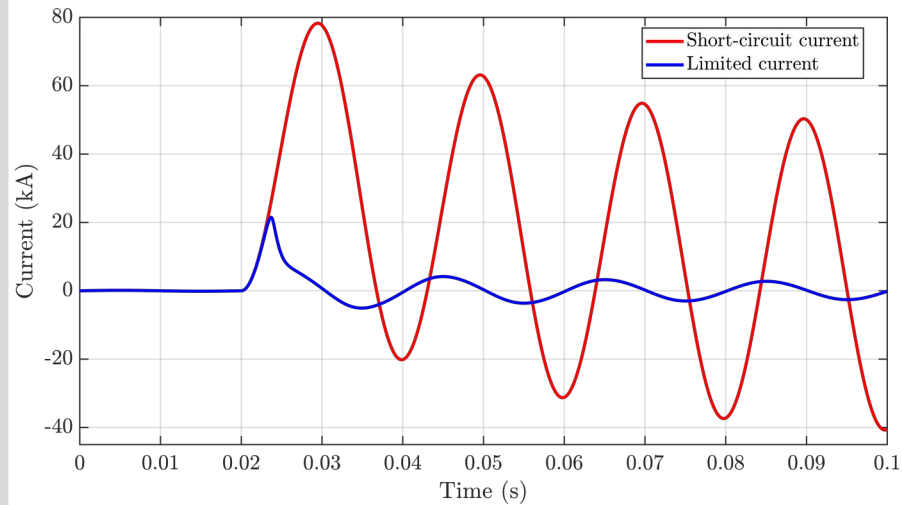Result – FCL temperature dependent transient behavior



■ Design a SFCL

- 10 kV
- 2 kA (Nominal Current)
- Fault Current = $40 \text{ kA}_{\text{rms}}$ ($X/R = 10$)
 - Determine number of HTS tapes
 - Find the total length of HTS material
 - Perform transient simulation and verify if maximal temperature is under 360 K