

Electronics for Physicists

Analog Electronics

Chapter 1; Lecture 02

Frank Simon

Institute for Data Processing and Electronics

26.10.2023

KIT, Winter 2023/24

Chapter 1

Basics

Part 1

- Charge, Current & Voltage
- Resistors
- Voltage- & Current Sources
- Capacitors

Overview

1. Basics

2. Circuits with R, C, L with Alternating Current

3. Diodes

4. Operational Amplifiers

5. Transistors - Basics

6. 2-Transistor Circuits



7. Field Effect Transistors

8. Additional Topics

- Filters
- Voltage Regulators
- Noise

- Electric charge: unit Coulomb [C]
 - $1 \text{ C} = 6.241 \times 10^{18} \text{ e}^-$ (for most “practical” cases: A very “large” unit)
 - $1 \text{ fC} = 10^{-15} \text{ C} = \sim 6000 \text{ e}^-$

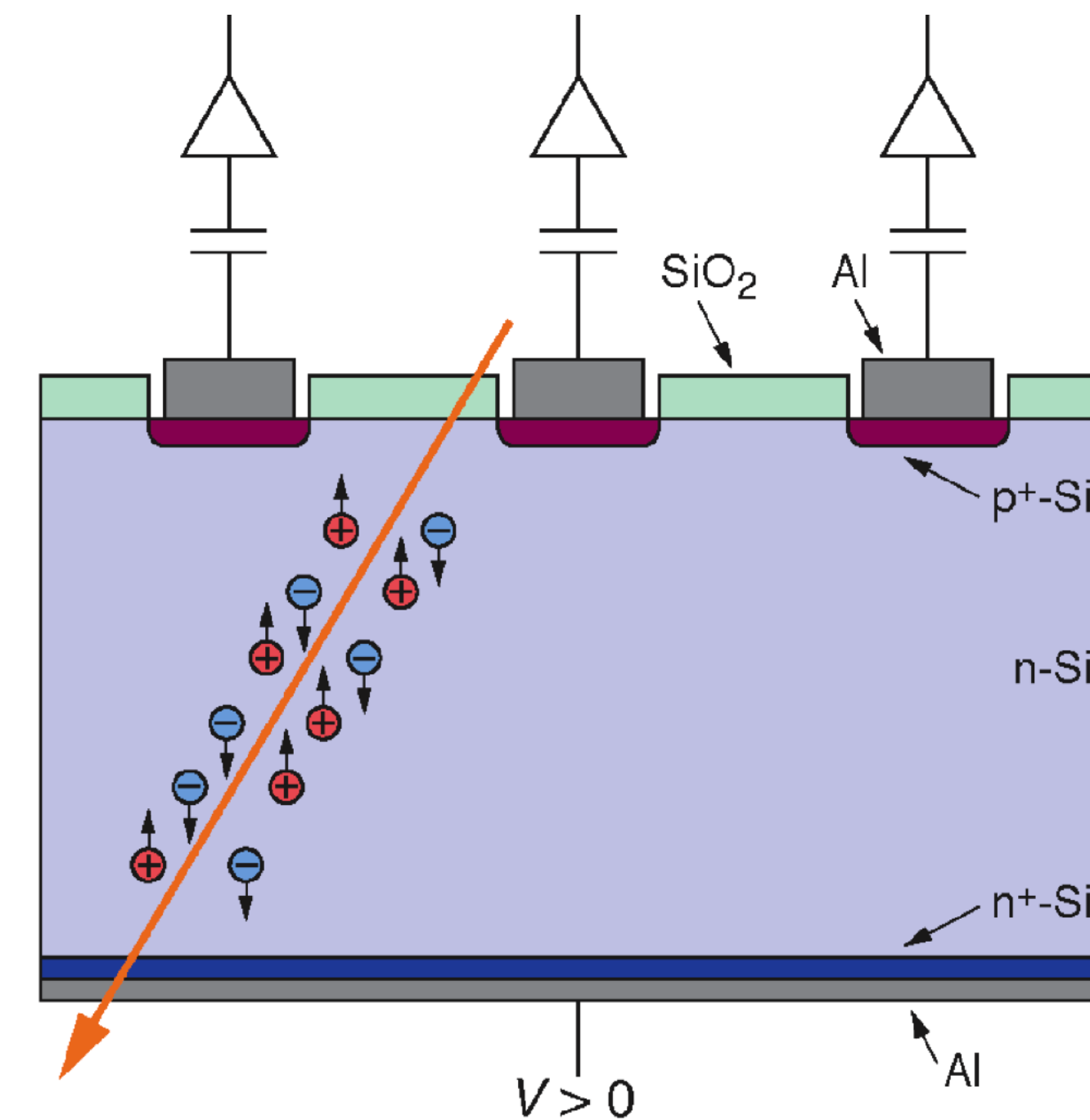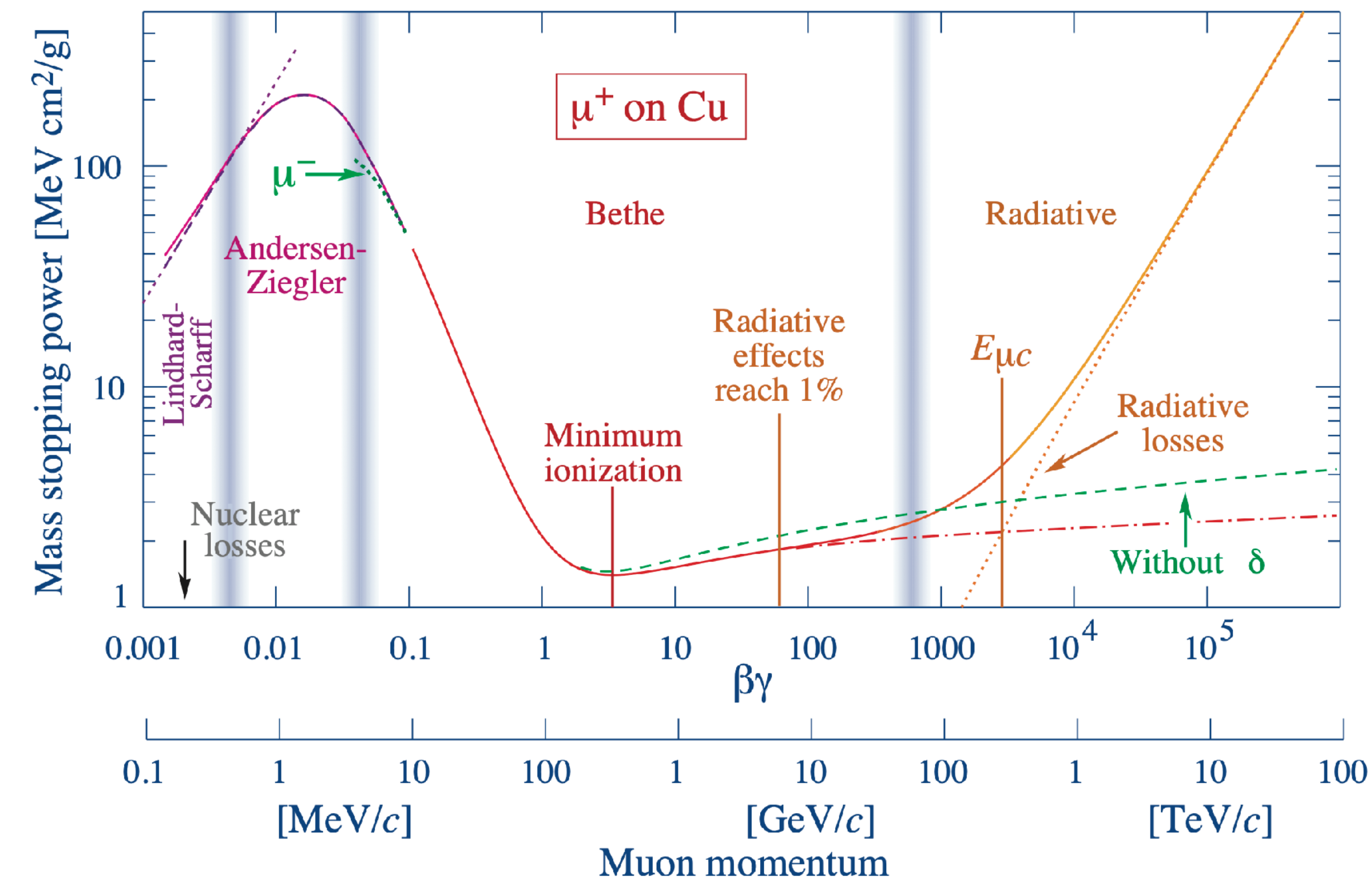Concrete example: Ionisation in particle detectors



In Silicon: 3.6 eV / e-hole pair; $\sim 80 \text{ e}^-$ per μm for MIPs
For 300 $\mu\text{m} \sim 4 \text{ fC}$

- Current = moving charge: charge / time

Strom

$$I = \frac{dQ}{dt}$$


I: current in Ampere [A] = [C/s]

Q: charge in C


t: time in seconds [s]

Convention: current flow from higher (+)
to lower (-) potential.

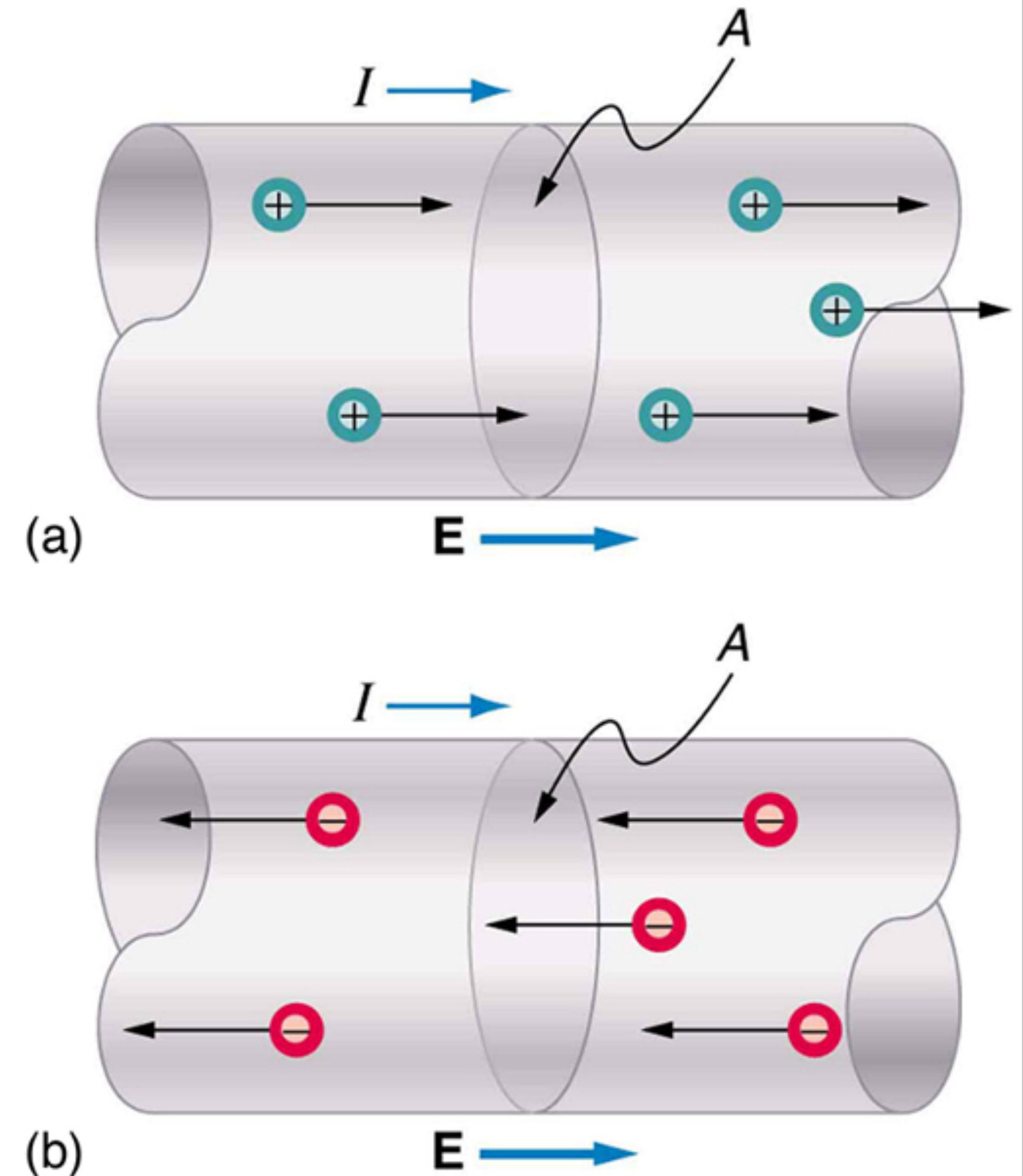For metallic conductors: flow of electrons, opposite to
the conventional direction of current flow.





- LHC magnets

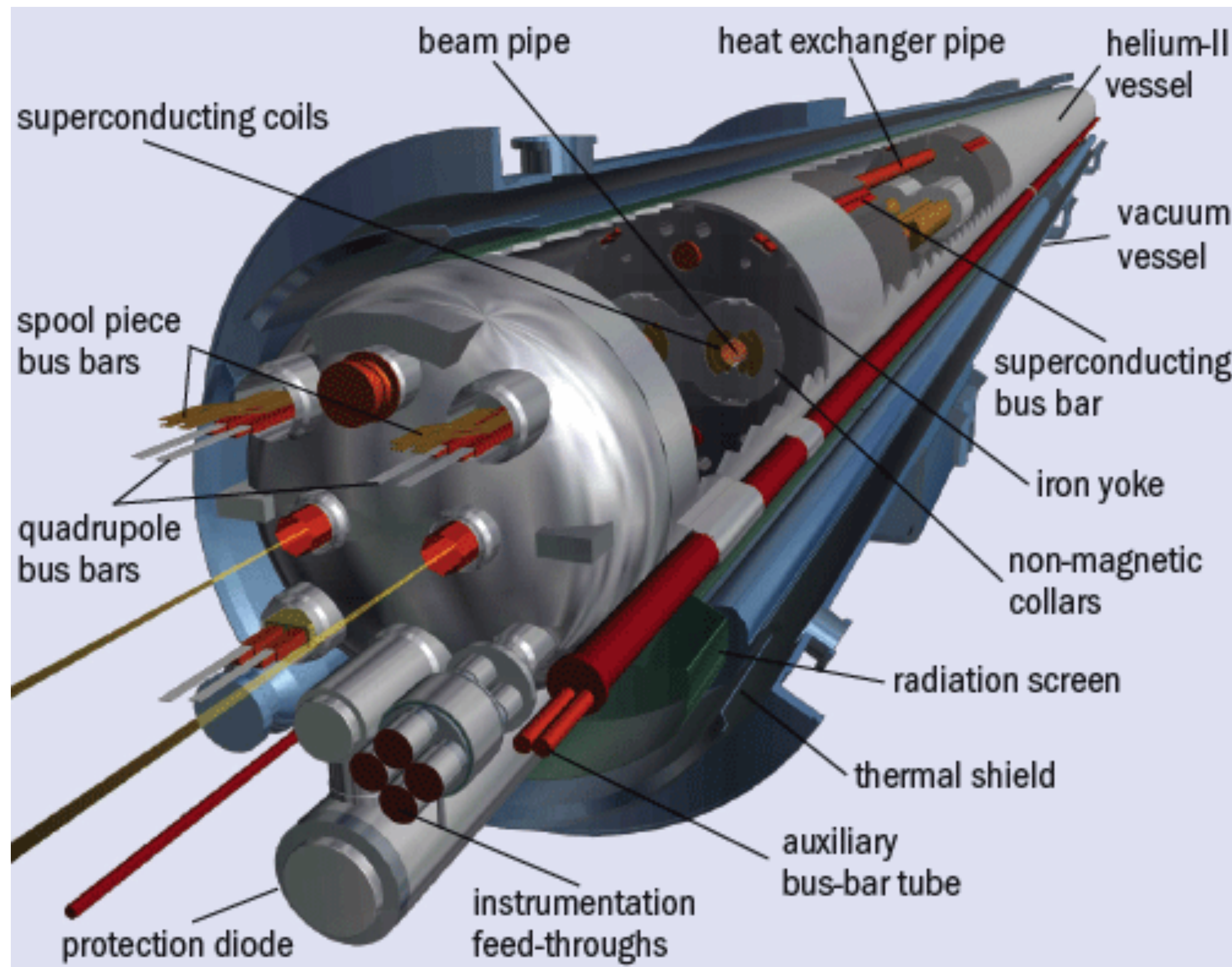

magnetic field up to 8.3 T
current up to 12 kA for
7 TeV beam energy

- leakage current in SiPMs: nA - μ A

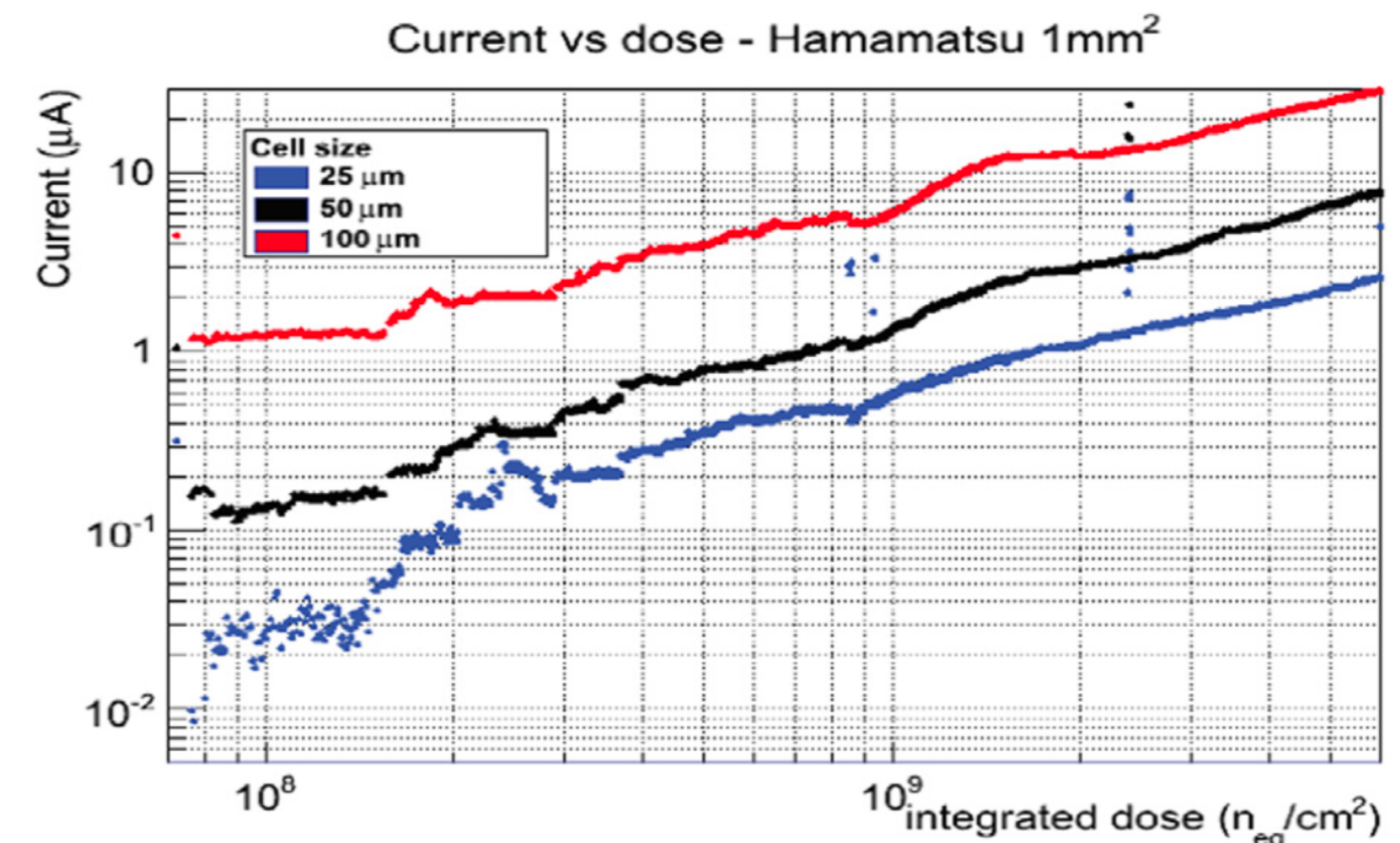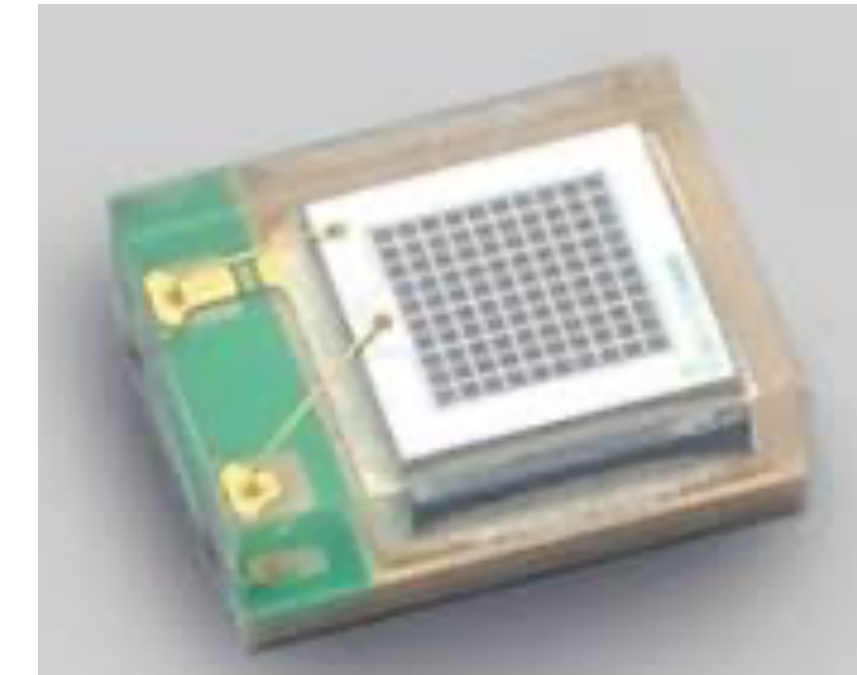

- Voltage, oder potential difference:

Energy W that has to be invested to move an electric charge q in a field E .

Also given by the electric field integrated over the distance of movement.

$$\frac{W}{q} = U = \int \vec{E} d\vec{s}$$

U : Voltage in Volt [V]

E : electric field strength [V/m]

s : distance [m]

In typical applications: Electric fields are relevant for example in detectors, electric circuits normally only the voltage is of interest.

Resistors, Ohm's Law

The connection of current and voltage

$$U = RI$$



Widerstand

R: resistance in Ohm [$\Omega = \text{V/A}$]

Often used as well: *Conductance*

$$G = 1/R$$

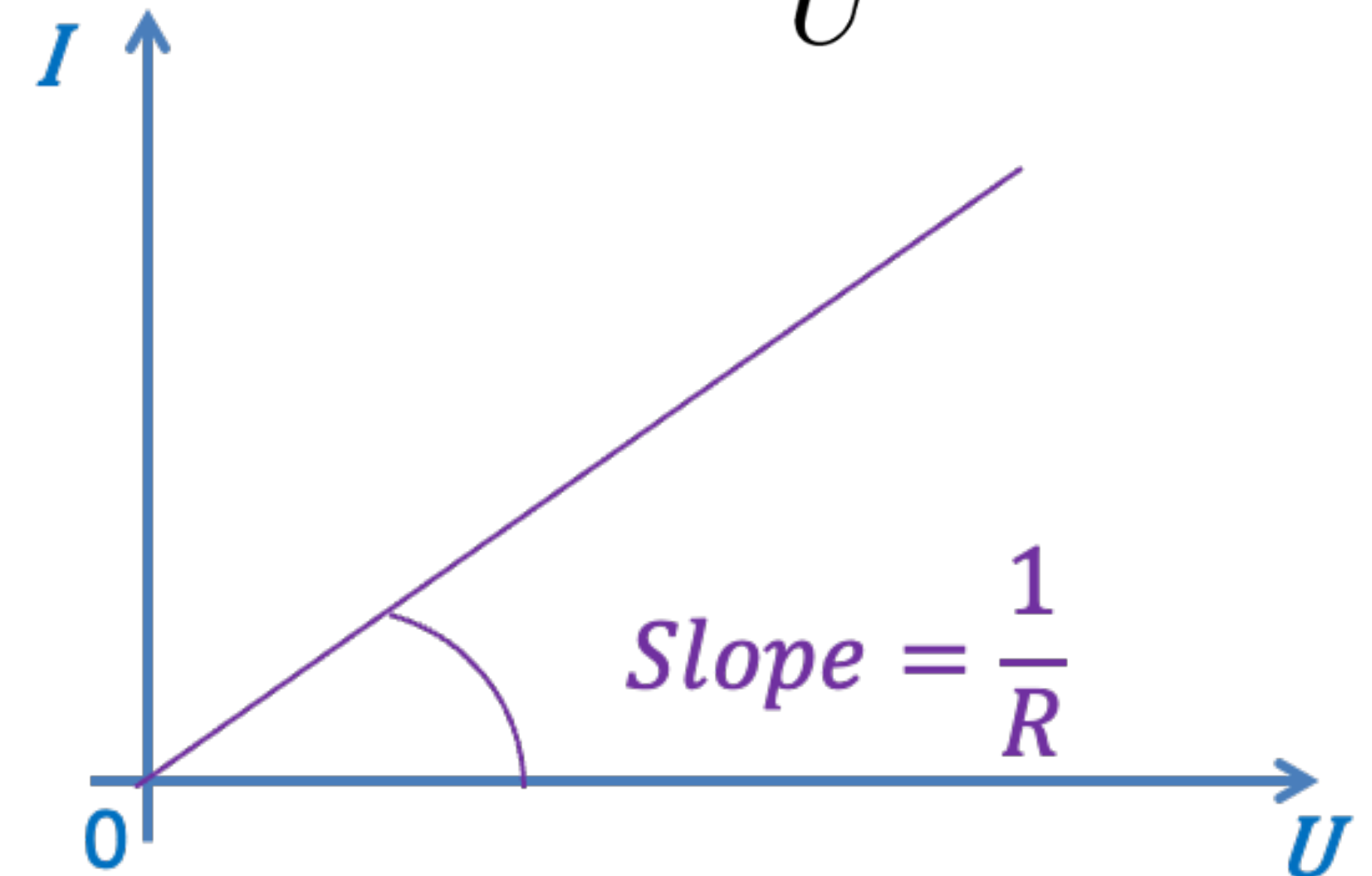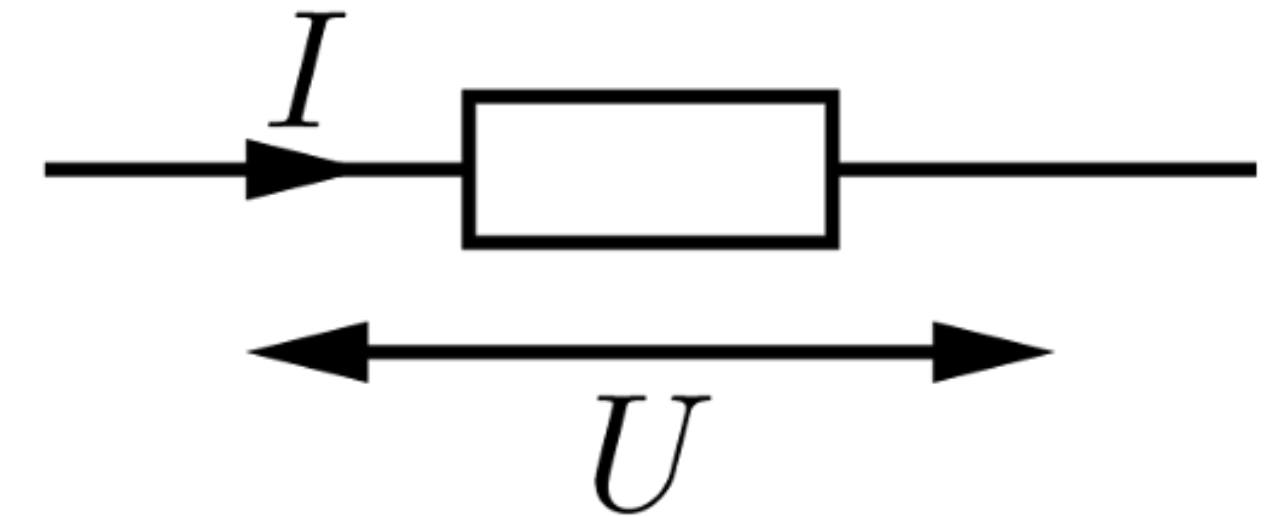- What Ohm's law means:
 - Voltage results in current flow
 - Current flow through a resistor results in a voltage drop across the resistor



- Power: Current and Voltage


$$P = UI = \frac{U^2}{R} = I^2 R$$

P: power in Watts [W = VA]

- In our daily lives: Power as a cost factor: “energy consumption” $P \cdot t \rightarrow \text{kWh} / \text{MWh} / \text{TWh} \dots$
- For detectors in high energy physics: power requires cooling!

Power in Detectors


Example: Power loss in cables

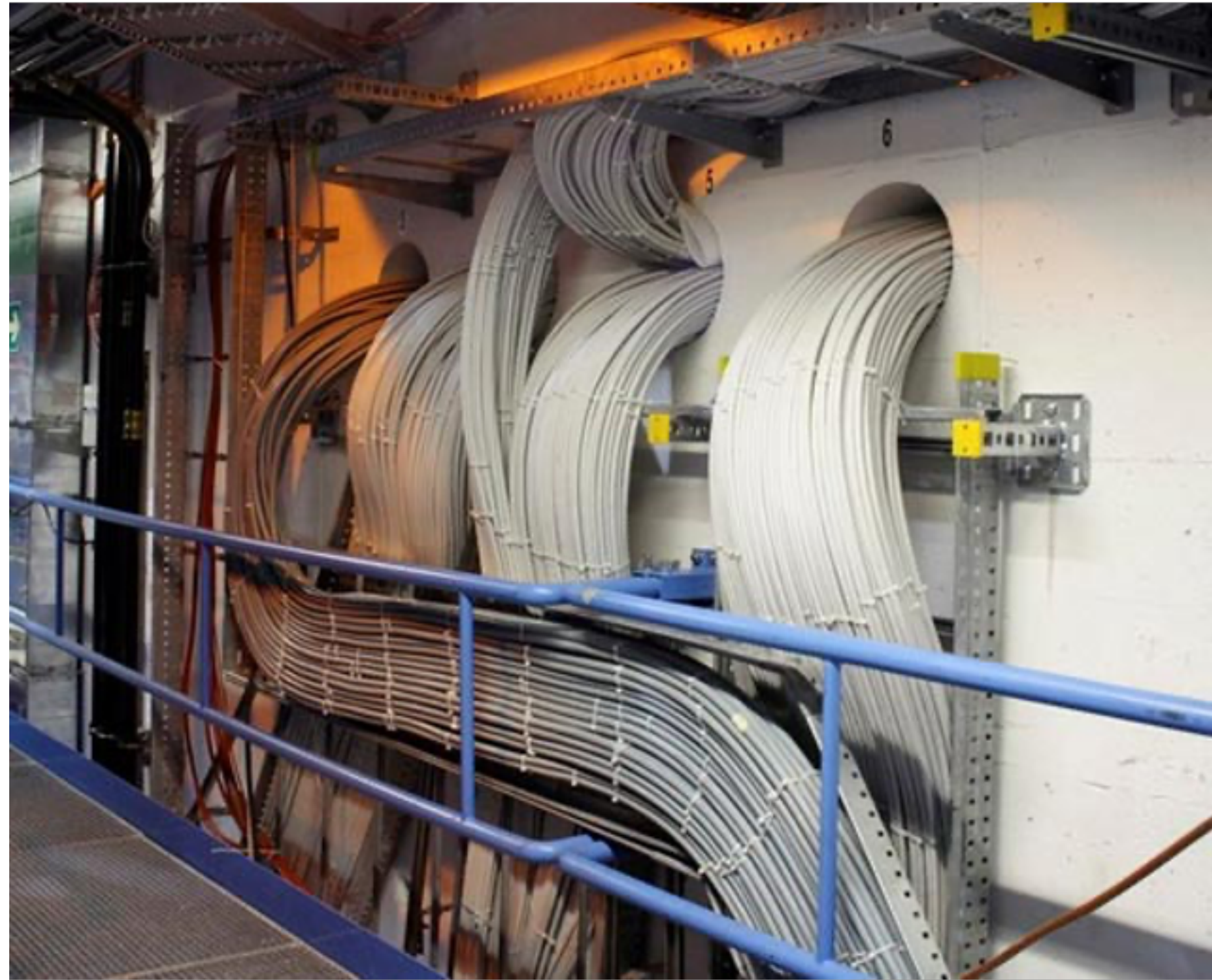

- Low voltage supply cables of the ATLAS SCT detectors
4 Ω cable resistance for 100 m long cables; 1 A for each of the 4000 modules
 $P = 4 \Omega \times 1 A^2 \times 4000 = 16 \text{ kW} \Rightarrow$ Pure power loss in the cables: Heating of the cables!

Reducing Power

Example: Frontend ASICs

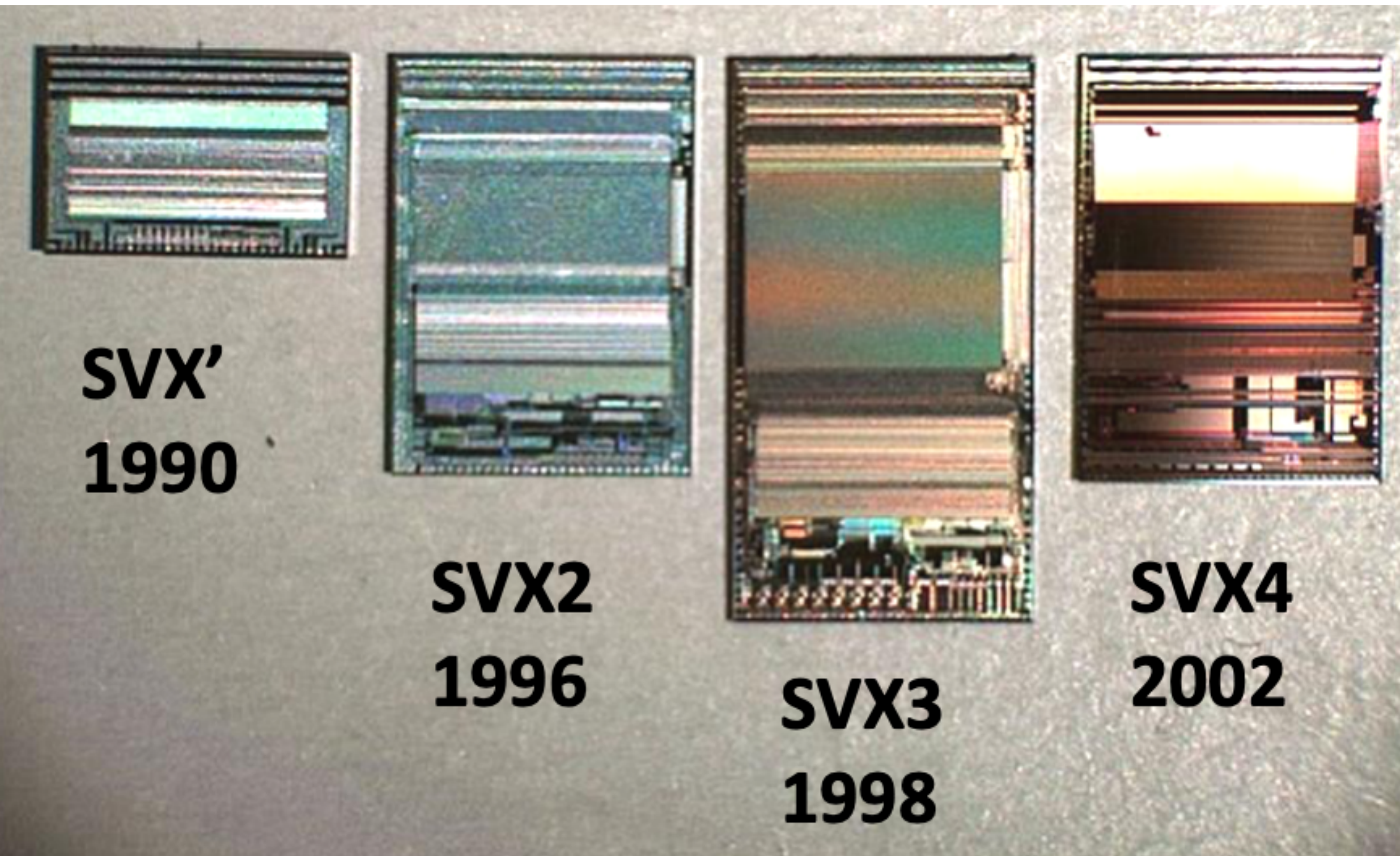


- The SVX2 ASIC was central for the discovery of the Top quark at Fermilab: Silicon strip, D0 Experiment; Further development as SVX3, 4 also for CDF
- Smaller feature size (transistor size) make ASICs smaller
- Additional functionality makes them bigger
- Smaller feature size typically means lower voltage, and with that also smaller charges: Lower power!
(This simple logic does not apply for technologies below 65 nm)

Specific Resistance

Spezifischer Widerstand

- A material property:

$$R = \rho \frac{l}{A}$$

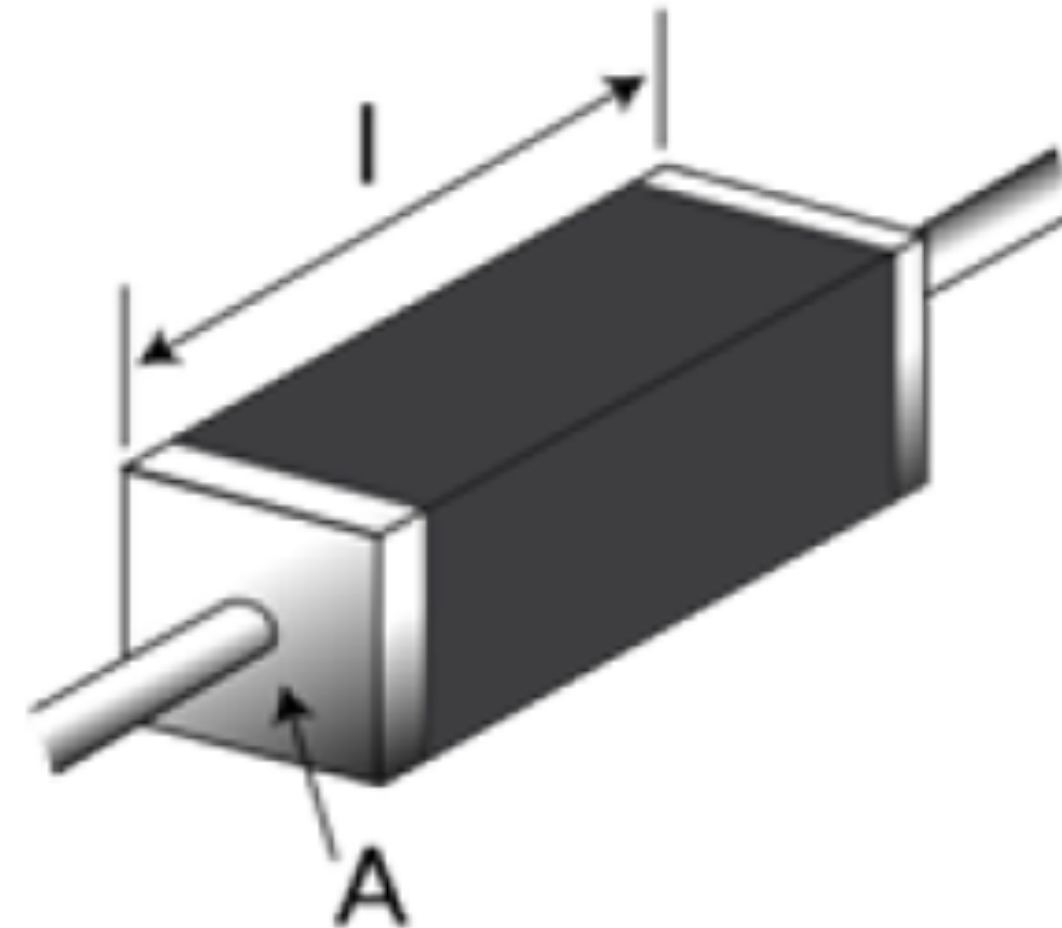

material	$\rho [10^{-8} \Omega \text{ m}]$	Z
silver	1,59	47
copper	1,68	29
gold	2,21	79
aluminium	2,65	13

Resistance of different metals at 20° C

R: Resistance [Ω]

ρ : specific resistance [$\Omega \text{ m}$]

A: (Cross section-) Area of resistor [m^2]

l: Length of resistor [m]

- ➡ The resistance increases with length, reduces with larger cross section (also applies for other components, such as field effect transistors (FETs))
- ➡ The material of the resistor determines the properties - also metals have a range of different values

Specific Resistance: Consequences

High energy physics view

- (Power) Cables are a significant fraction of the (unwanted) material of particle detectors, in particular in tracking systems in collider experiments: The choice of the right material is of high importance.

material	$\rho [10^{-8} \Omega \text{ m}]$	Z
silver	1,59	47
copper	1,68	29
gold	2,21	79
aluminium	2,65	13


Multiple scattering determined by radiation length X_0 :
 $\sim A/Z^2$ in g/cm^2 , also depends on density: $\sim 1/\rho$
(NB: Large is good, means small Z, small ρ)

Copper: 14.4 mm; Aluminum: 88.9 mm


=> Despite higher specific resistance much less X_0 when using Al.

ATLAS tracker material:

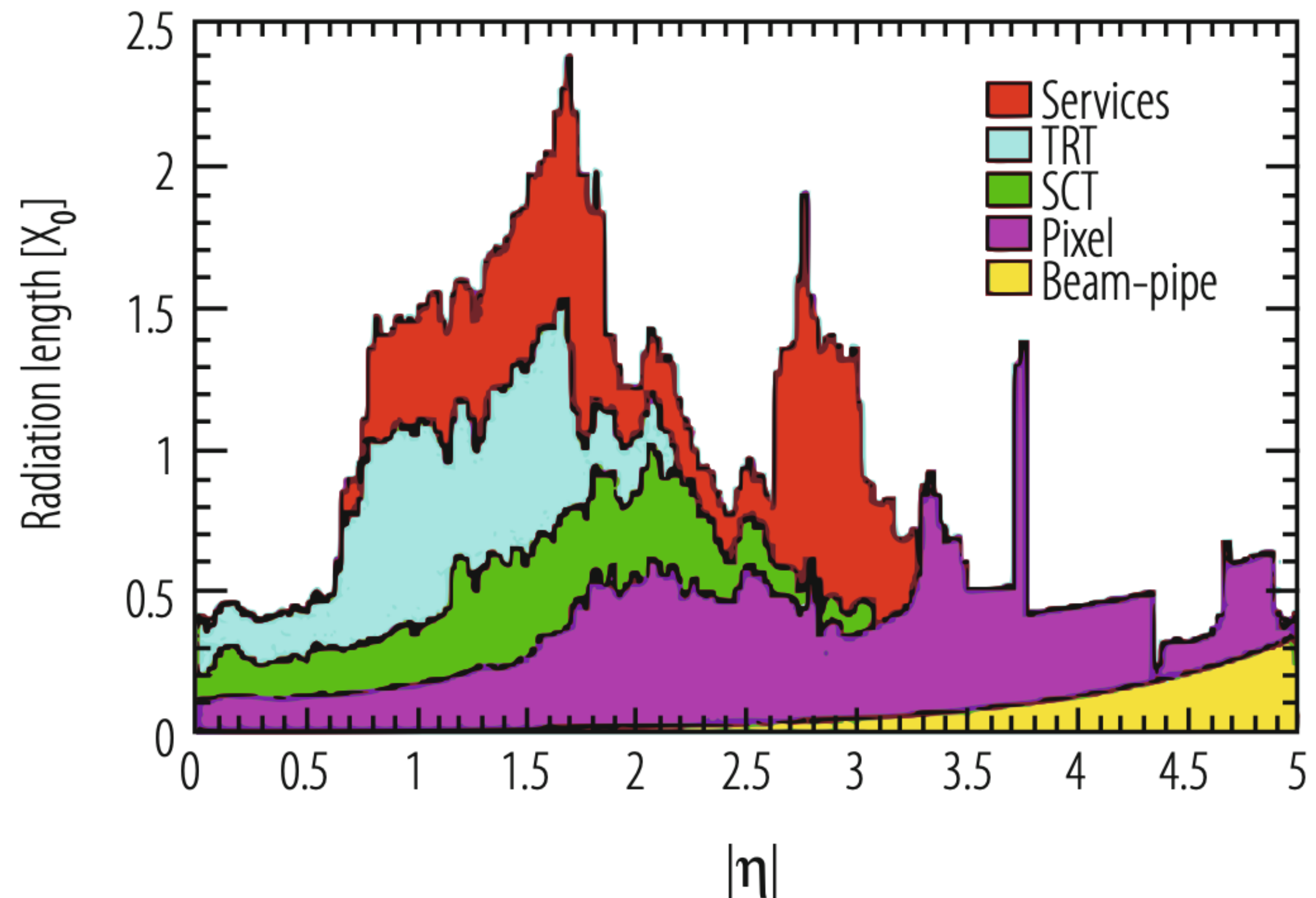
“Services”: Cables beyond the detector itself (cables, cooling). Distribution of detectors include “internal” services within detector volume



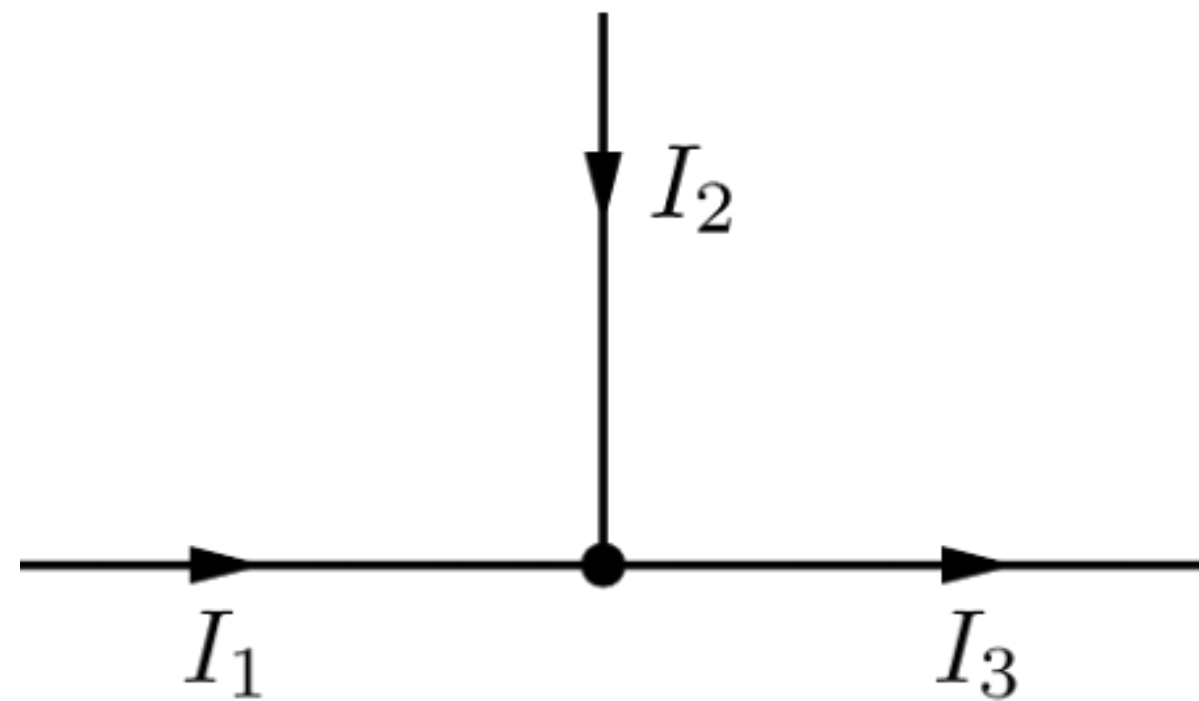- Follow from basic conservation laws:
Charge, energy



$$I_1 + I_2 = I_3$$

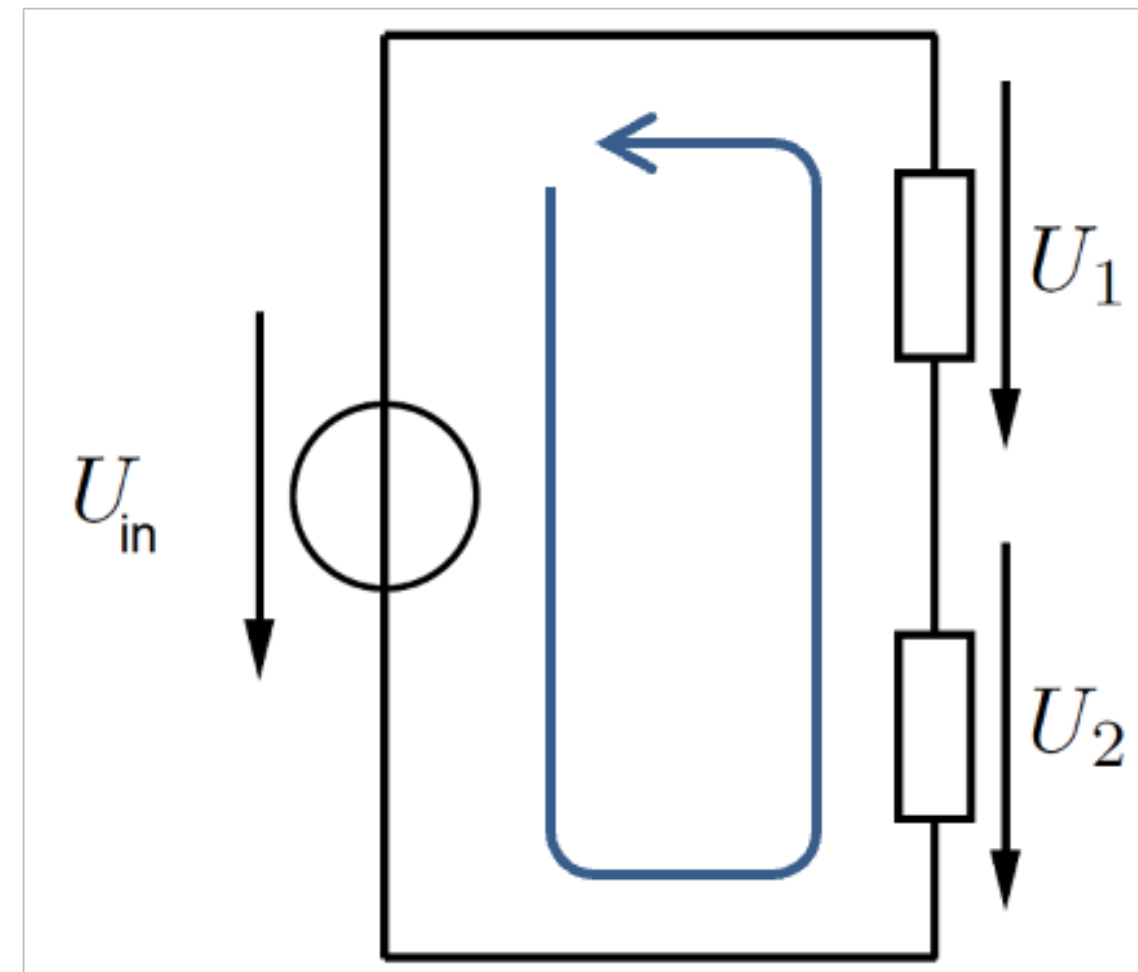

note the direction of the arrows!

Kirchhoff's Voltage Law KVL

Maschenregel / 2. Kirchhoffsches Gesetz

$$U_{in} - U_2 - U_1 = 0$$

Kirchhoff's Current Law KCL

Knotenregel / 1. Kirchhoffsches Gesetz


Charge conservation:

Current entering the node =
current leaving the node

Energy conservation:


The sum of all voltage drops around a loop ("Masche") is 0.
[Applies only without induction due to time-dependent magnetic fields, KVL also follows from the induction law]

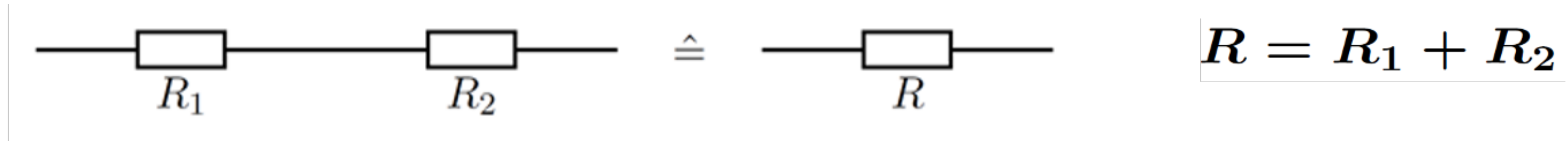- Resistors in series (“*Reihenschaltung*”)



Same current through all resistors in series.


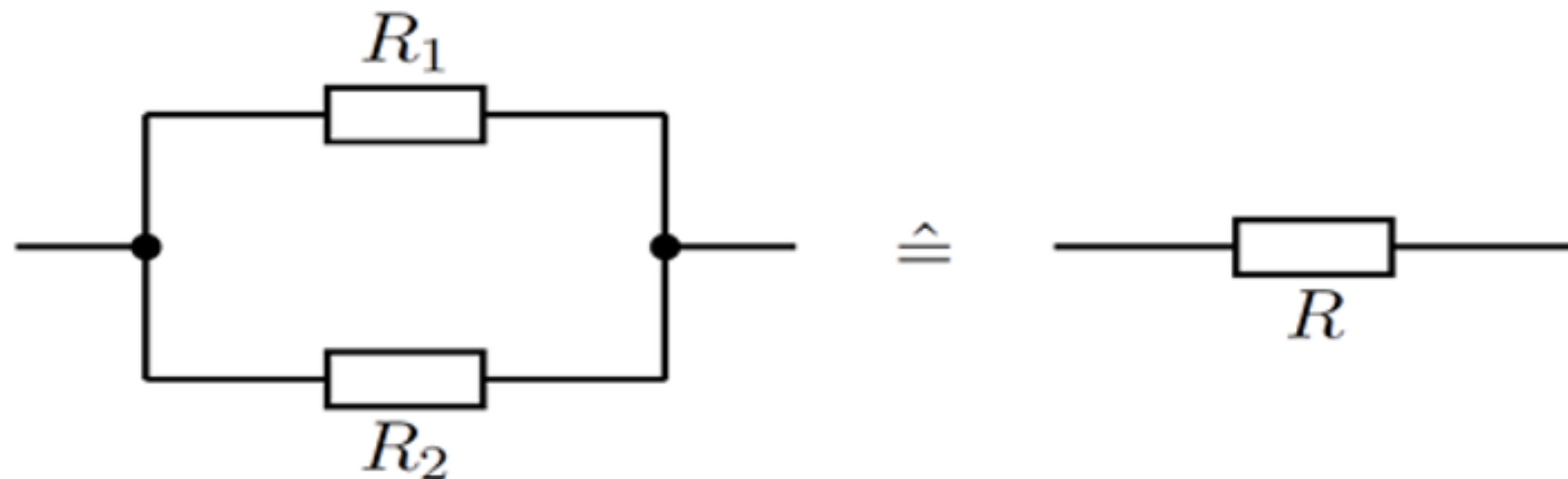
- Parallel resistors (“*Parallelschaltung*”)



$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$$

Same voltage drop across all parallel resistors.

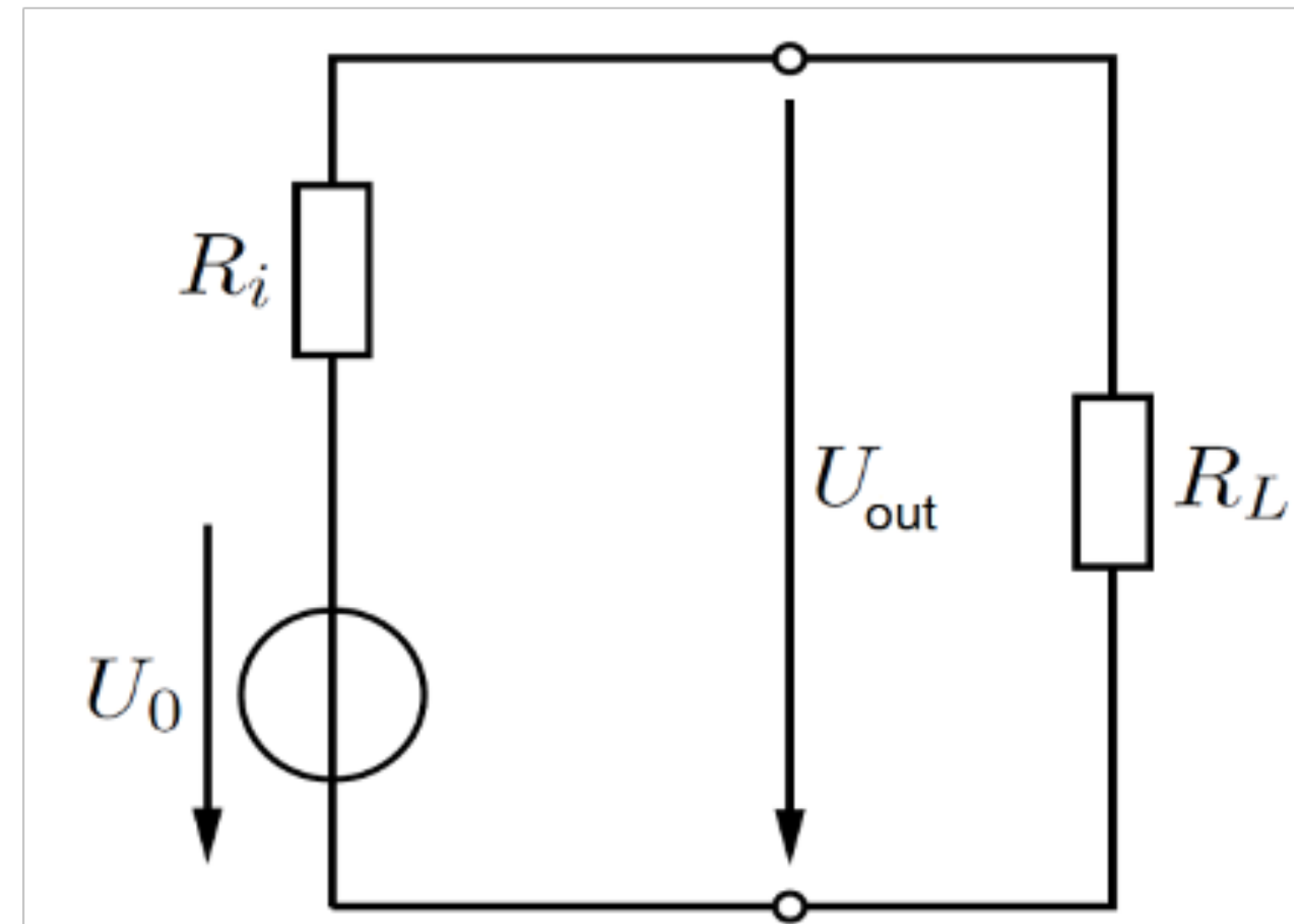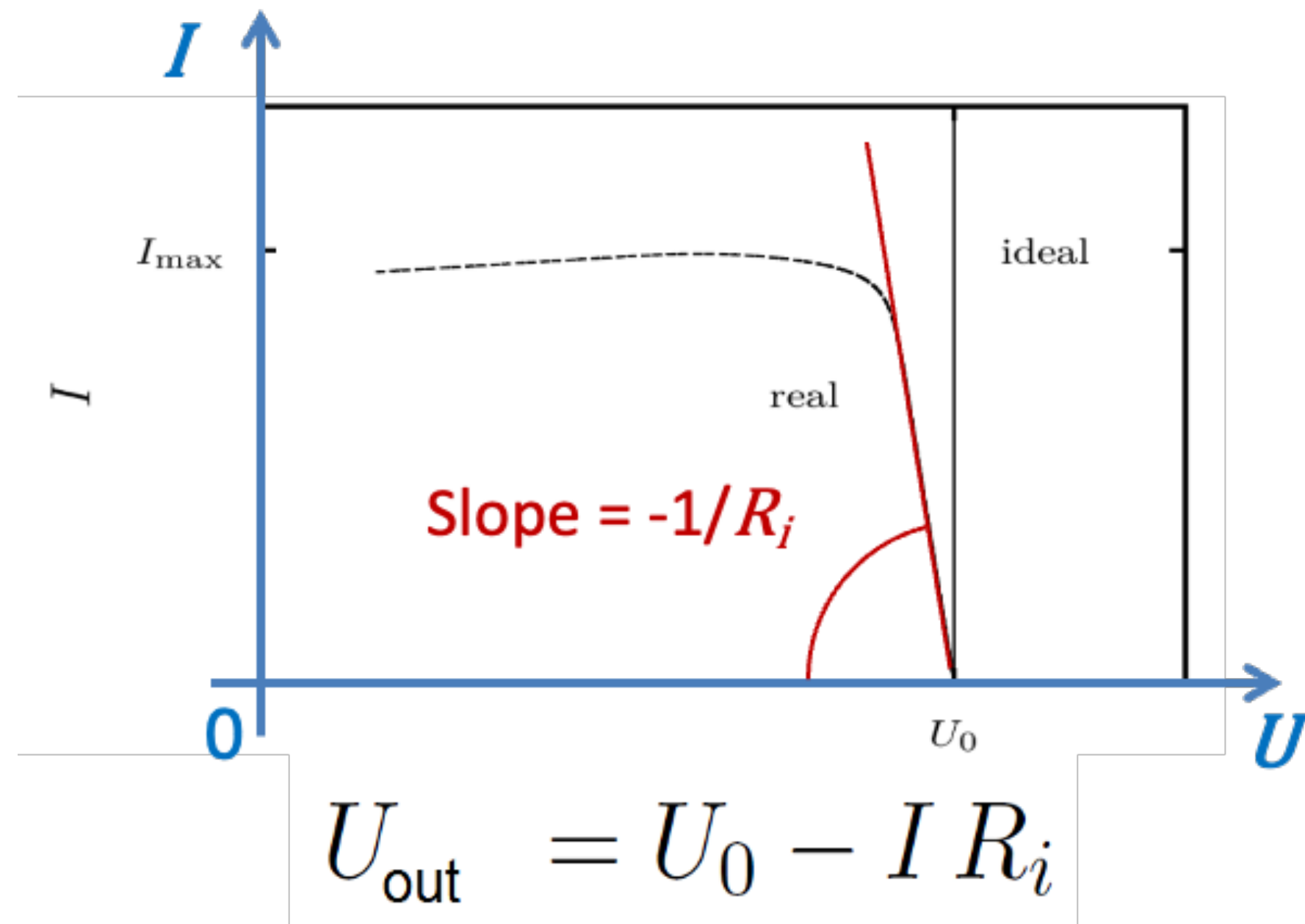- Two types of power supplies (“*Stromversorgungen*”): **voltage sources**, **current sources**
- Ideal voltage source: Constant voltage, independent of load current



R_i : internal resistor

R_L : load resistor

lab power supply: $\sim 10^{-5} \Omega$

car battery: $\sim 10^{-2} \Omega$


(BEV battery cell: $\sim 10^{-3} \Omega$)

Mono-cell: $0.1 - 1 \Omega$


Voltage sources are best at:

- no (or small) load $R_L \gg R_i$
- small load currents
- constant current

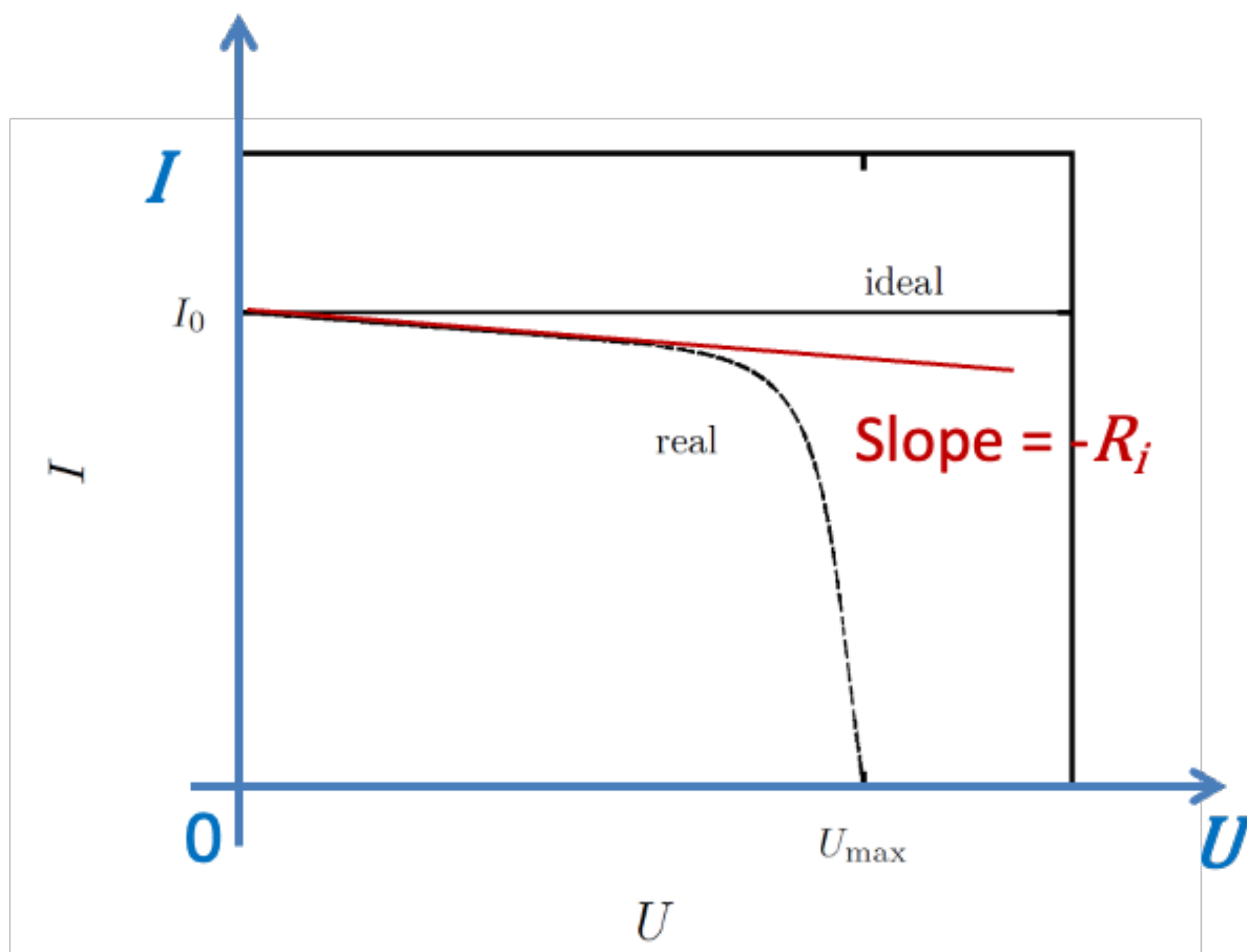- Two types of power supplies (“*Stromversorgungen*”): **voltage sources**, **current sources**
- Ideal current source: Constant current independent of voltage at the load




$$I = I_0 - \frac{U}{R_i}$$

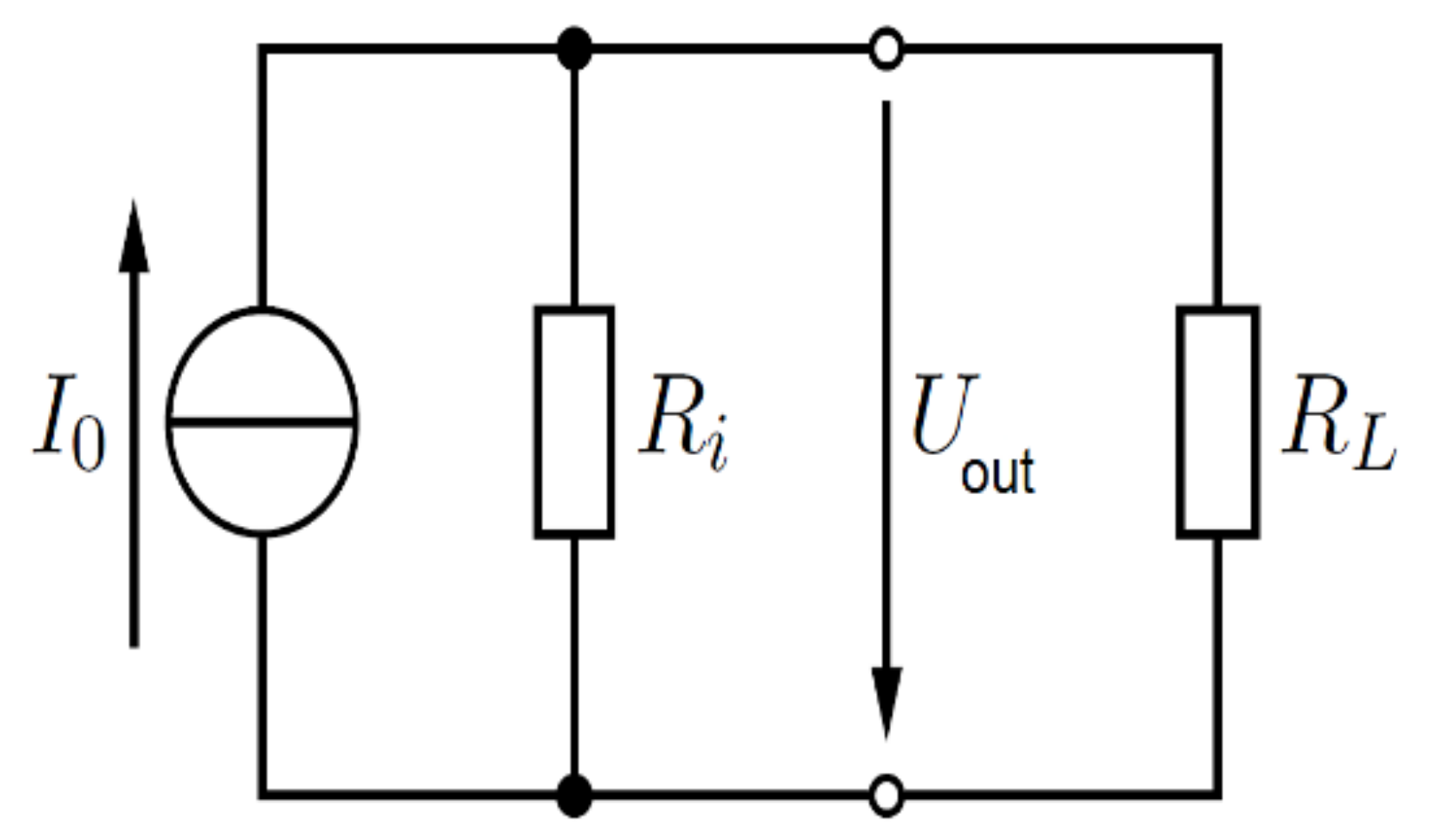


Current sources are at their best in short-circuit:
 $R_L \ll R_i$

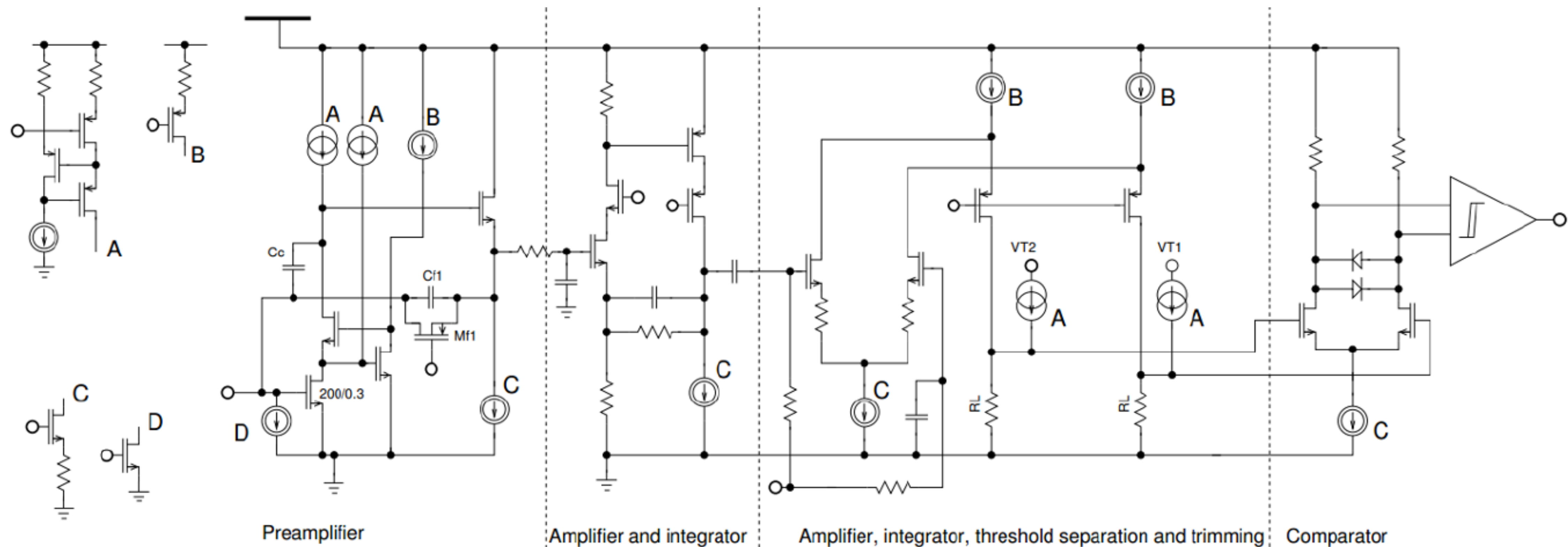- Current sources are quite common (even though we mostly “see” voltage sources in everyday life):
Central elements in integrated circuits / ASICs



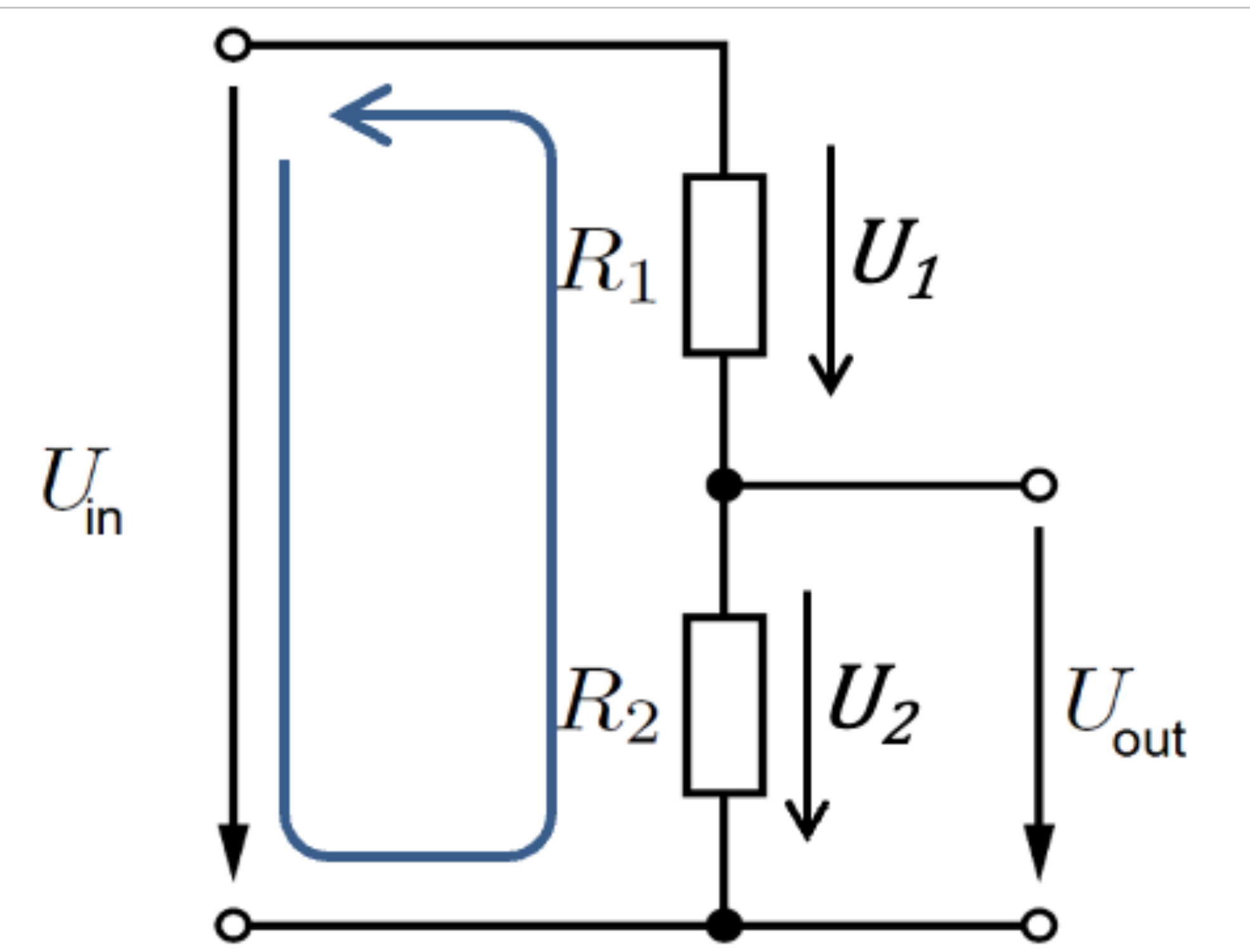Example ABCN ATLAS silicon detector readout ASIC prototype - different current sources in operation

- Voltage dividers are some of the most common circuits



Assumption: R_1 and R_2 are relatively large, load currents are small

Kirchhoff's Voltage Law (KVL):

$$U_{in} = U_1 + U_2 = (R_1 + R_2) I \quad \text{and} \quad U_{out} = R_2 I$$

$$U_{out} = U_{in} \frac{R_2}{R_1 + R_2}$$

- Symbol:



$$Q = C U$$

C: Capacity in Farad [F = As/V]

Q: Charge [C = As]

U: Voltage [V]

Current and voltage with capacitors:

$$I = \frac{dQ}{dt} = C \frac{dU}{dt}$$

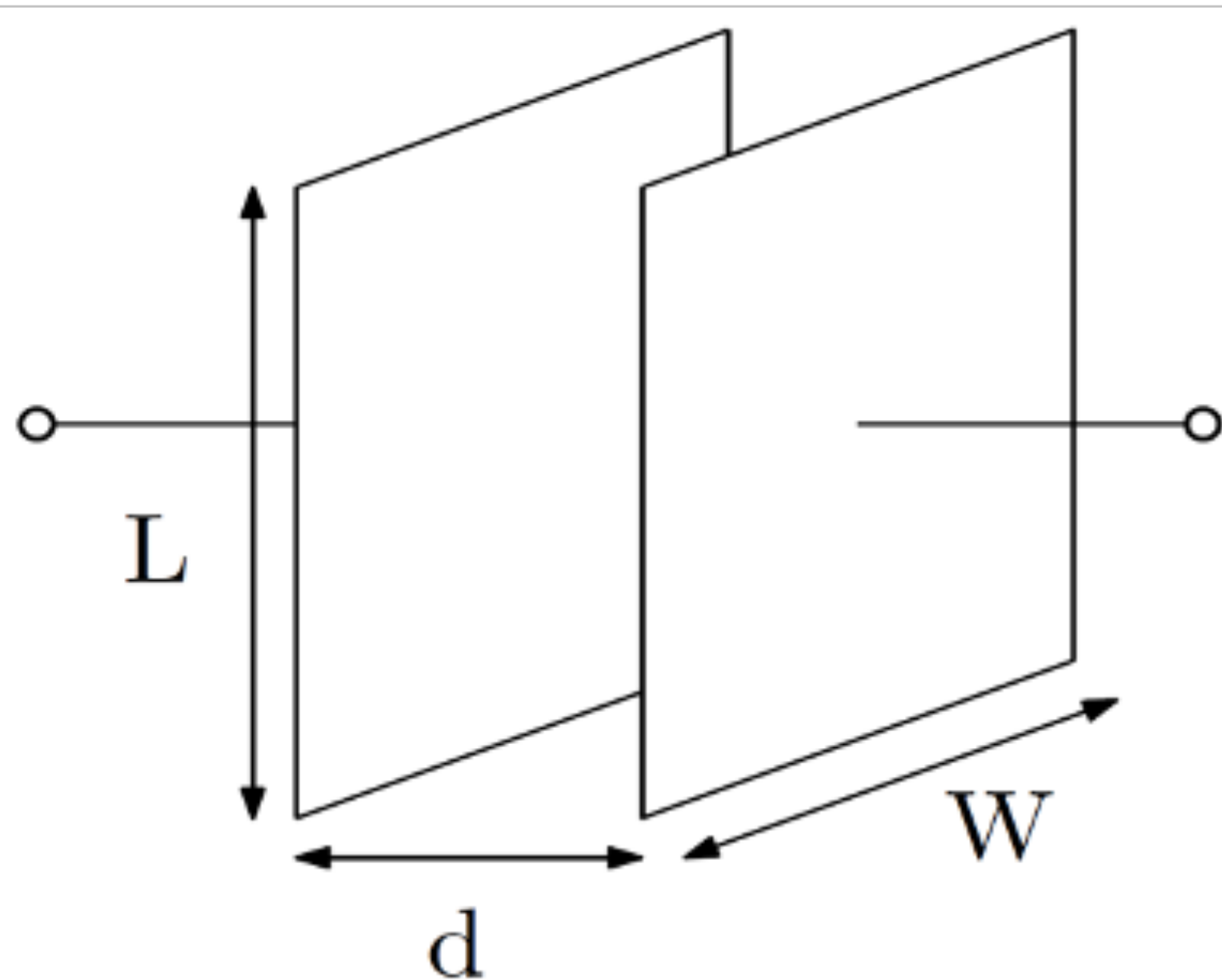


Plate capacitor

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$


$$\epsilon_0 = 8,859 \cdot 10^{-12} \text{ [F/m]}$$

Stored energy:

$$E = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} C U^2$$

Example: Capacity of Silicon Detectors

Silicon Strip Detectors

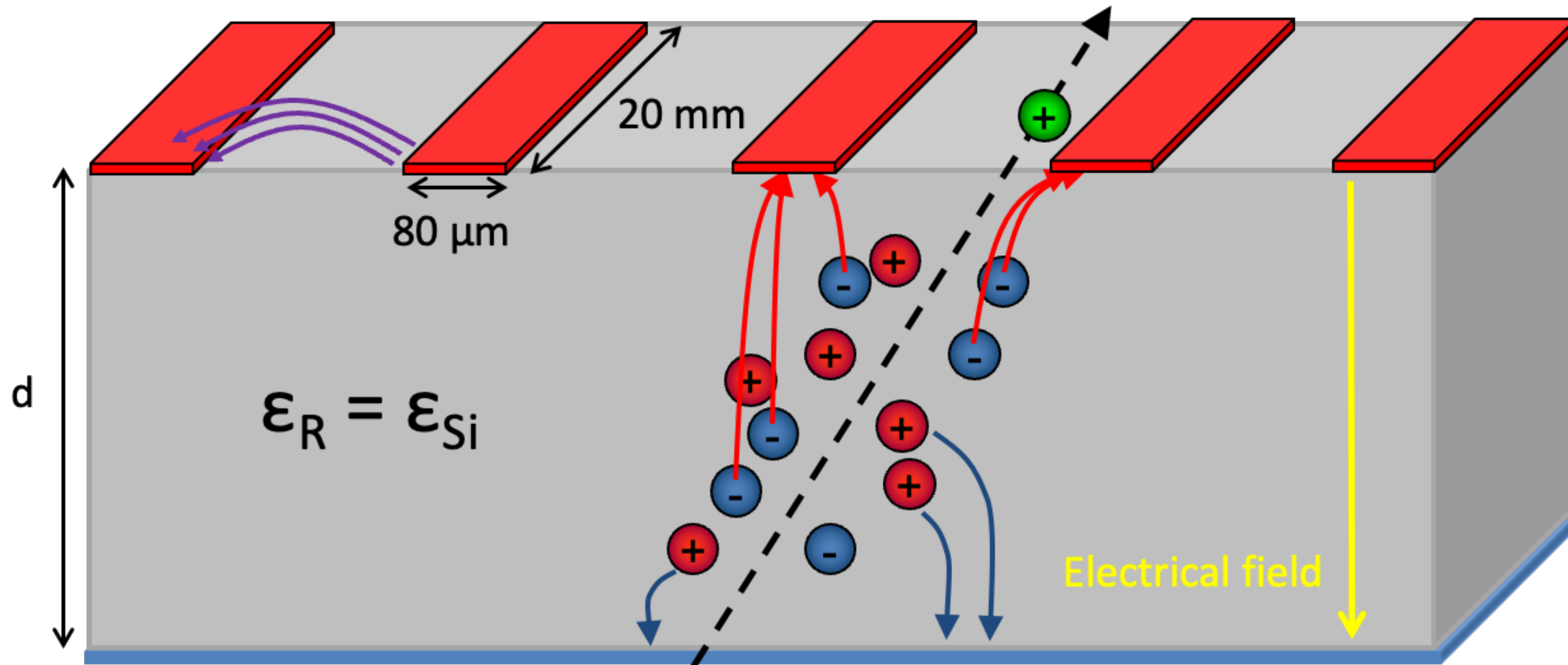

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

Capacity of one strip:

$$A = 80 \mu\text{m} \times 20 \text{ mm}$$

$$d = 300 \mu\text{m}$$


$$\epsilon_0 = 8.9 \times 10^{-12} \text{ F/m and}$$

$$\epsilon_R = 11.8 \text{ (Silizium)}$$

With full depletion, and neglecting neighboring strips and other effects: $\sim 0.56 \text{ pF}$


When considering all effects (neighboring strips dominate!): $1\text{-}2 \text{ pF/cm} \times \text{strip length}$

- Parallel capacitors

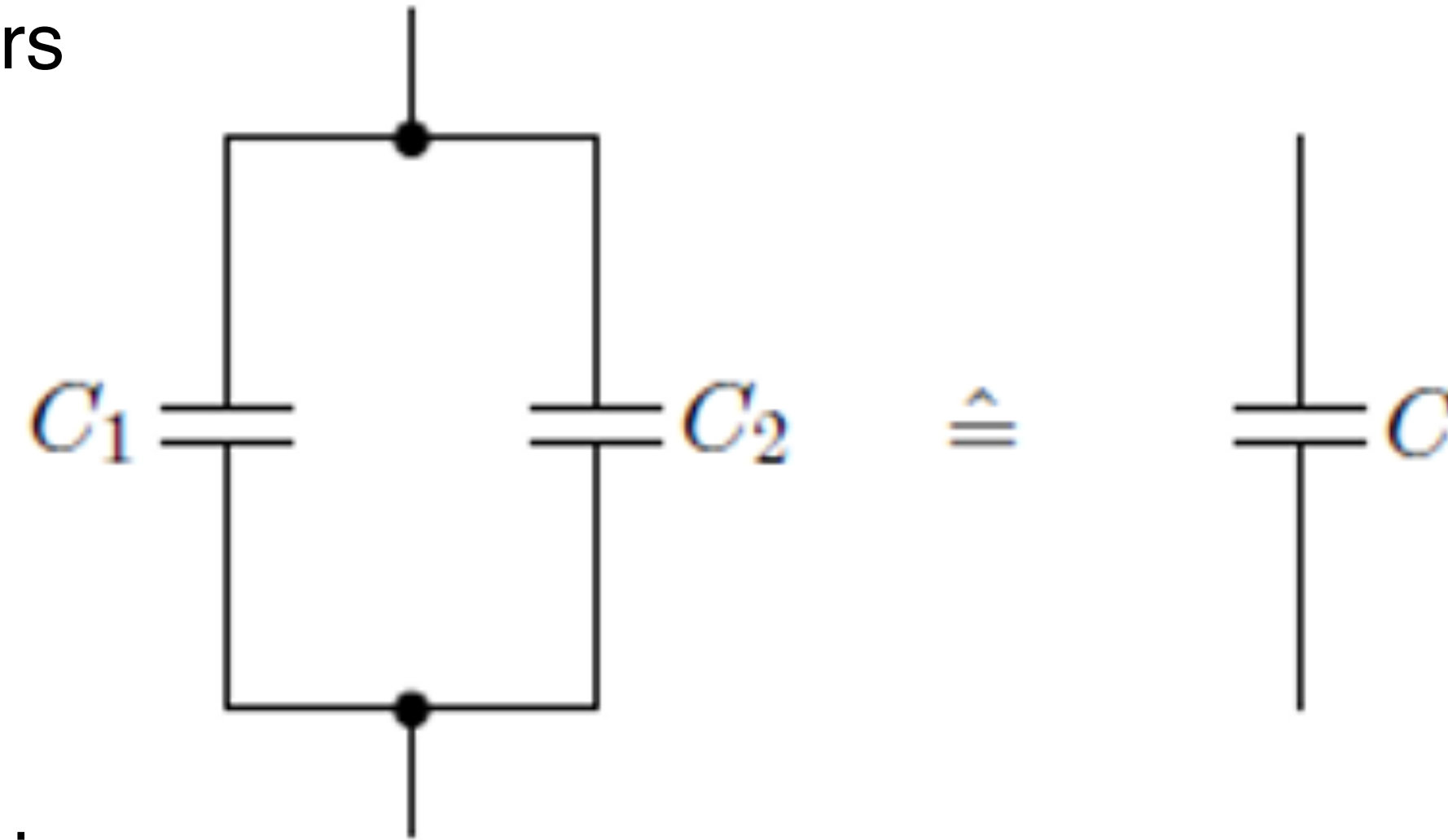

$$C = C_1 + C_2$$

- Capacitors in series

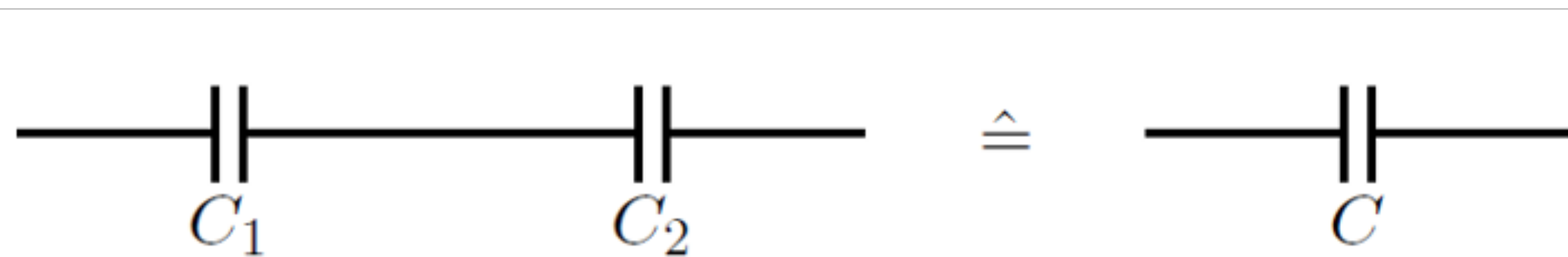

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C = \frac{C_1 C_2}{C_1 + C_2}$$


Overview: Circuits with passive Components

Resistor, Capacitor

	Series	Parallel
Resistor	$R = R_1 + R_2$ increases	$R = \frac{R_1 R_2}{R_1 + R_2}$ decreases
Capacitor	$C = \frac{C_1 C_2}{C_1 + C_2}$ decreases	$C = C_1 + C_2$ increases

Discharging a Capacitor

Entladen

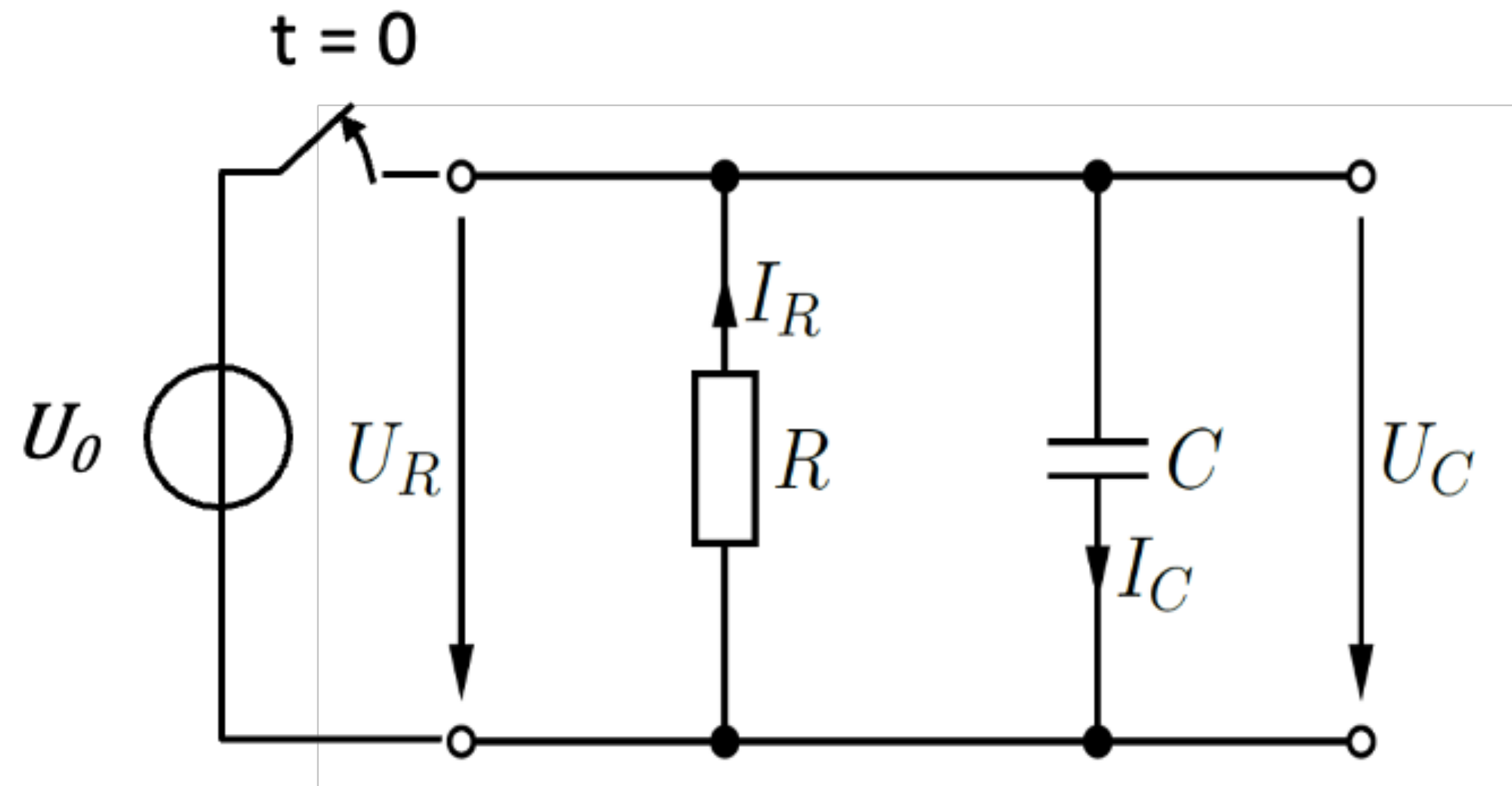

Solving the differential equation

$$U_C(t) = U_0 e^{-\frac{t}{RC}}$$


Exponential decrease with time constant

$$\tau = RC$$

For $t > 0$: Disconnecting the voltage source.
Discharging the capacitor via R , starting from $U_C = U_0$

Kirchhoff's Current Law:

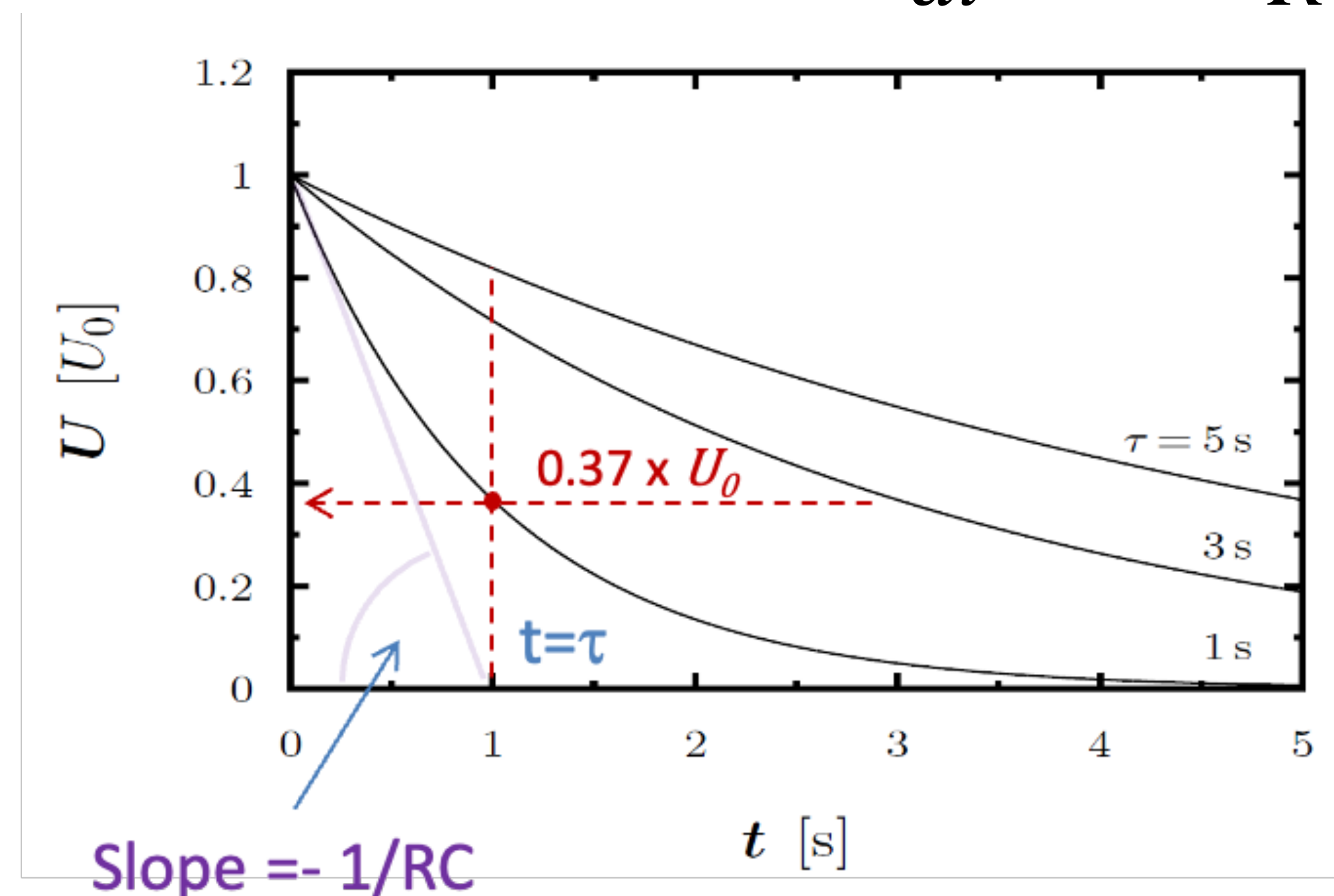
$$I_C = I_R \quad I_C = C \frac{dU_c}{dt} = - \frac{U_C}{R}$$



Charging a Capacitor

with a Voltage Source

- Charging via resistor

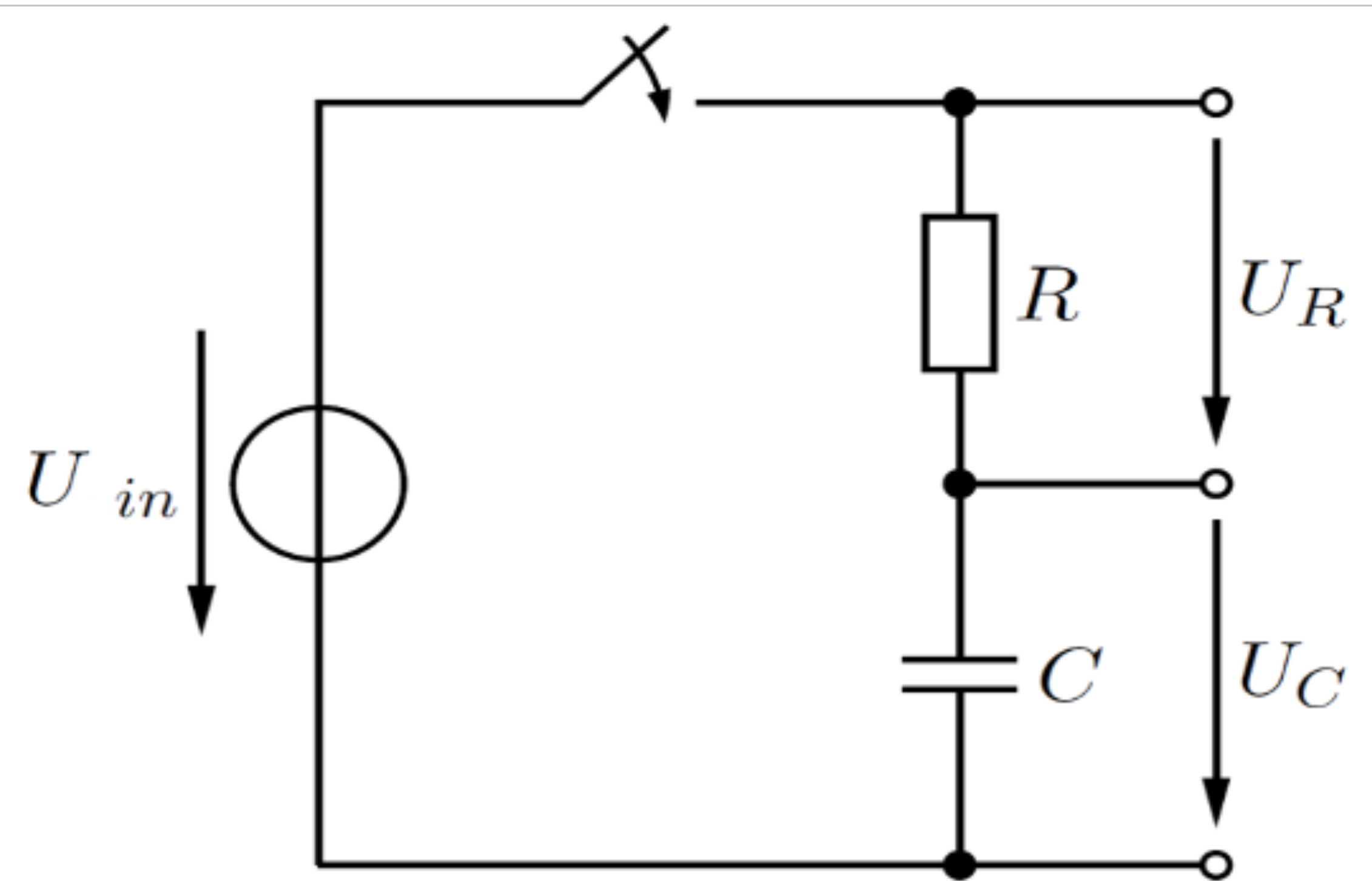

Large capacitor: longer charging time


Large resistor: longer charging time

Starting point ($t = 0$): $U_C = 0$

“charging current”: $I = U_R/R = (U_{in} - U_C)/R$

U_C depend on capacitor charge: $U_C = Q_C/C$, with that depending on the integral of the current I from $t=0$:


$$U_C = U_{in}(1 - e^{-\frac{t}{RC}})$$

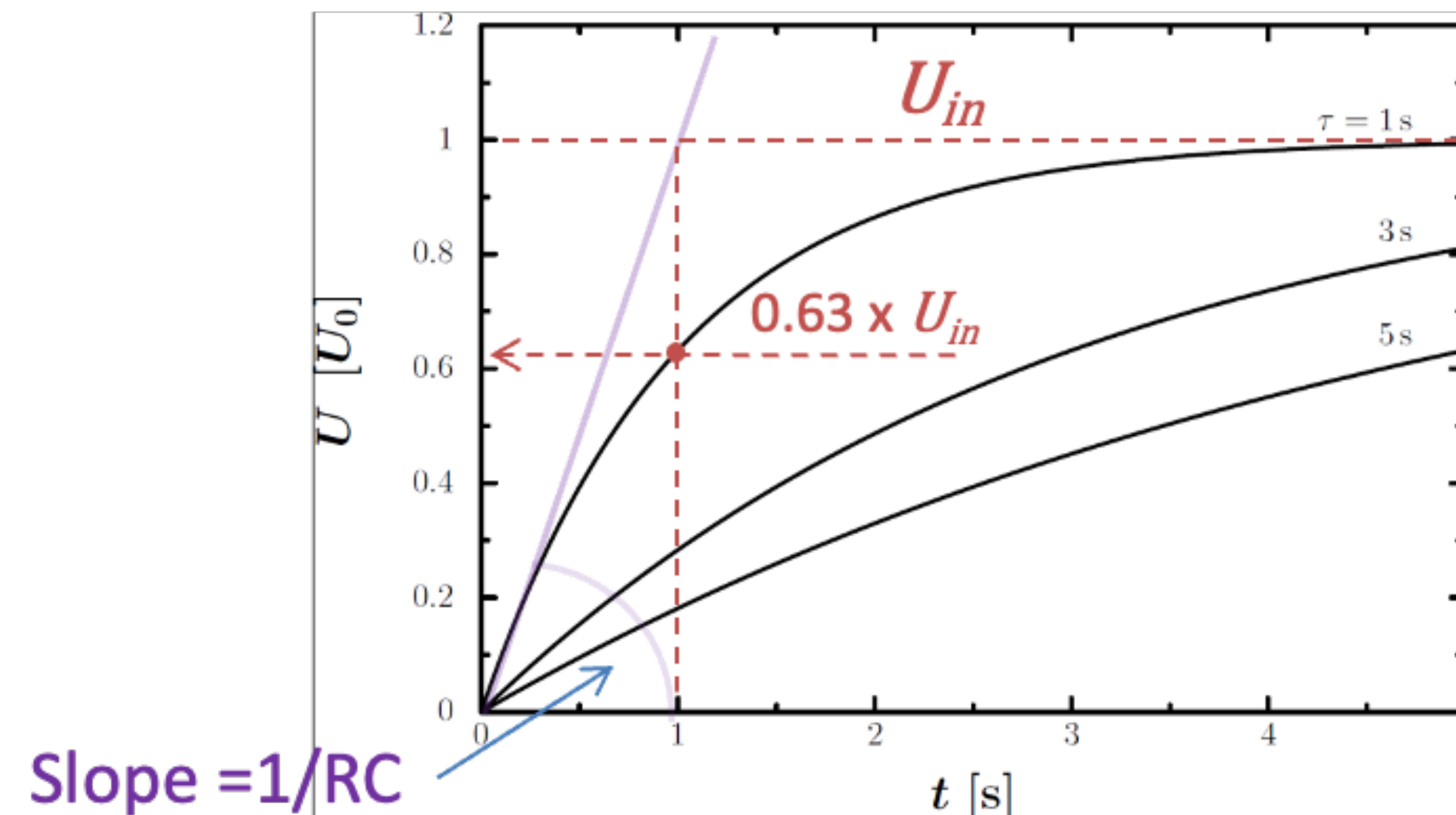

Charging a Capacitor


with a Current Source

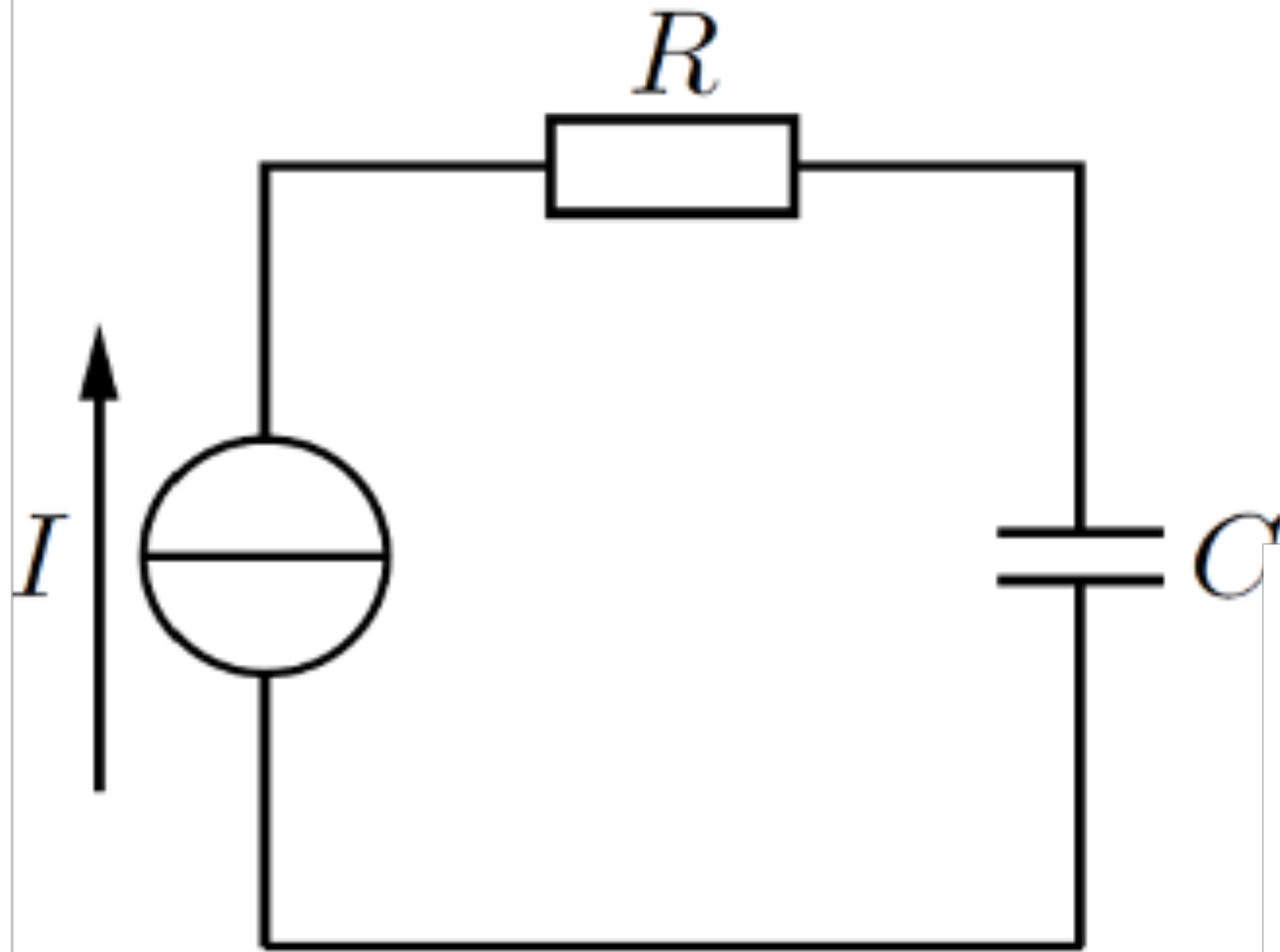- In contrast to the voltage source: charging current stays constant!



$$I = C \frac{dU_C}{dt} \Leftrightarrow U_C = \frac{1}{C} \int_0^T I dt = \frac{IT}{C}$$

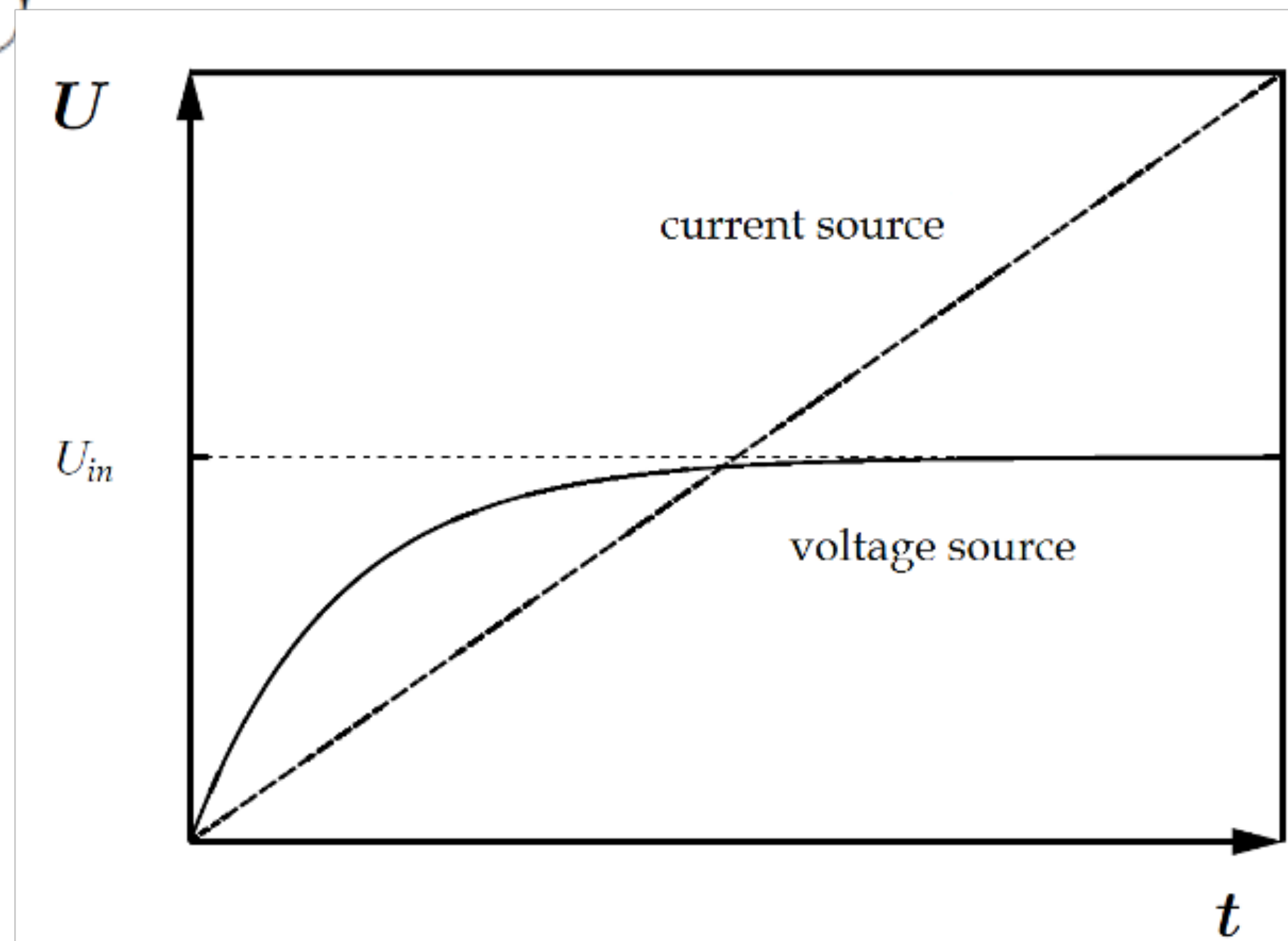Example: 1 s bei $C = 1 \mu\text{F}$ und $I = 1 \text{ mA}$ results in $U_C = 1 \text{ kV}$




Comparison of charging behavior with voltage and current source

Low Pass / Integrator

Tiefpass / Integrator

- Behavior for time-dependent voltages

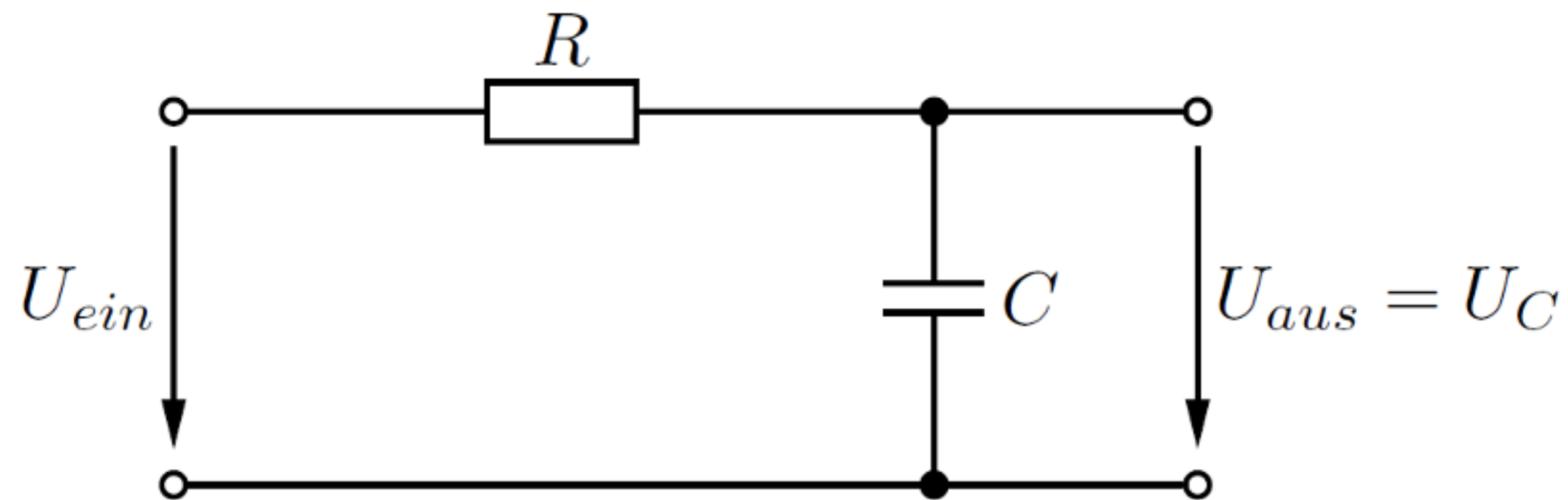

$$\frac{dU_C}{dt} + \frac{U_C}{RC} = \frac{U_{ein}}{RC}$$

First approximation: U_C is small

$$U_C = U_{aus} = \frac{1}{RC} \int U_{ein} dt$$

Integrator circuit!

Kirchhoff's Laws:


$$I_C = I_R$$

KCL

$$U_{ein} - U_C - U_R = 0$$


KVL
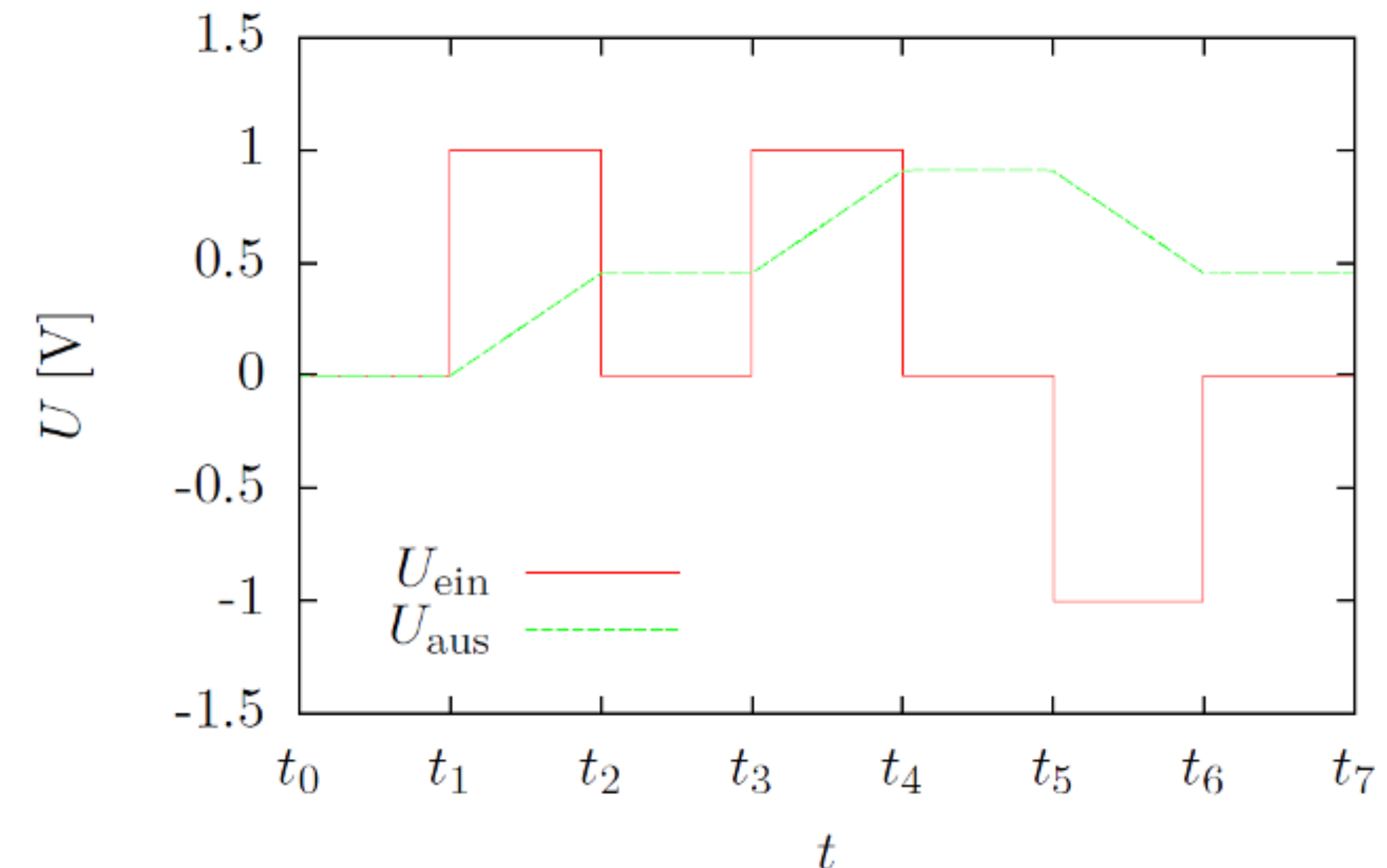
$$I_C = I_R \rightarrow C \frac{dU_C}{dt} = \frac{U_{ein} - U_C}{R}$$



High Pass / Differentiator

Hochpass / Differenzierer


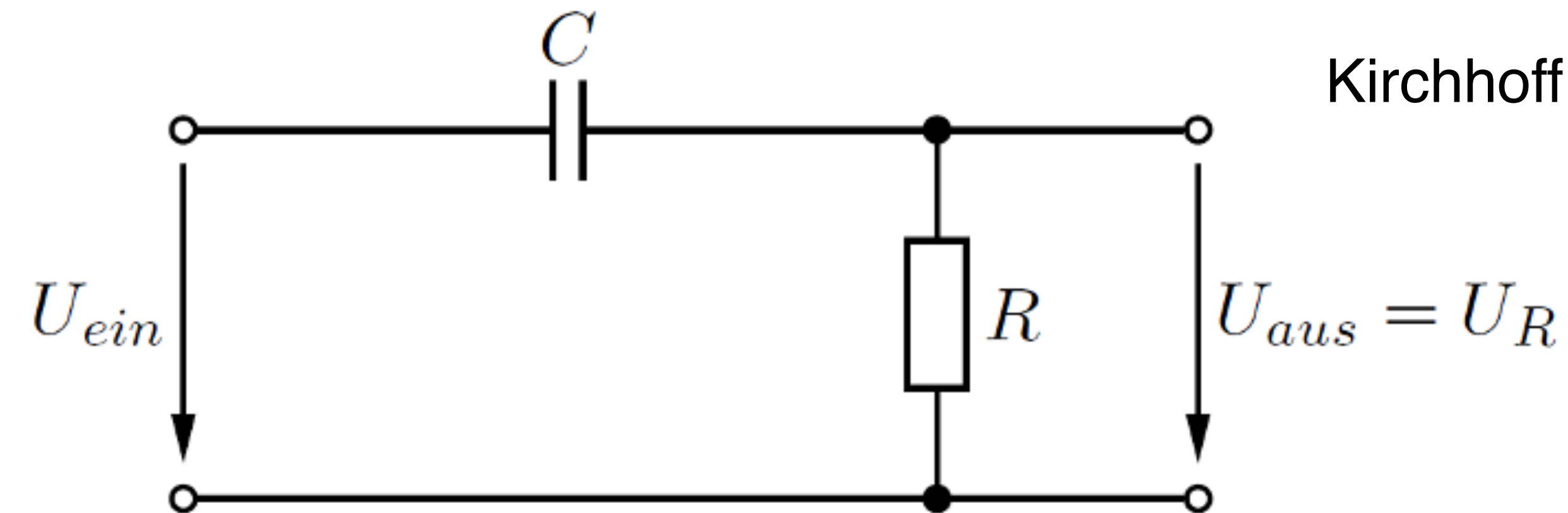


$$U_{ein} = U_C + RC \frac{dU_C}{dt}$$

$$U_{ein} - U_C = RC \frac{d(U_{ein} - U_{aus})}{dt} = U_{aus}$$


For small R: $U_{ein} - U_{aus} \sim U_{ein}$ (only small voltage drop)

$$U_{aus} = RC \frac{dU_{ein}}{dt}$$

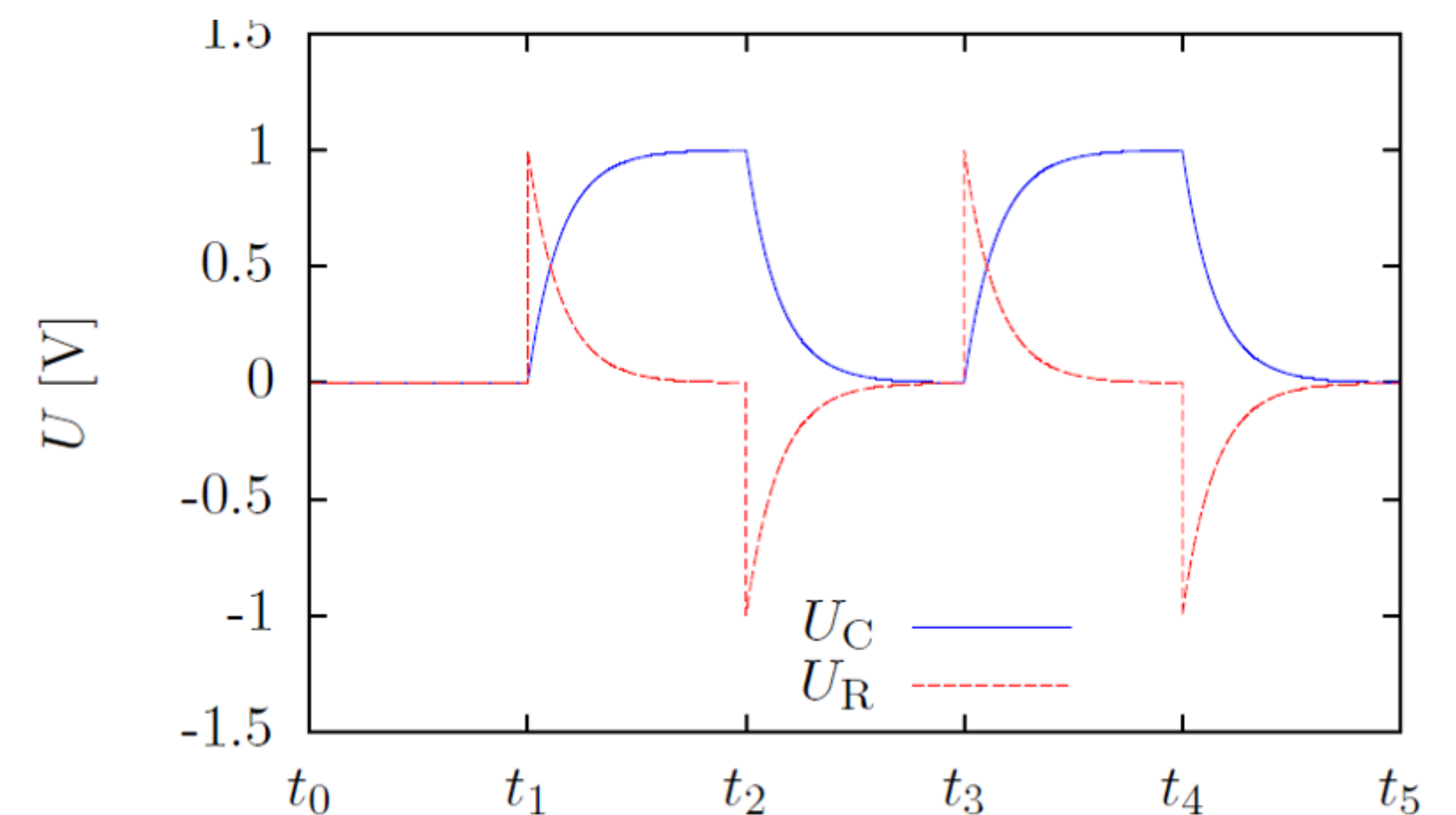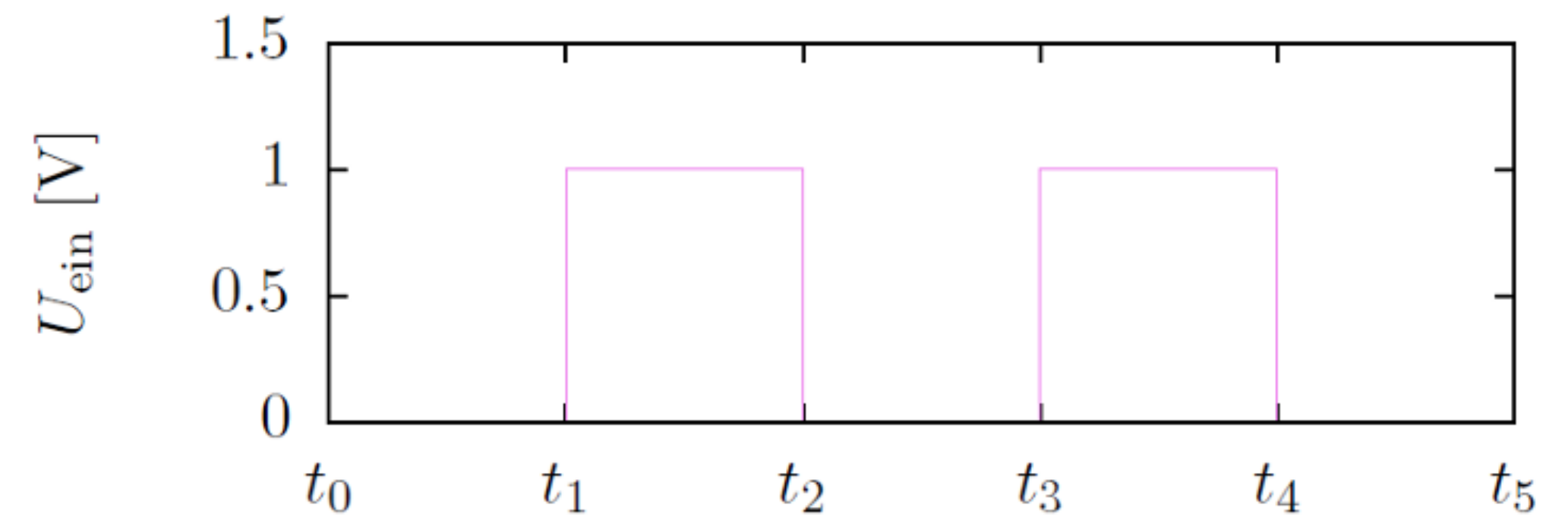

Next Lecture: Analog 03 - Chapter 01

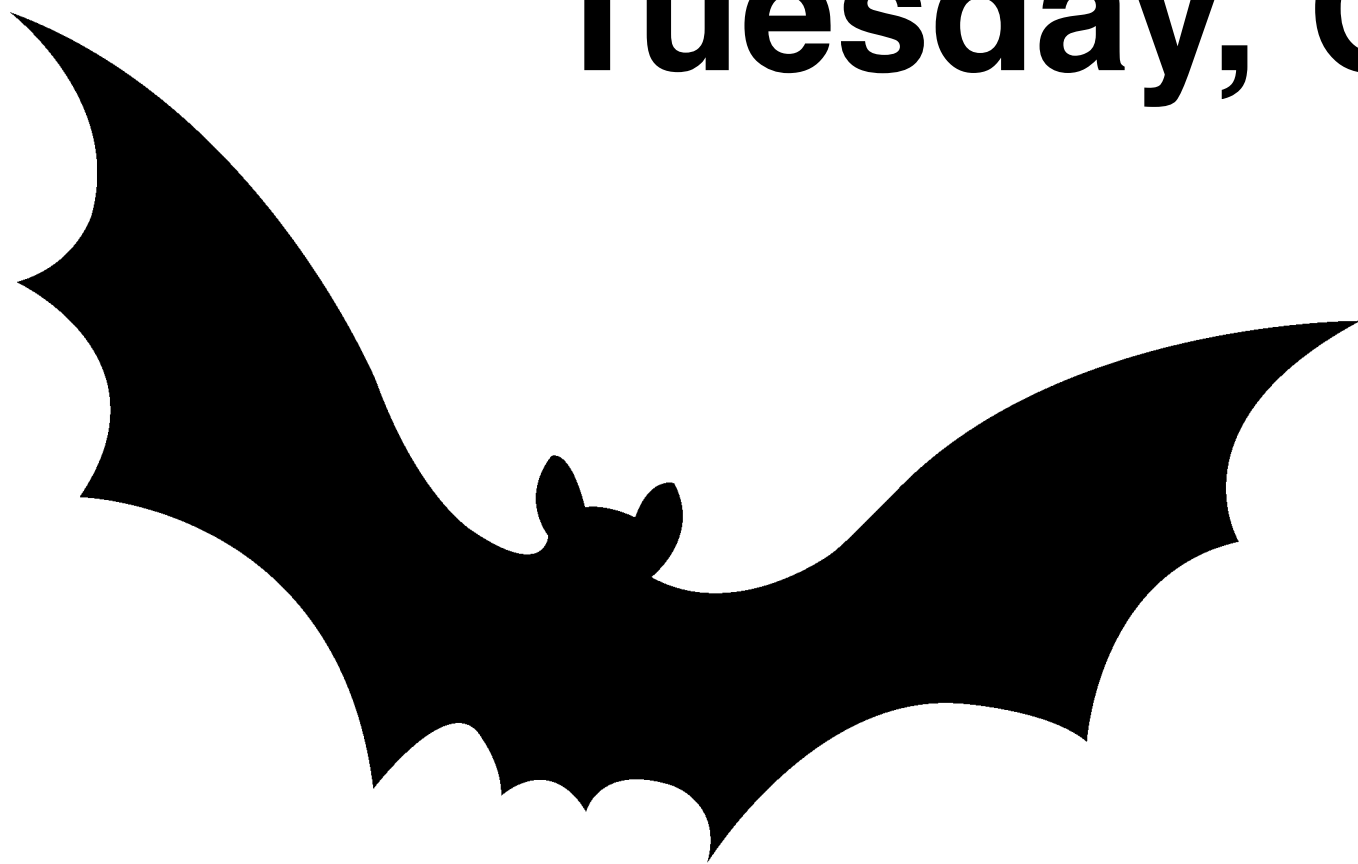Tuesday, October 31 - same time, same place.



Electronics for Physicists

Analog Electronics

Chapter 1; Lecture 02

Frank Simon

Institute for Data Processing and Electronics

26.10.2023

KIT, Winter 2023/24