

Electronics for Physicists

Analog Electronics

Chapter 1; Lecture 03

Frank Simon

Institute for Data Processing and Electronics

31.10.2023

KIT, Winter 2023/24

Chapter 1

Basics

Part 2

- Simple RC Filters
- Inductors
- RC and RL Circuits
- Linear Networks

Overview

1. Basics

2. Circuits with R, C, L with Alternating Current

3. Diodes

4. Operational Amplifiers

5. Transistors - Basics

6. 2-Transistor Circuits

7. Field Effect Transistors


8. Additional Topics

- Filters
- Voltage Regulators
- Noise

Low Pass / Integrator

Tiefpass / Integrator

- Behavior for time-dependent voltages

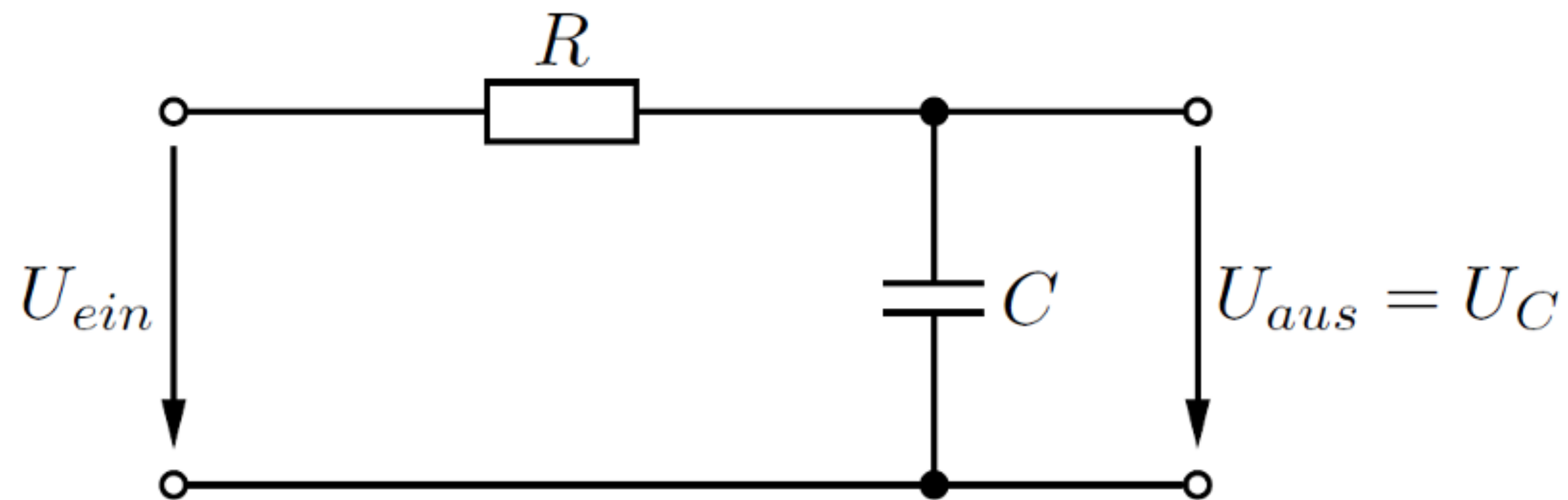

$$\frac{dU_C}{dt} + \frac{U_C}{RC} = \frac{U_{ein}}{RC}$$

First approximation: U_C is small

$$U_C = U_{aus} = \frac{1}{RC} \int U_{ein} dt$$

Integrator circuit!

Kirchhoff's Laws:


$$I_C = I_R$$

KCL

$$U_{ein} - U_C - U_R = 0$$


KVL
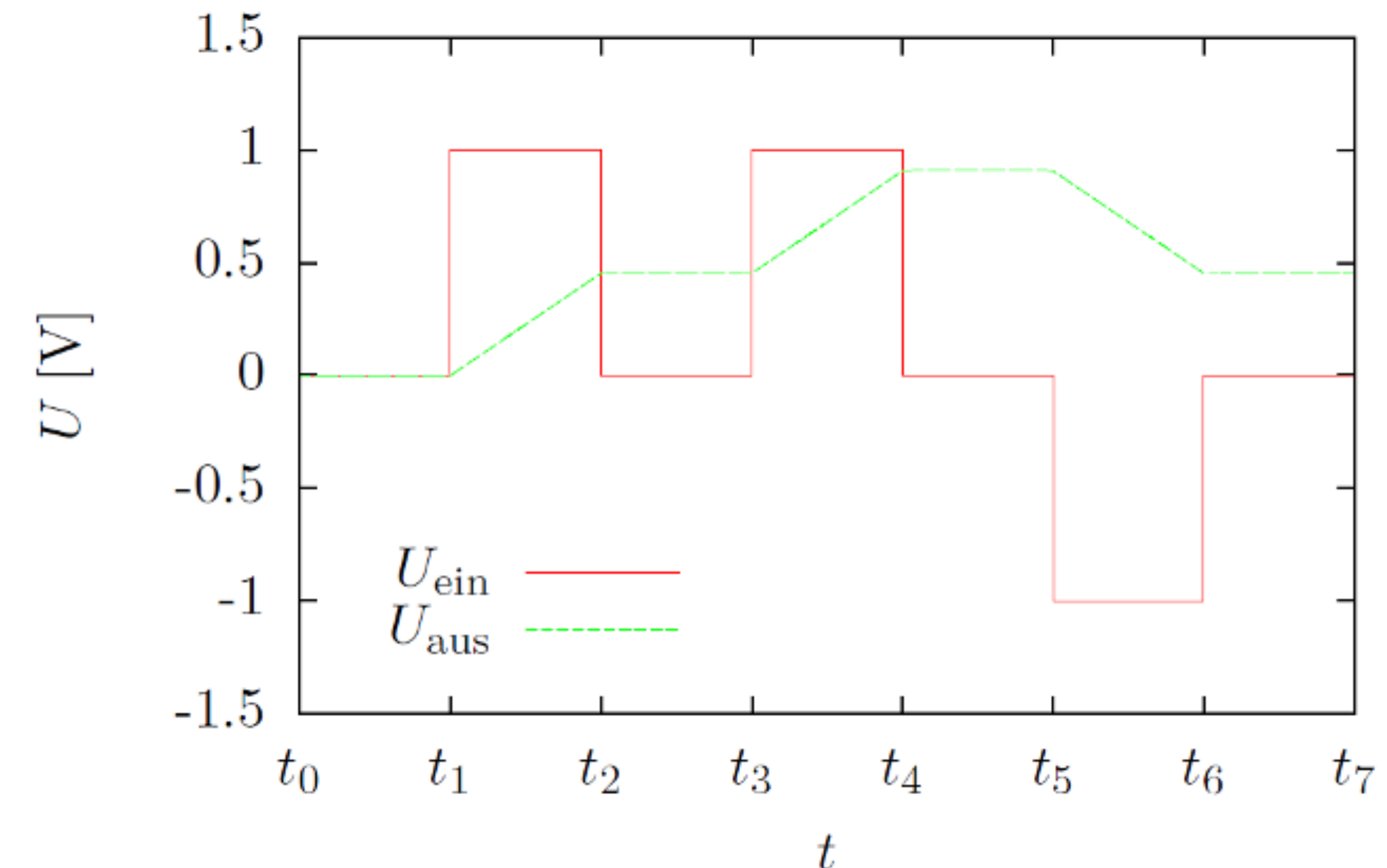
$$I_C = I_R \rightarrow C \frac{dU_C}{dt} = \frac{U_{ein} - U_C}{R}$$



High Pass / Differentiator

Hochpass / Differenzierer


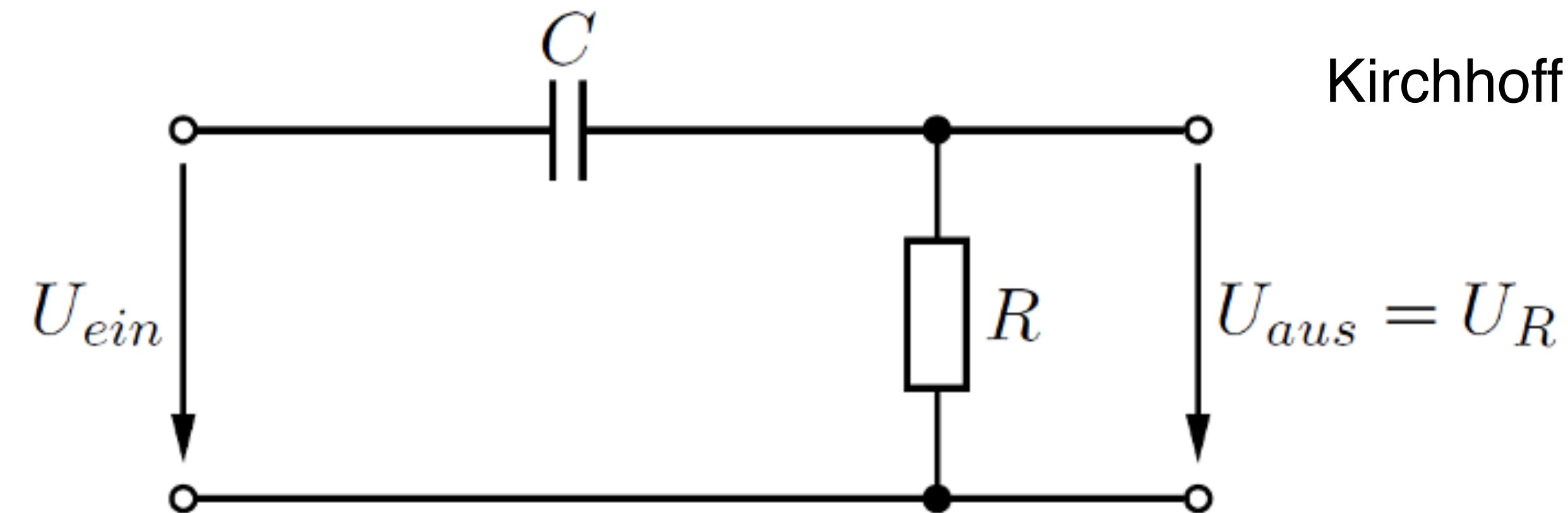


$$U_{ein} = U_C + RC \frac{dU_C}{dt}$$


$$U_{ein} - U_C = RC \frac{d(U_{ein} - U_{aus})}{dt} = U_{aus}$$

For small R: $U_{ein} - U_{aus} \sim U_{ein}$ (only small voltage drop)

$$U_{aus} = RC \frac{dU_{ein}}{dt}$$

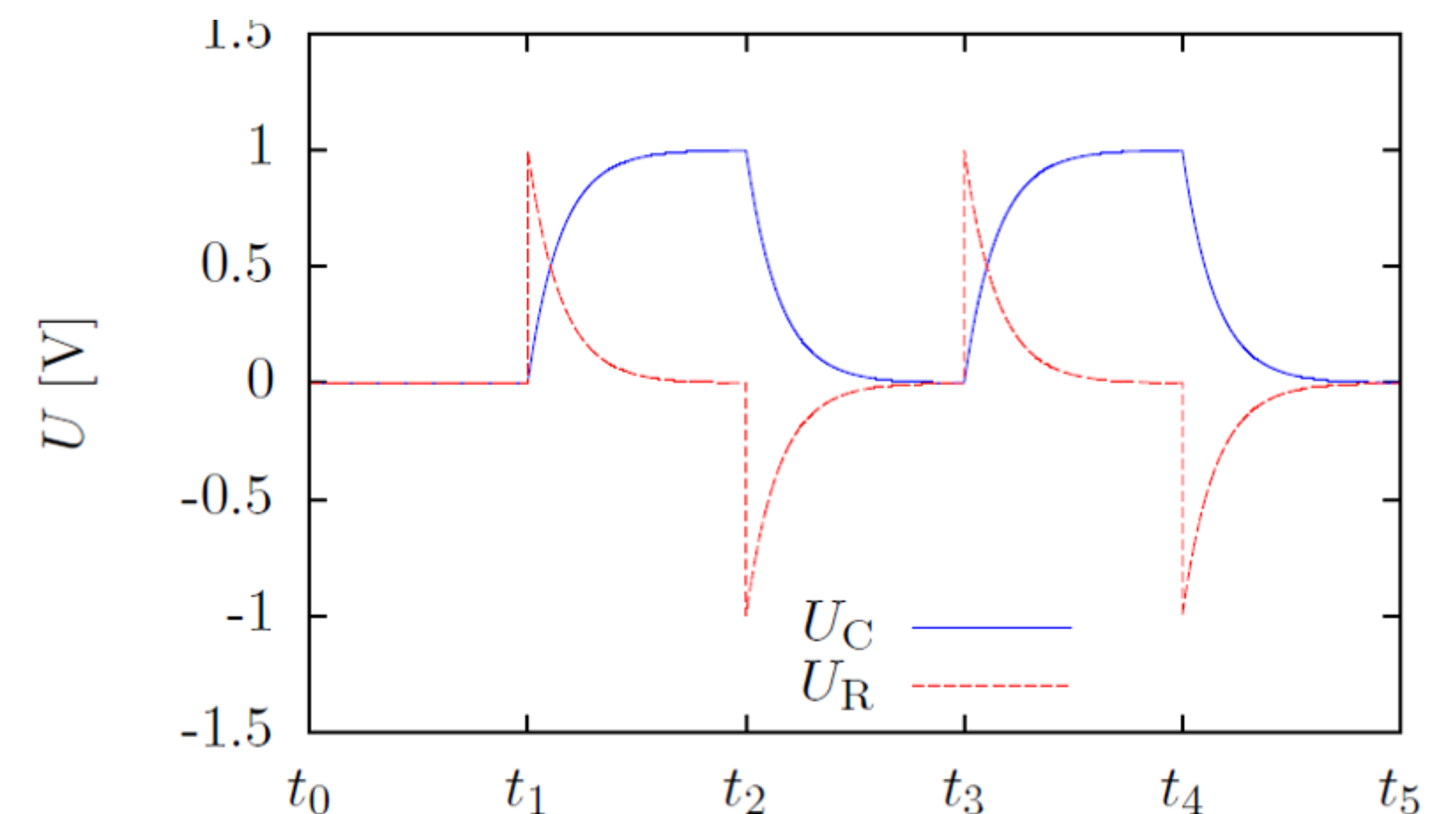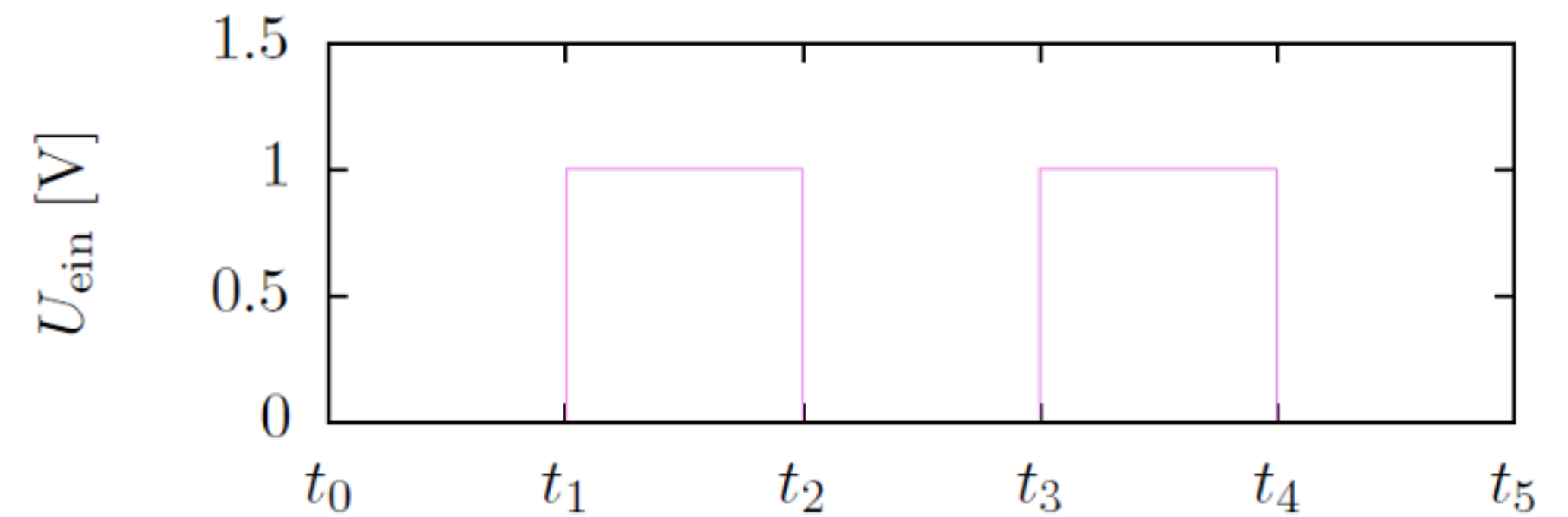

- Symbol:

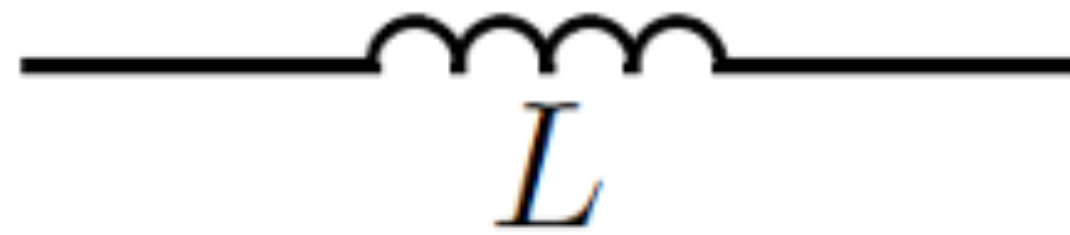


L: Inductance in Henry [H = Vs/A]

Induktivität

$$U = L \frac{dI}{dt}$$

$$E = \frac{1}{2} L I^2$$

“classic” inductor: Solenoid - “coil”

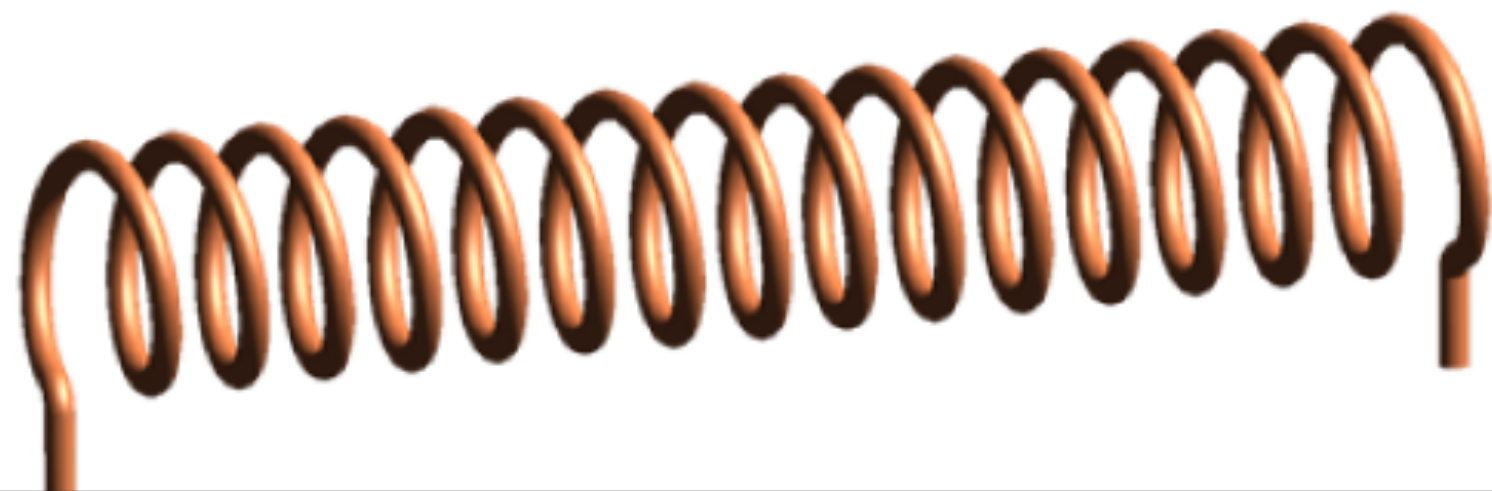

$$L \approx \mu_0 \mu_r N^2 \frac{A}{l} \frac{1}{1 + 0,45 \frac{D}{l}}$$

Inductivity of a coil with finite length

$$\mu_0 = 4 \pi 10^{-7} \left[\frac{\text{H}}{\text{m}} \right] = 12,566 \dots 10^{-7} \left[\frac{\text{H}}{\text{m}} \right]$$

N: Number of windings

A: cross section area of the coil [m²]

D: diameter [m]


l: length [m]

μ_r : permeability of the core (1 für Luft/Vakuum;

~ 2000+ for Fe, up to ~ 10⁵ for specialized alloys)

Magnetic Field of a Coil

Magnetfeld einer Spule

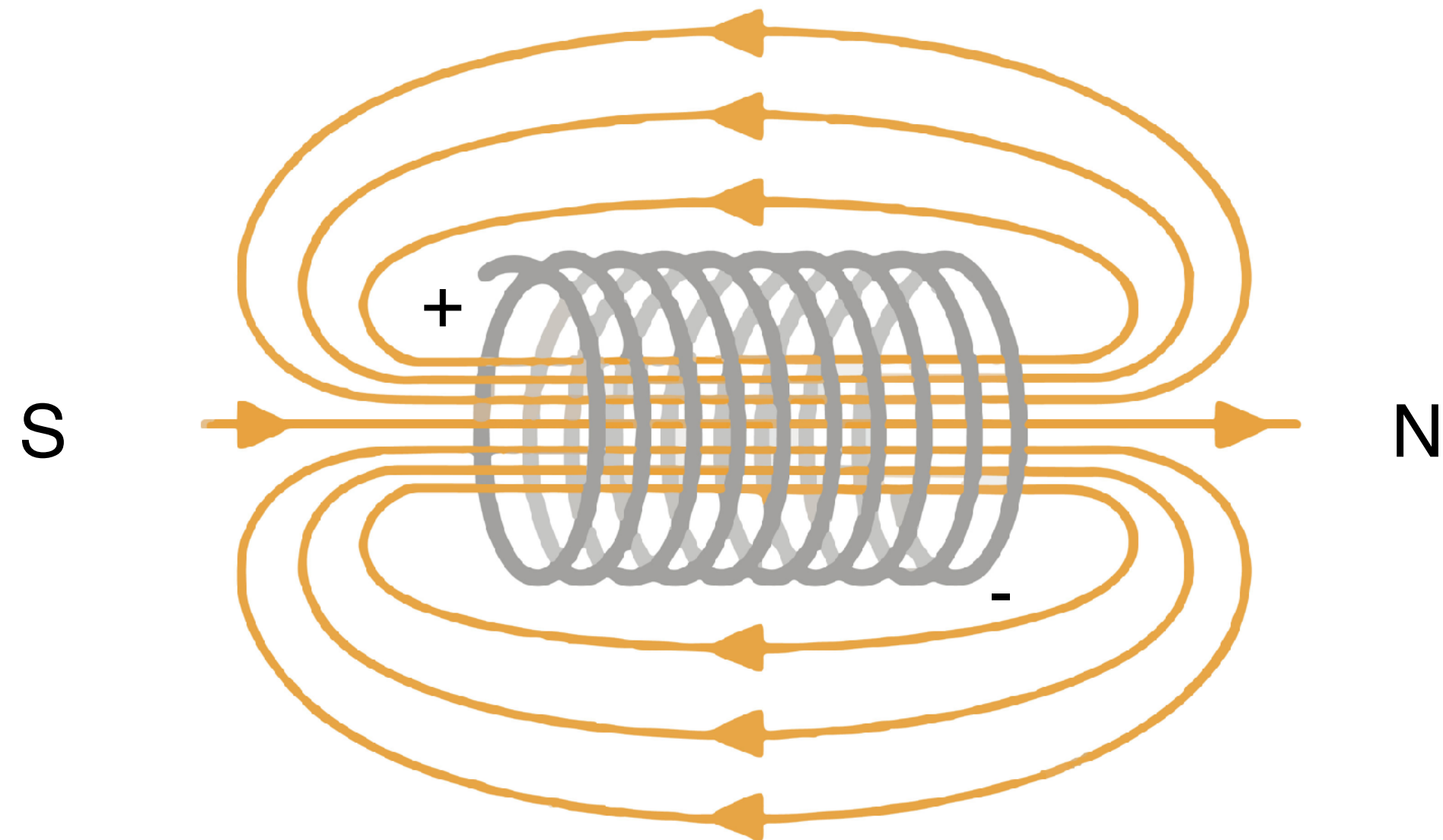

$$B = \mu_0 \frac{N}{l} I$$

B: Magnetic field [T]


N: Number of windings

l: Length of the coil

- For applications in electronics normally not relevant - but interesting, and helpful for in-depth understanding.

Very large Coils

An Example

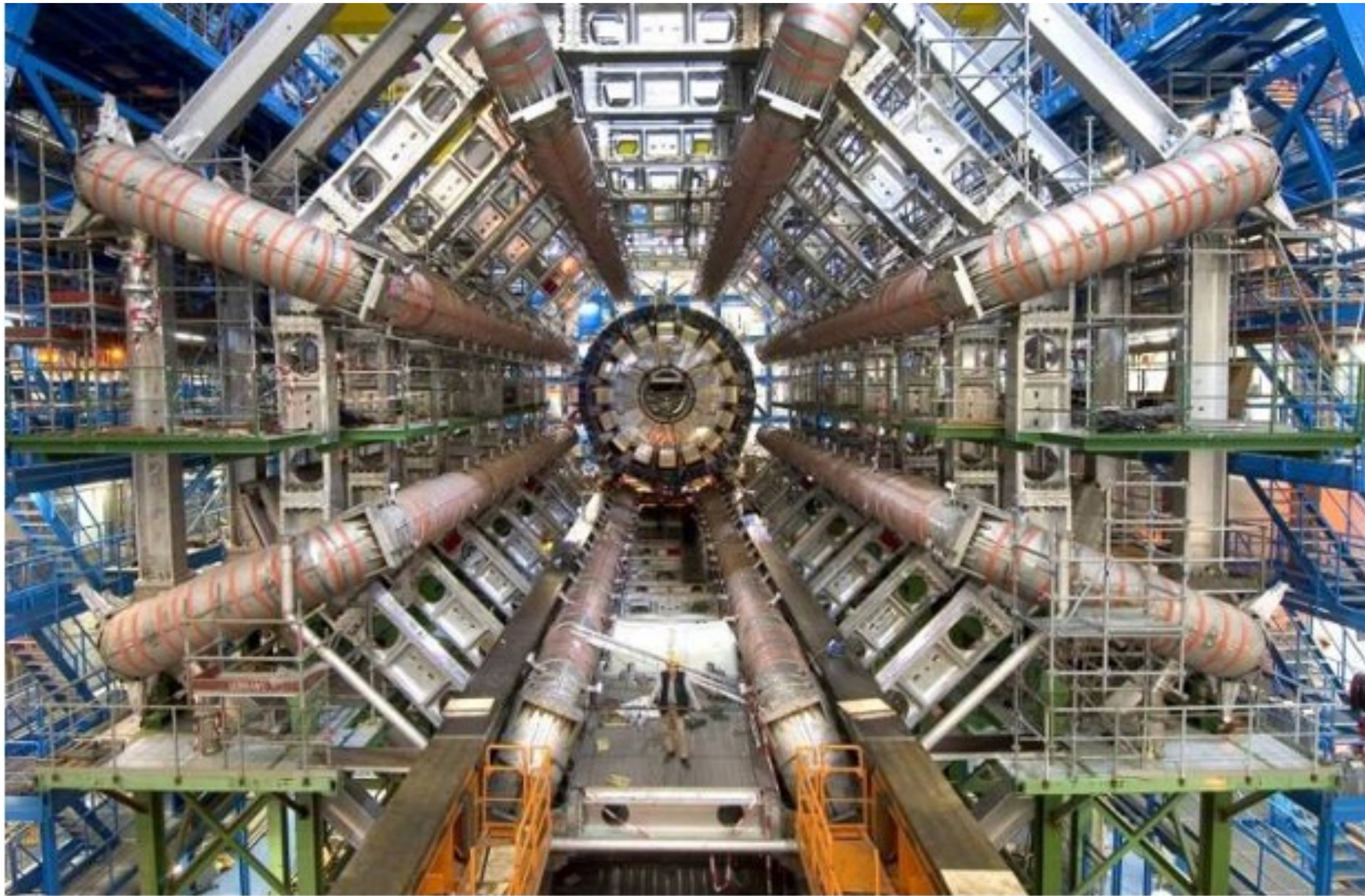


- ATLAS main magnet: Air core toroid

Overview: Behavior of passive Components

Resistor, Capacitor, Inductor

	Voltage	Current
Resistor	$U = RI$	$I = \frac{U}{R} = GU$
Capacitor	$U = \frac{1}{C} \int Idt$	$I = C \frac{dU}{dt}$
Inductor	$U = L \frac{dI}{dt}$	$I = \frac{1}{L} \int Udt$


- Inductors in series

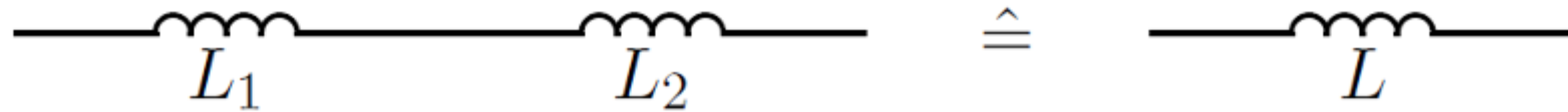

$$L = L_1 + L_2$$

Same current through all inductors: $I_{L1} = I_{L2}$

- Inductors in parallel

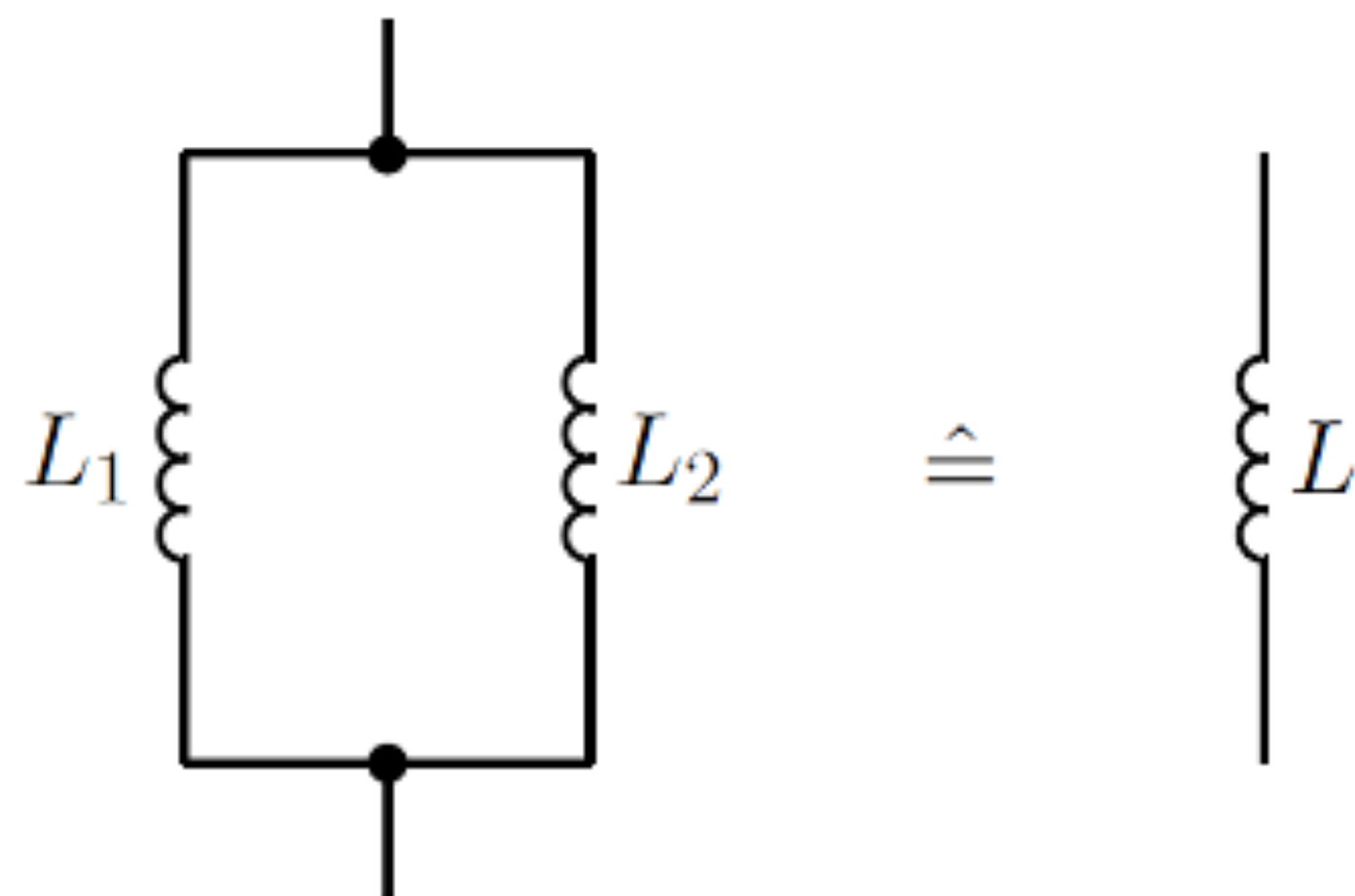

The same voltage across all inductors

$$U_{L1} = U_{L2}$$

(but the current is split over all)

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$L = \frac{L_1 L_2}{L_1 + L_2}$$

Overview: Circuits with passive Components

Resistor, Capacitor, Inductor

	Series	Parallel
Resistor	$R = R_1 + R_2$ increases	$R = \frac{R_1 R_2}{R_1 + R_2}$ decreases
Capacitor	$C = \frac{C_1 C_2}{C_1 + C_2}$ decreases	$C = C_1 + C_2$ increases
Inductor	$L = L_1 + L_2$ increases	$L = \frac{L_1 L_2}{L_1 + L_2}$ decreases

Inductance

Examples & Orders of Magnitude



- Depending on the application a very wide spectrum of numerical values - in general: H (Henry) is a “large” unit

Example 1: The CMS Solenoid

- $B = 3.8 \text{ T}$ as standard, design for 4 T
- Stored energy: 2.3 GJ (at 3.8 T)
- Current: 18.2 kA (at 3.8 T)
- Inductance L : 14 H
- Length: 13 m ; Diameter 6 m

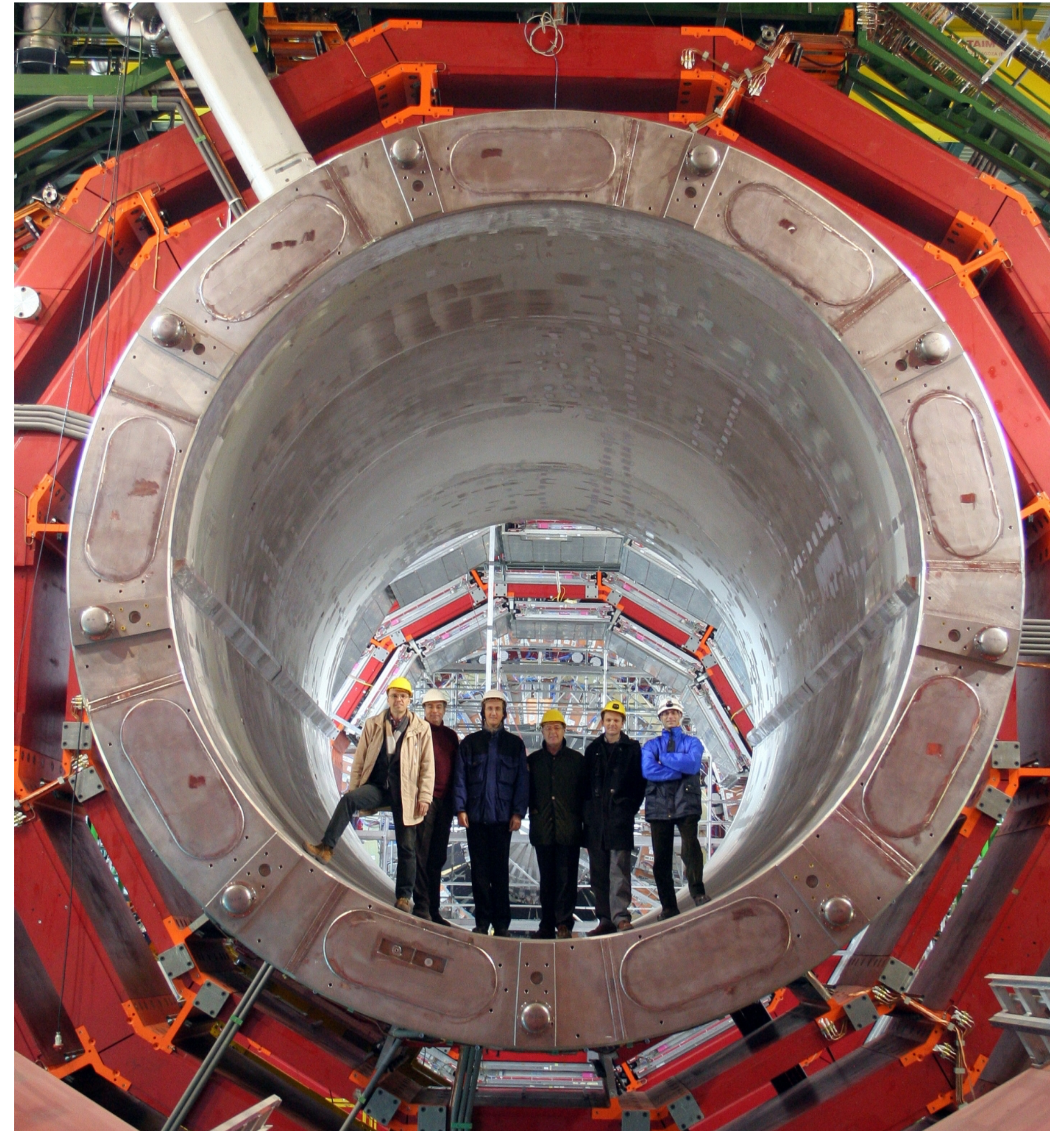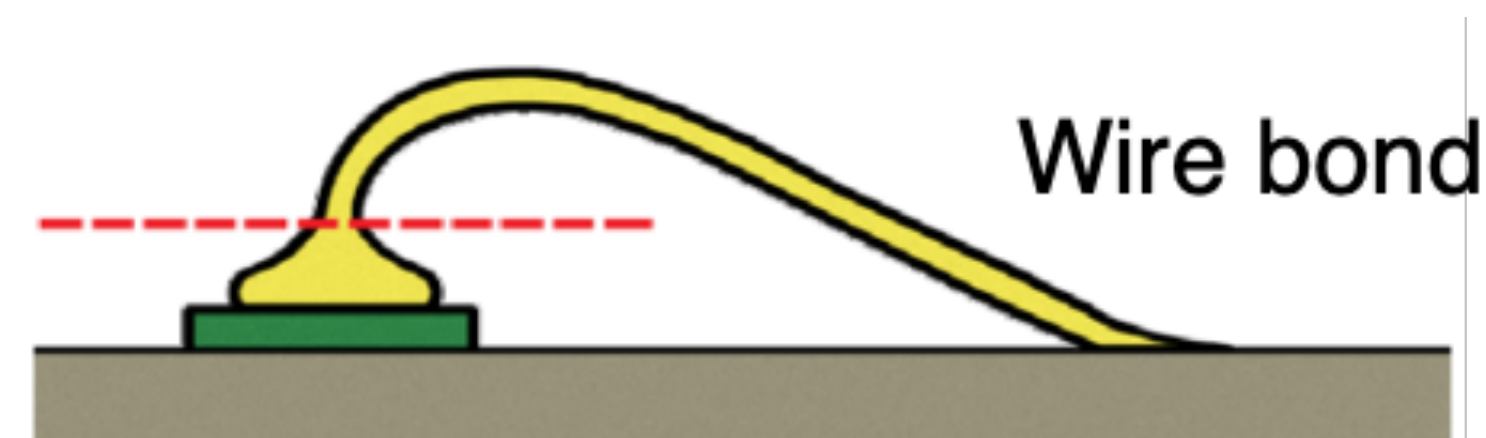Example 2: A single wire bond


- Length: a few mm
- Inductance L : a few nH



Discharging an Inductor

Entladen

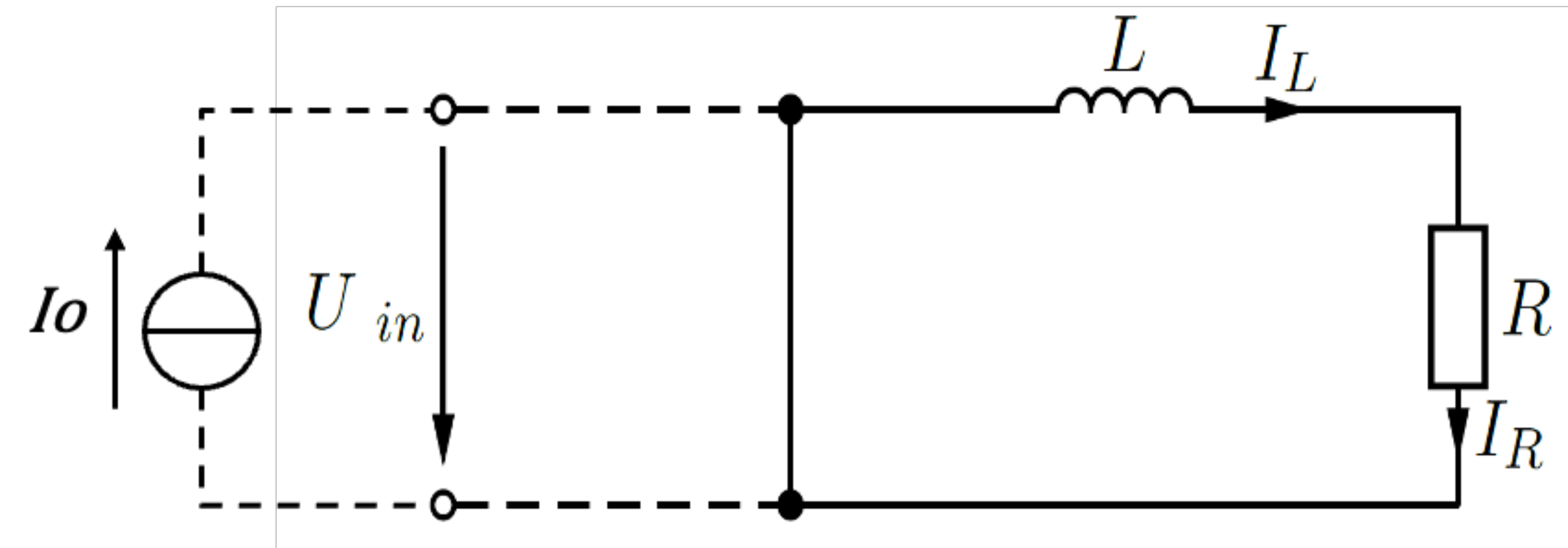- Discharging of an inductor through a resistor



Initial conditions at $t=0$: $I_L = I_0$

Solving the differential equation

$$I = I_0 e^{-\frac{t}{L/R}} = I_0 e^{-\frac{t}{\tau}} \quad \tau = \frac{L}{R}$$

for $t > 0$: Exponential decay of the current

$$\Rightarrow U_L = L \frac{dI}{dt} = -R I_0 e^{-\frac{t}{\tau}}$$


Comparing to a capacitor:

Exponential decay of the voltage

Magnetizing an Inductor

Magnetisieren

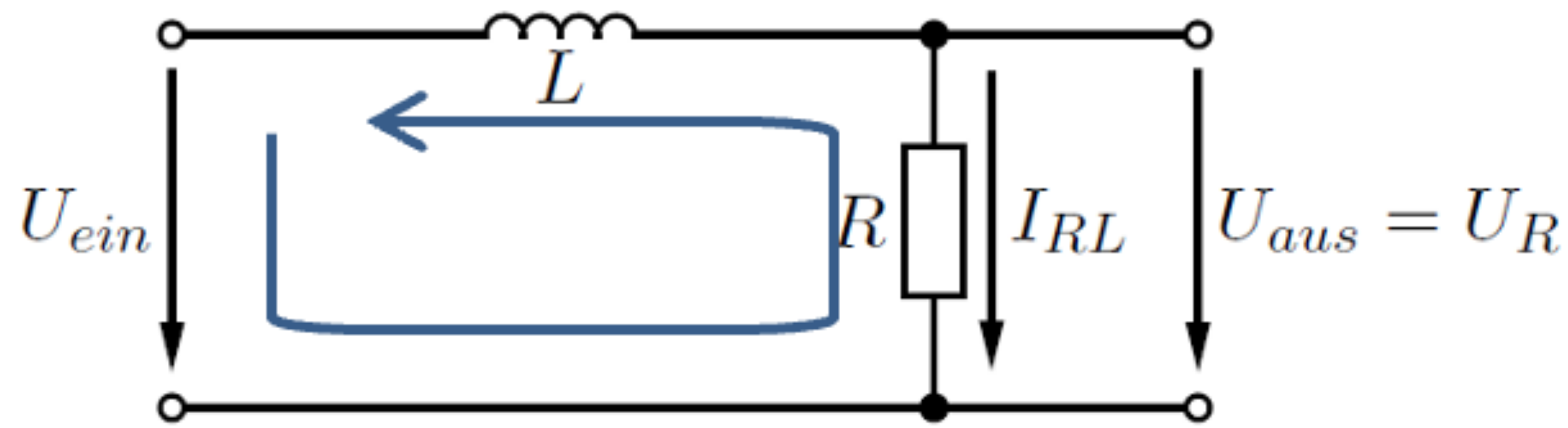- An electric circuit with a voltage source, inductor and resistor



$$\Rightarrow \frac{dI_{RL}}{dt} + \frac{R}{L} I_{RL} = \frac{U_{ein}}{L} \quad \Rightarrow \quad I_{RL} = \frac{U_{ein}}{R} (1 - e^{-\frac{Rt}{L}})$$

$$\tau = \frac{L}{R}, \quad U_R = U_{in} \left(1 - e^{-\frac{t}{\tau}}\right), \quad U_L = U_{in} e^{-\frac{t}{\tau}}$$

For $t = 0$: A non-magnetized inductor behaves like an “open” circuit


For $t = \infty$: A magnetized inductor behaves like a short circuit

Kirchhoff:

$$I_L = I_{RL}$$

$$U_{ein} - U_L - U_R = 0$$


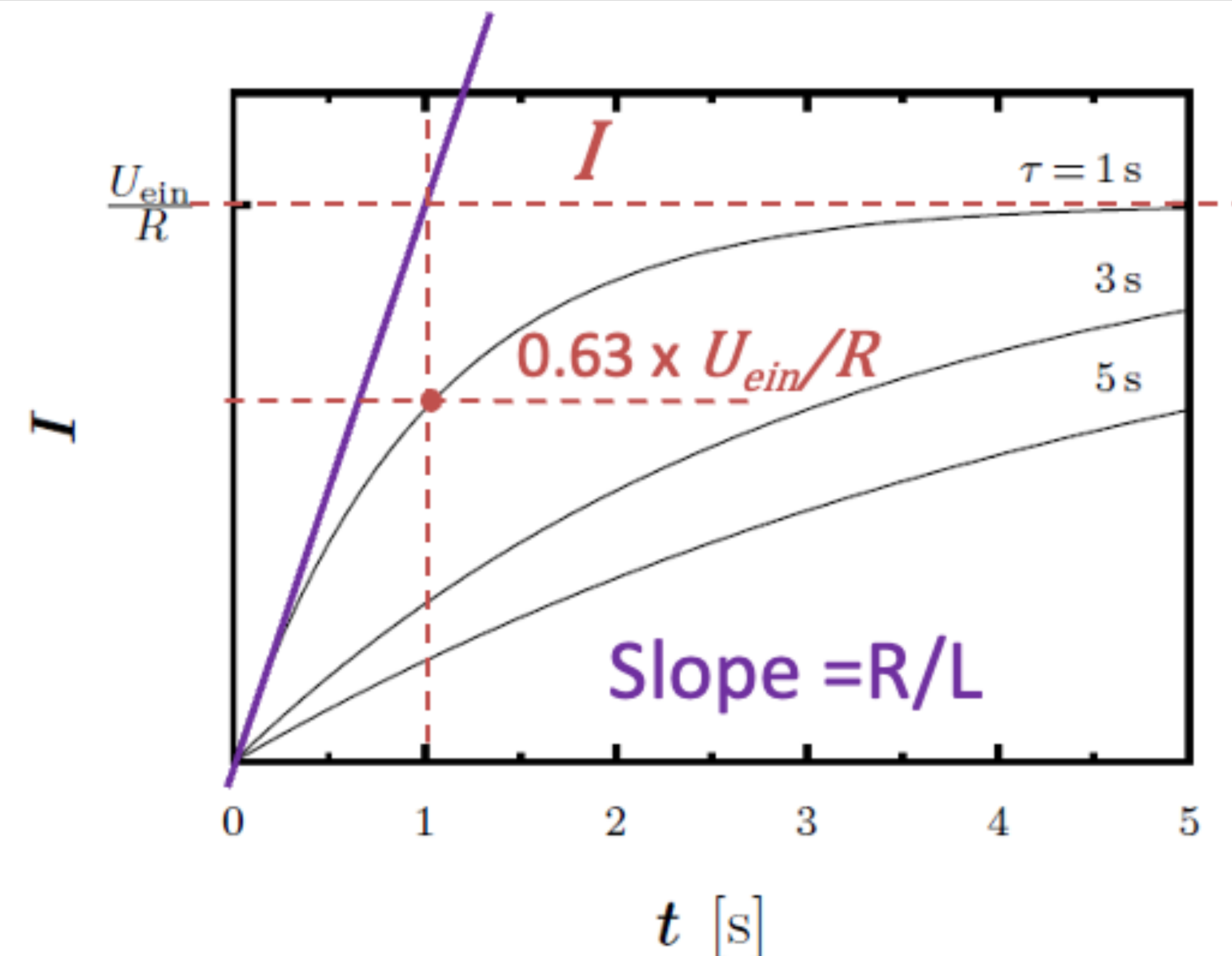
$$\Rightarrow U_{ein} = L \frac{dI}{dt} + RI$$



Time-Dependent Voltage

Behavior for a sequence of rectangular pulses

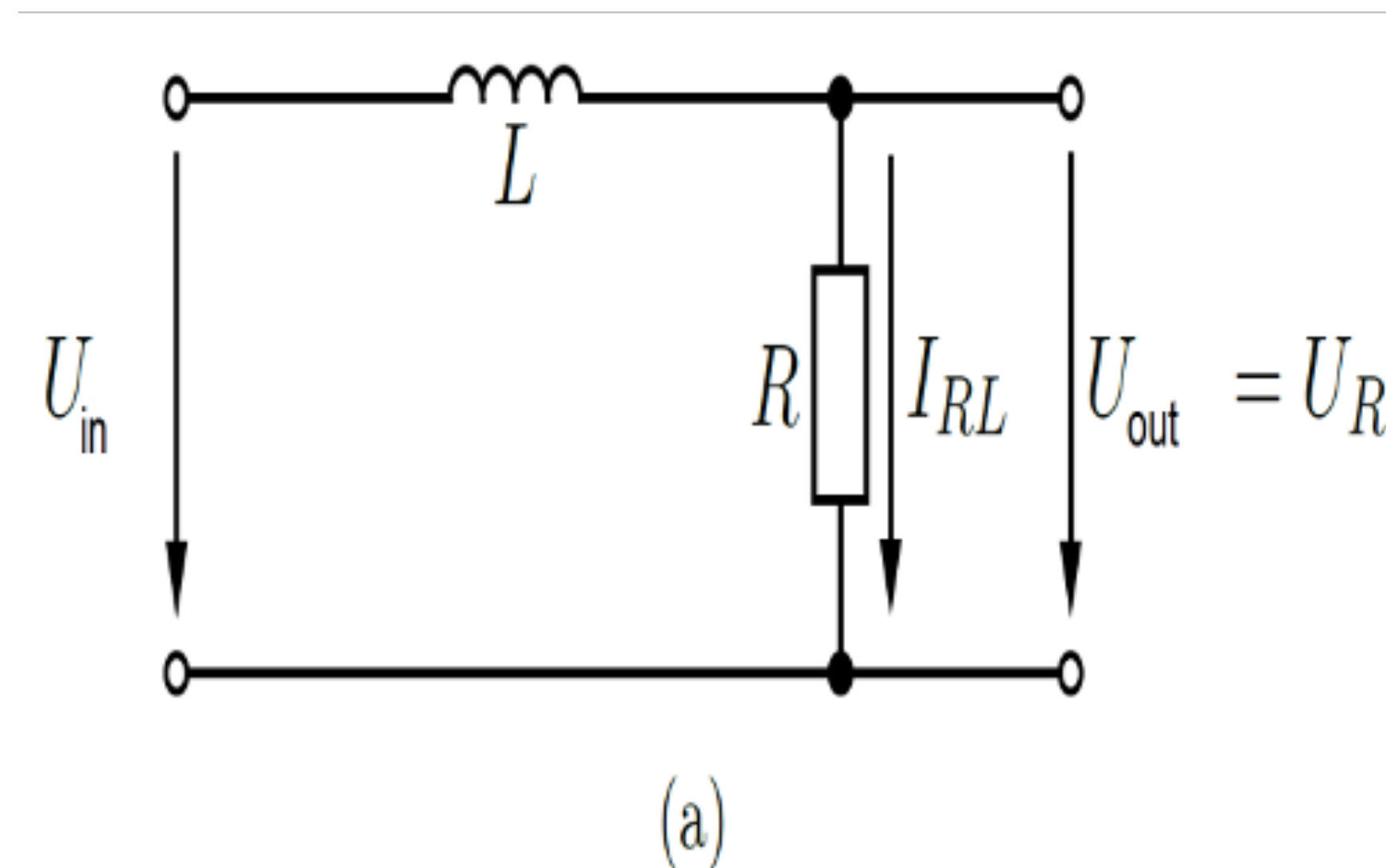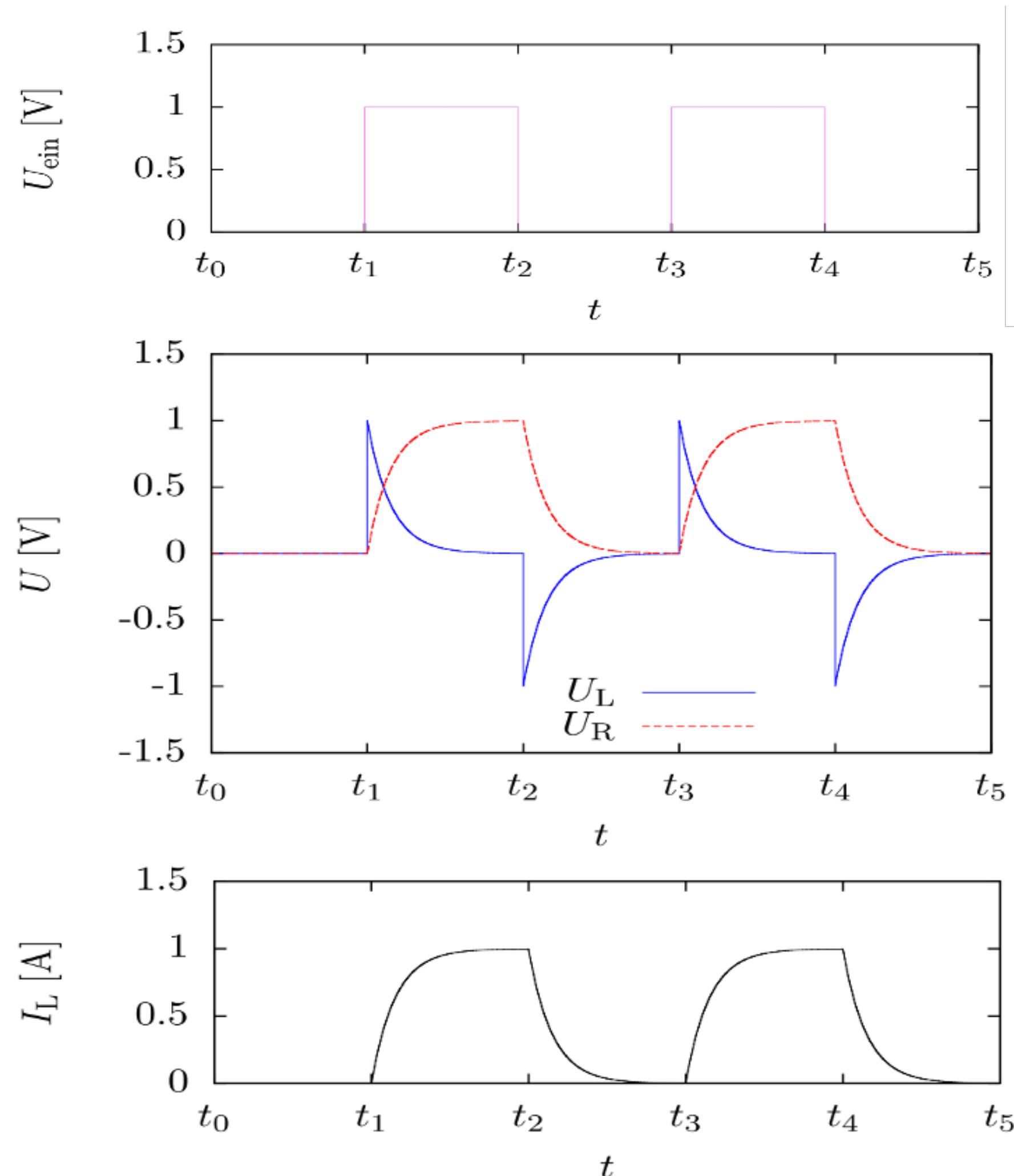- Comparable to the behavior of a capacitor (but with swapped integration / differentiation)



RL low pass: integrator

To discuss: Can a high pass be constructed as well?


Overview: Time behavior of passive Components

Resistor, Capacitor, Inductor

	Stored Energy	$t = 0$ (when switching on)	$t \rightarrow \infty$ (in equilibrium)
Resistor	-	time independent	
Capacitor	electric charge Q : -> voltage	$Q = 0; U = 0$: -> short circuit $Q \neq 0; U \neq 0$: -> voltage source	Q konstant $dQ/dt = I = 0$: -> open circuit
Inductor	magnetic field B : -> current	$B = 0; I = 0$: -> open circuit $B \neq 0; I \neq 0$: -> current source	B konstant $dI/dt = U = 0$: -> short circuit


RC and RL Circuits

A Comparison

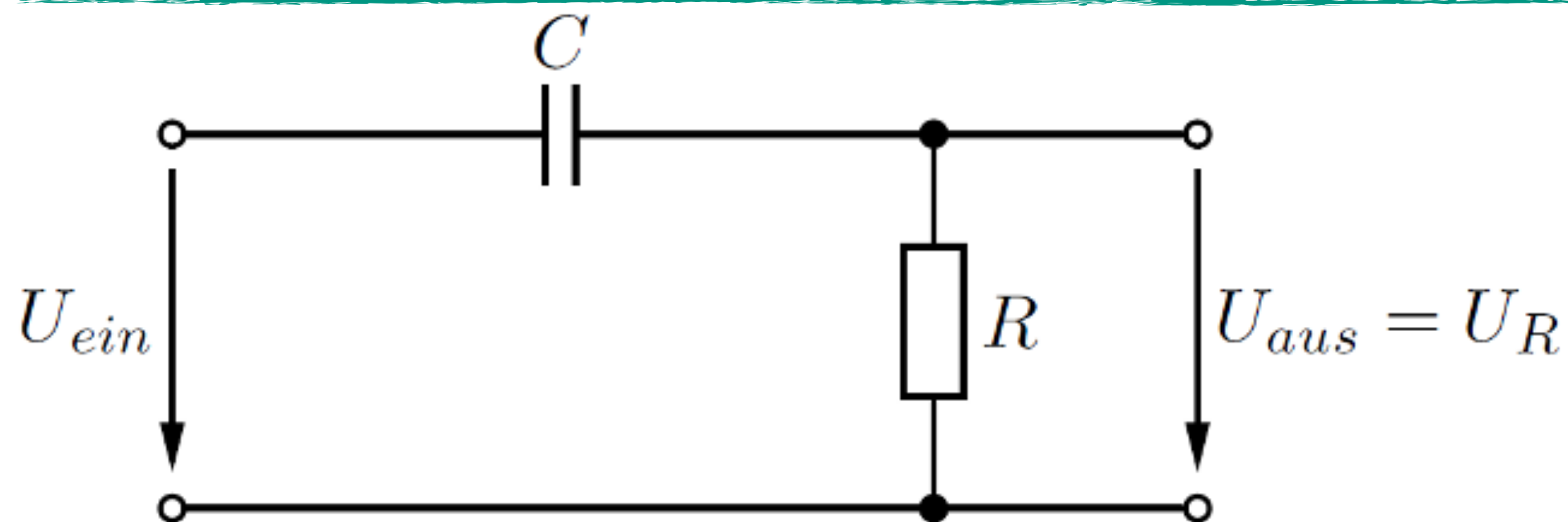

$t = 0 \rightarrow$ A capacitor behaves like a short circuit

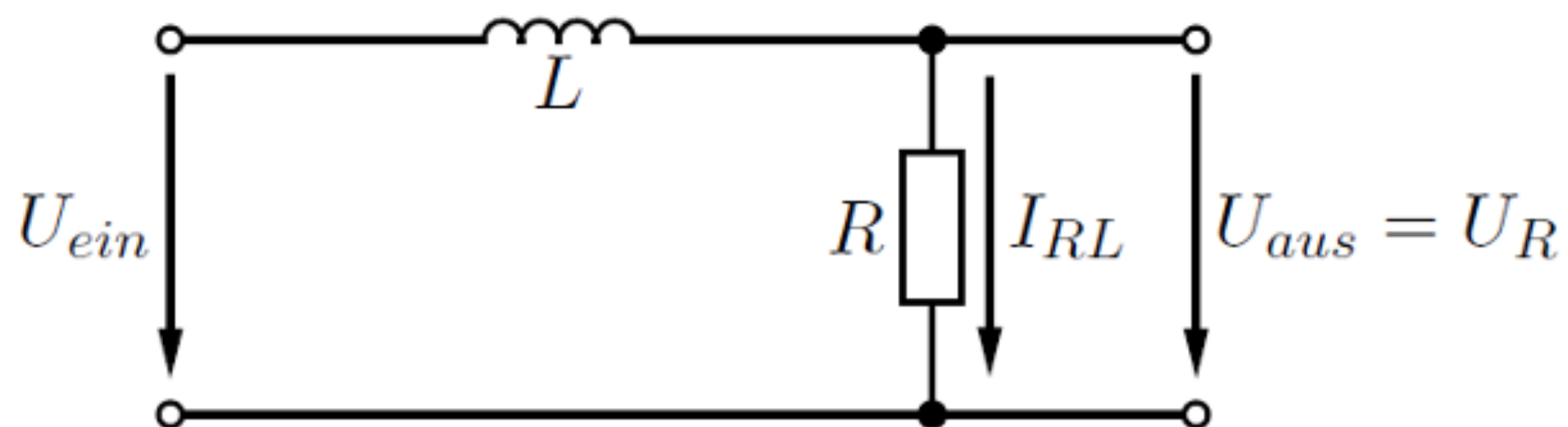$t = \infty \rightarrow$ Capacitor as open circuit




$t = 0 \rightarrow$ An inductor behaves like an open circuit

$t = \infty \rightarrow$ An inductor behaves like a short circuit


$$I_R = \frac{U_{ein}}{R}$$

$$I_R = 0$$

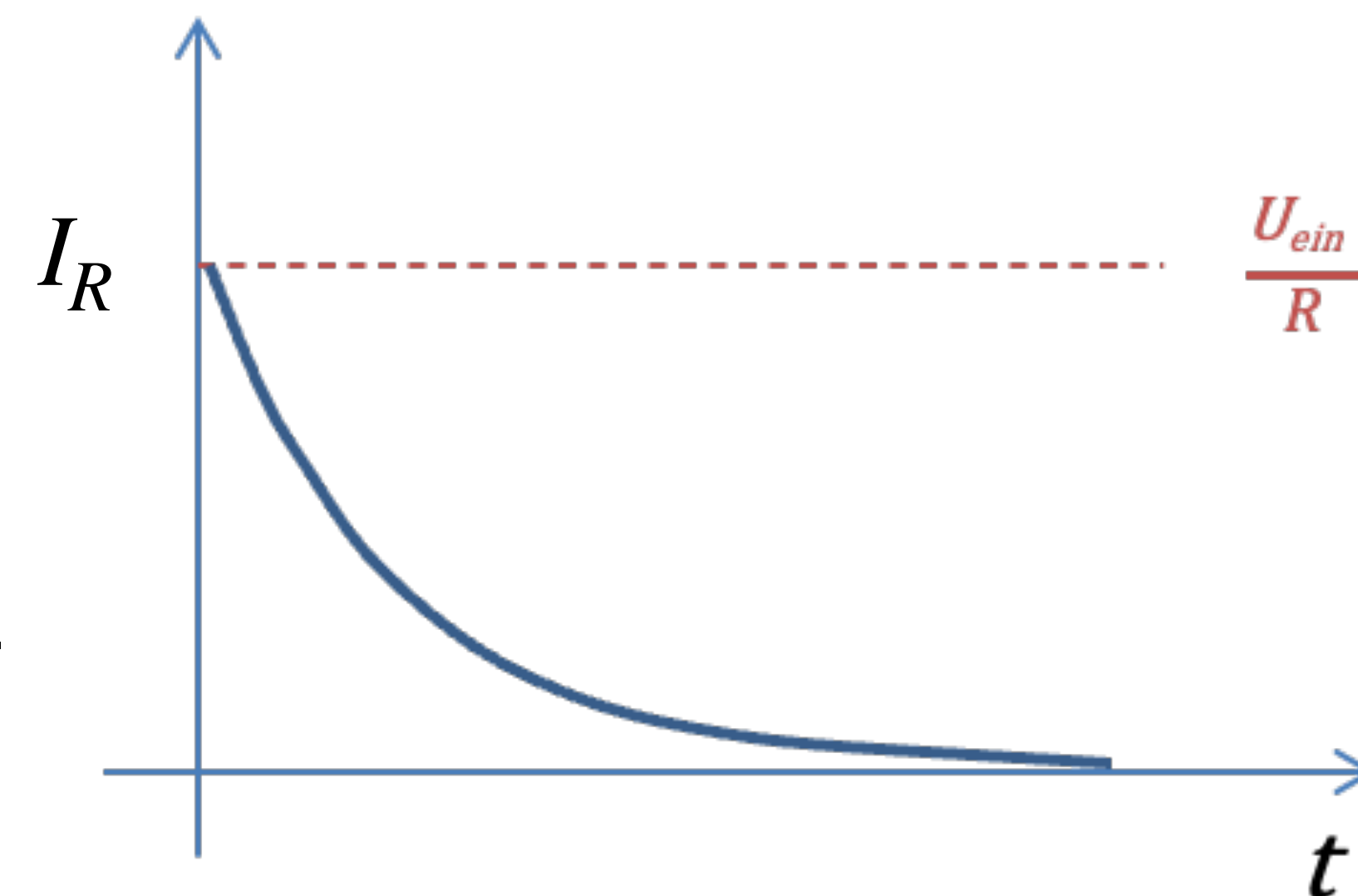

$$I_{RL} = 0$$


$$I_{RL} = \frac{U_{ein}}{R}$$

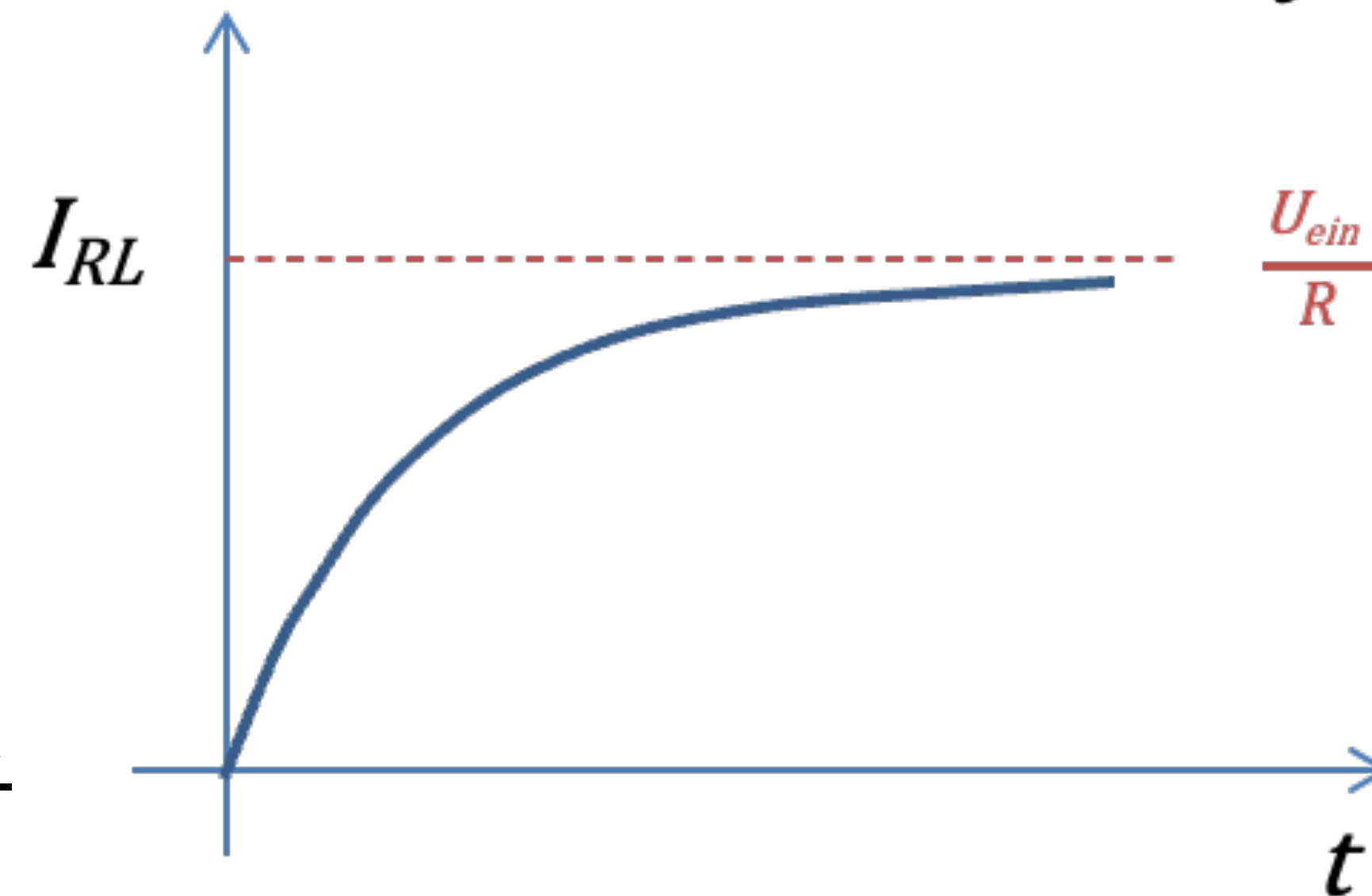

High and Low Pass


To follow in detail at home

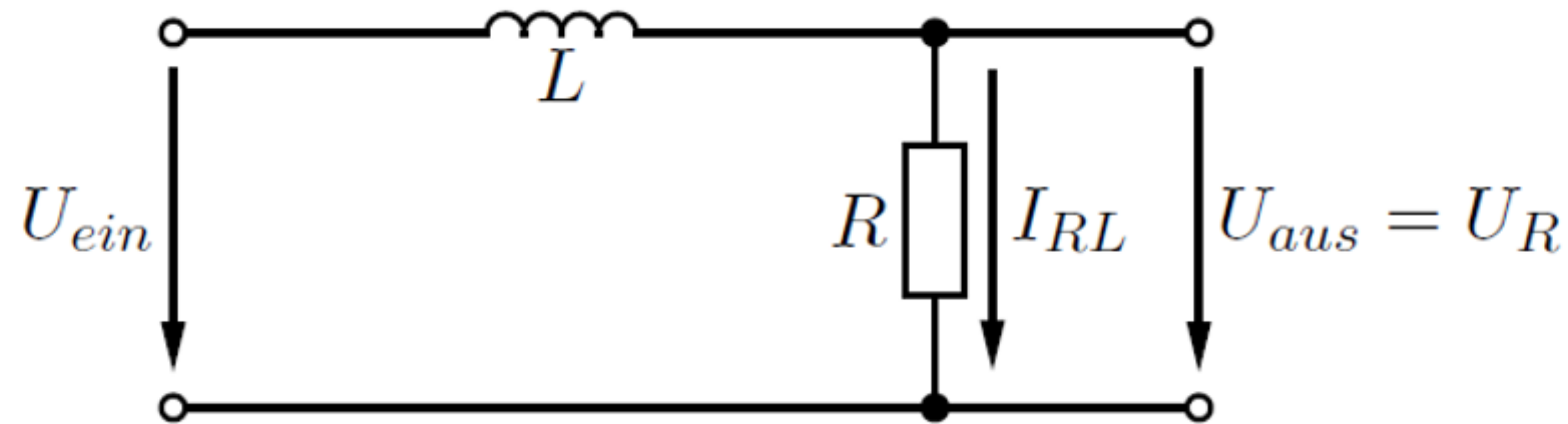- Building on slide 43, analogous to slides 30, 31:
Try to follow the math




Transfer from capacitor case

Low pass / integrator

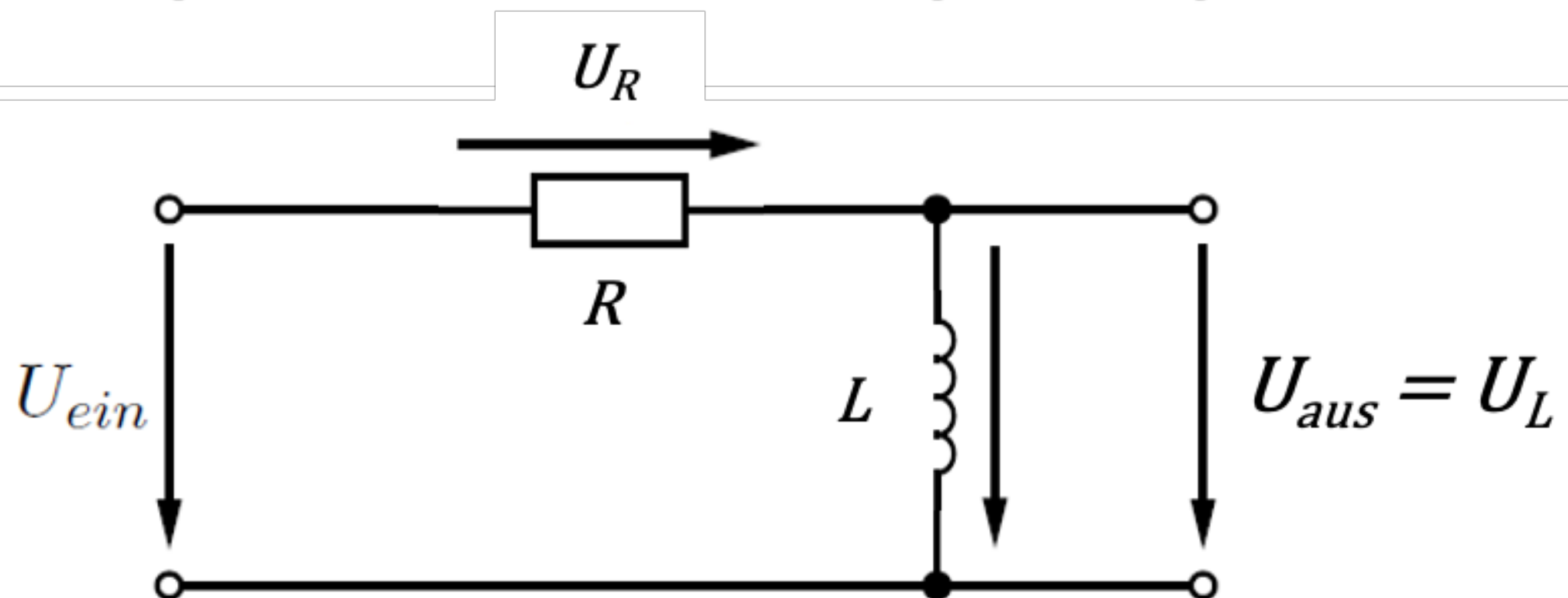

High pass / differentiator

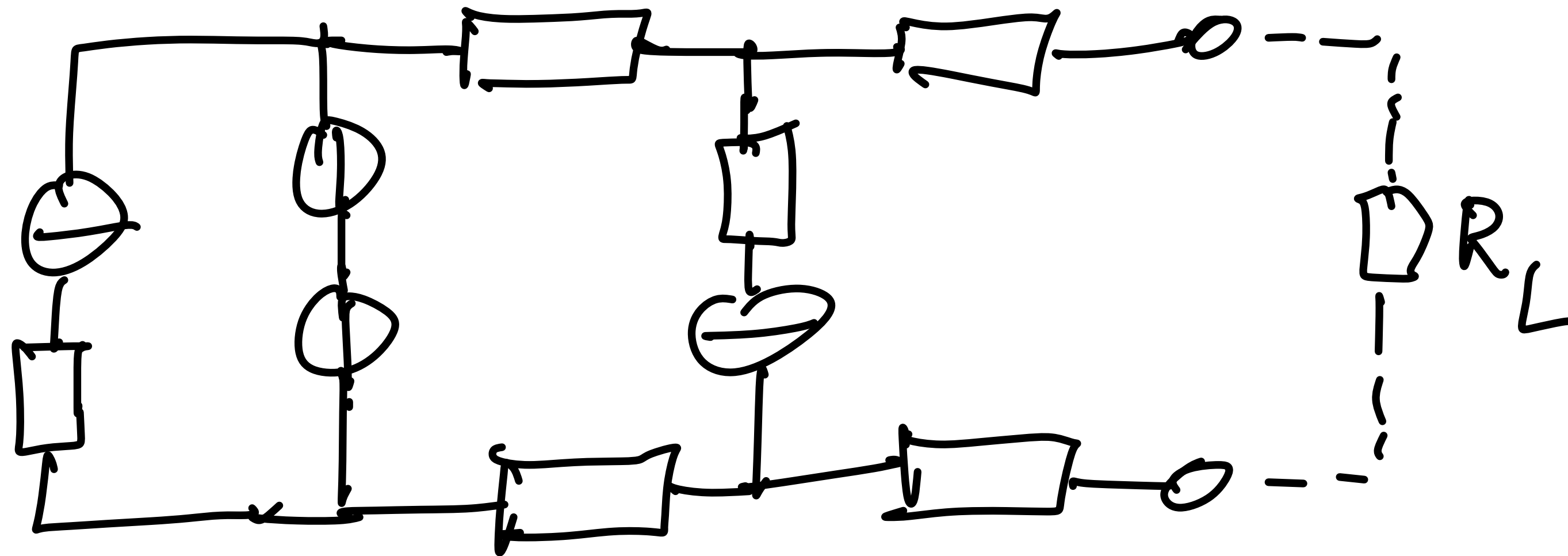- Circuits with resistors, capacitors, inductors and an arbitrary number of current and voltage sources: No limit to complexity!




$U_L?$
 $I_L?$

Thévenin Theorem

also known as: Helmholtz Theorem

- Every linear network can be described by one ideal voltage source U_{Th} and one (internal) resistance R_{Th} in series:
- Answers the following question:
What is the voltage across and the current through a load resistor connected between any 2 nodes of the net?
(NB: the power consumption may not be predicted correctly!)


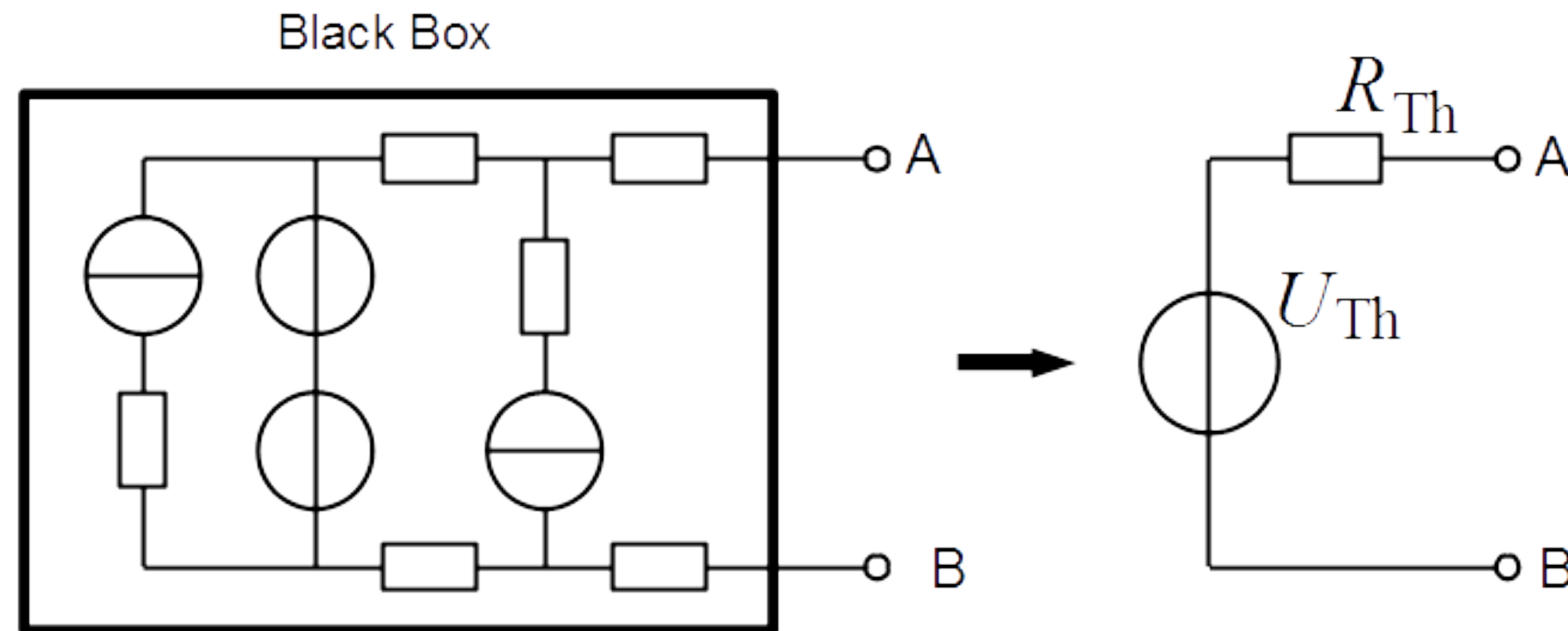
$\Rightarrow$ Thévenin equivalent, with U_{Th} and R_{Th}



Source: Saure, CC-BY-SA-3.0; wikipedia commons

Example: Voltage Divider

Determining the Thévenin Equivalent

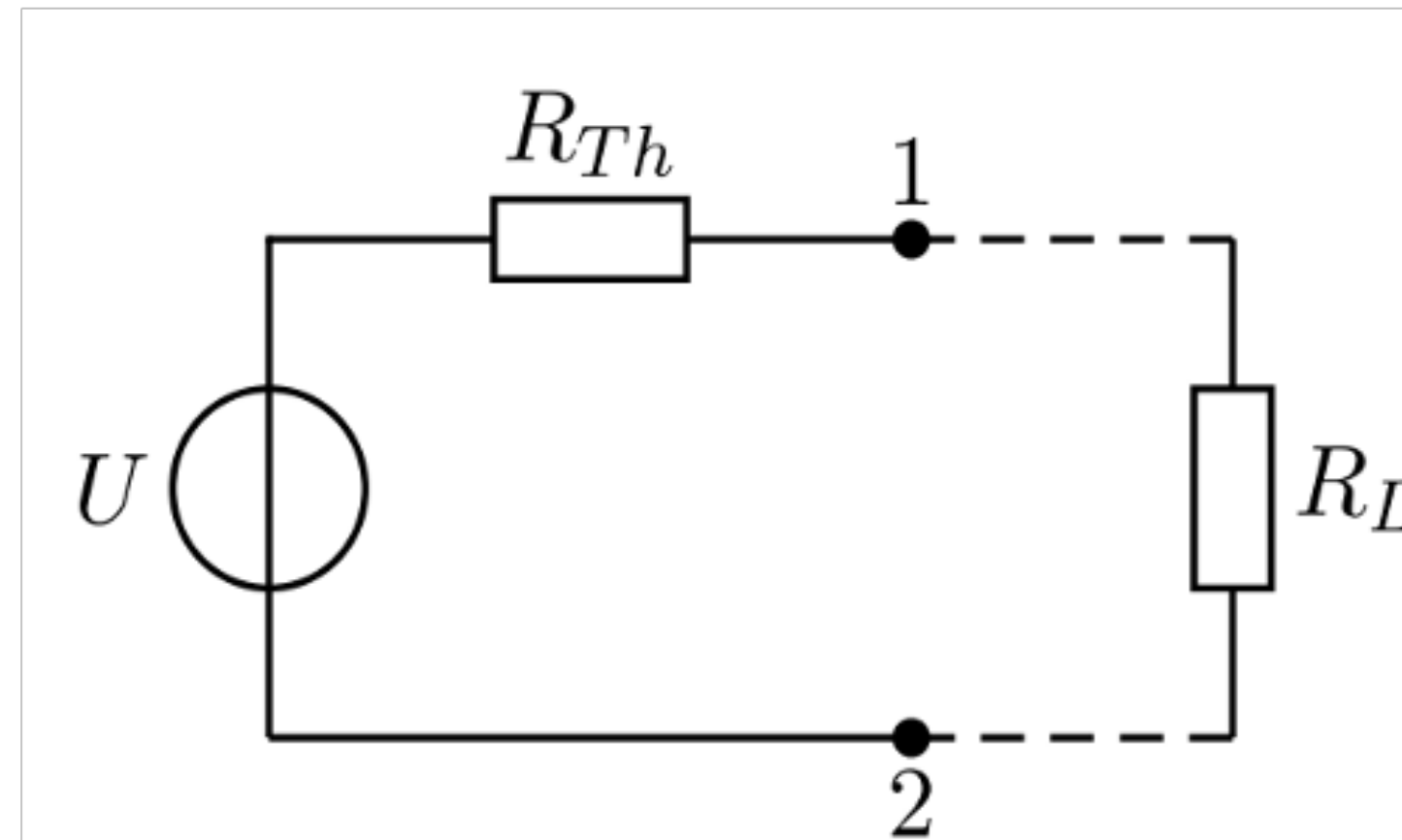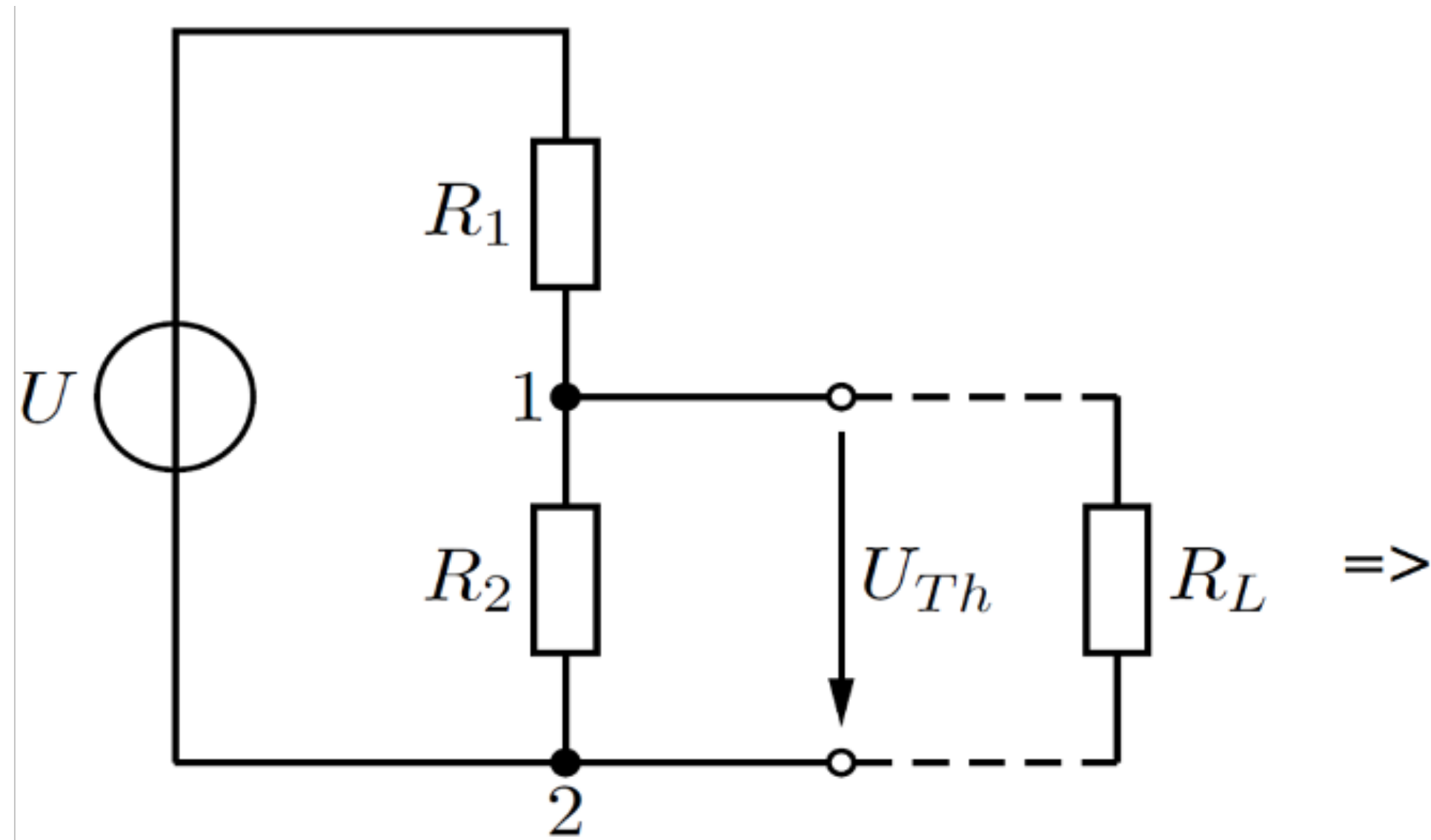

- How are U_{Th} and R_{Th} calculated?


1. U_{Th} corresponds to the output voltage of the divider for the case of no load ($R_L = \infty$)

$$U_{Th} = \frac{UR_2}{R_1 + R_2}$$

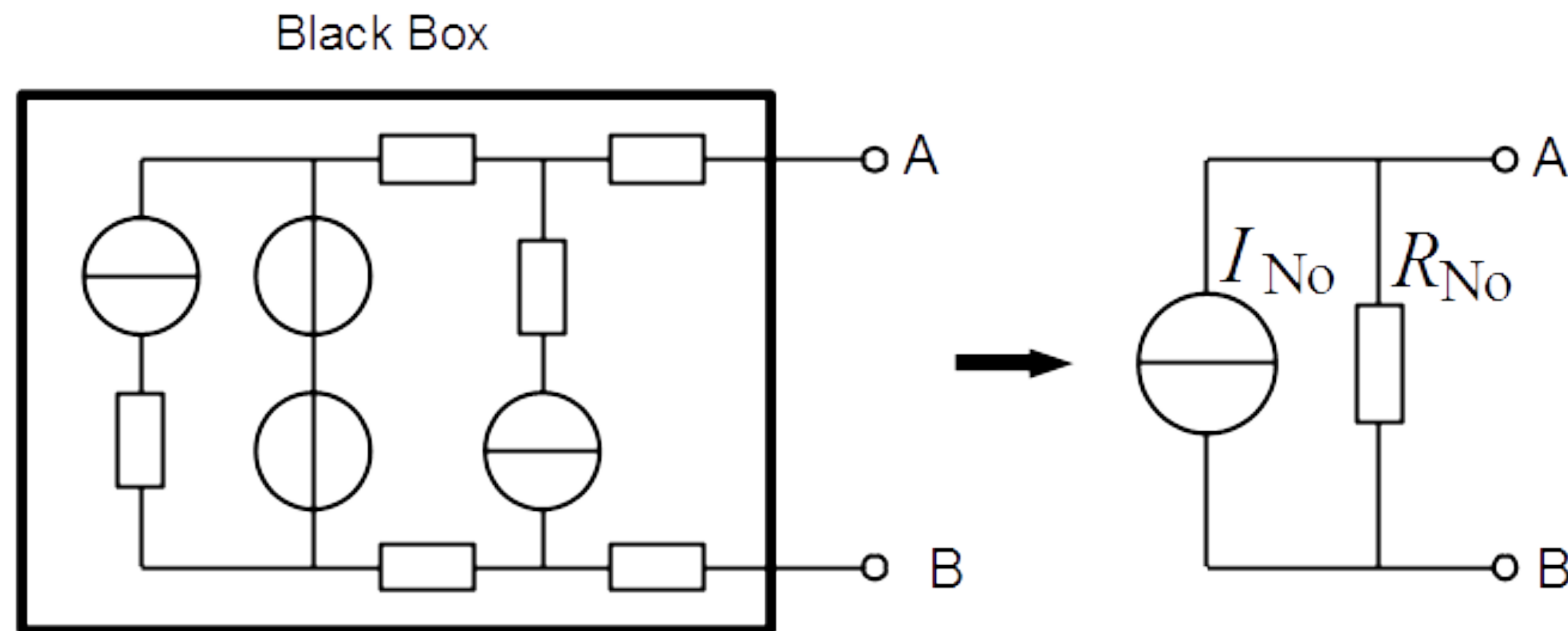2. R_{Th} is determined for the case where all voltage sources are replaced by a short circuit and all current sources are replaced with an open circuit.

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$

- Every linear network can be described by an ideal current source I_N and a parallel internal resistor R_N :




$\Rightarrow$ Northon Equivalent, with I_{No} and R_{No}

Source: Saure, CC-BY-SA-3.0; wikimedia commons

Example: Voltage Divider

Determining the Northon Equivalent

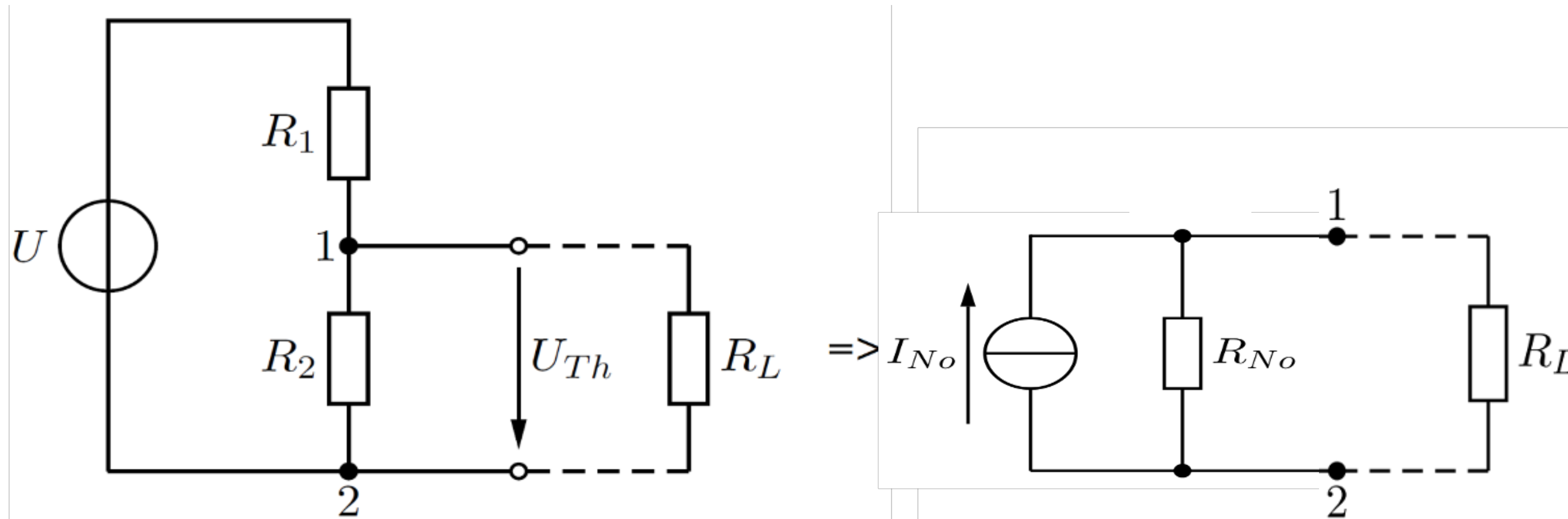

- Same procedure as for the Thévenin equivalent

1. I_{No} corresponds to the output current of the voltage divider for a short circuit ($R_L = 0$).

$$I_{No} = \frac{U}{R_1}$$



2. R_{No} is calculated by replacing all voltage sources by a short circuit and all current sources by an open circuit.

$$R_{No} = \frac{R_1 R_2}{R_1 + R_2}$$

Thévenin and Northon

Conversions between the two schemes

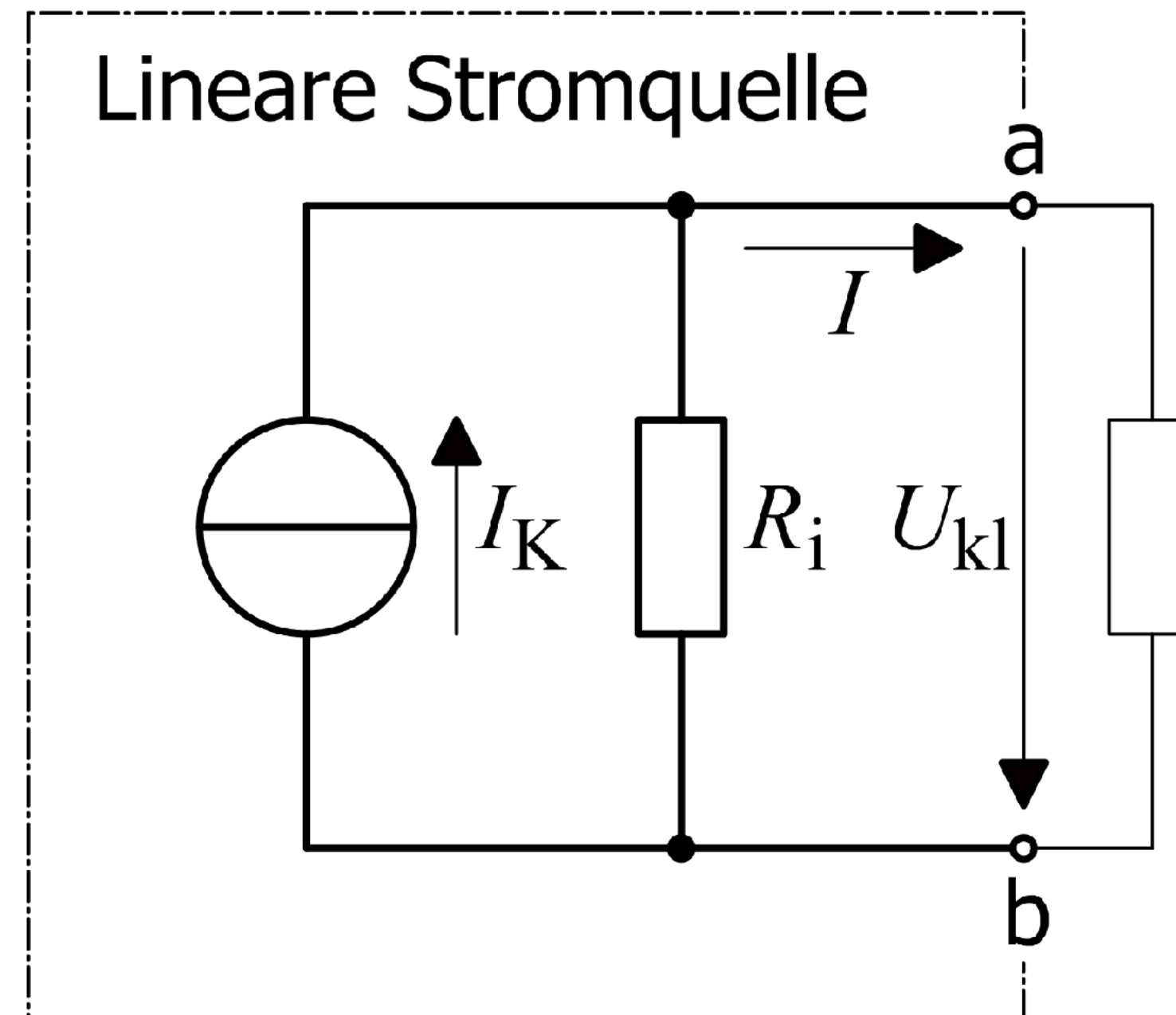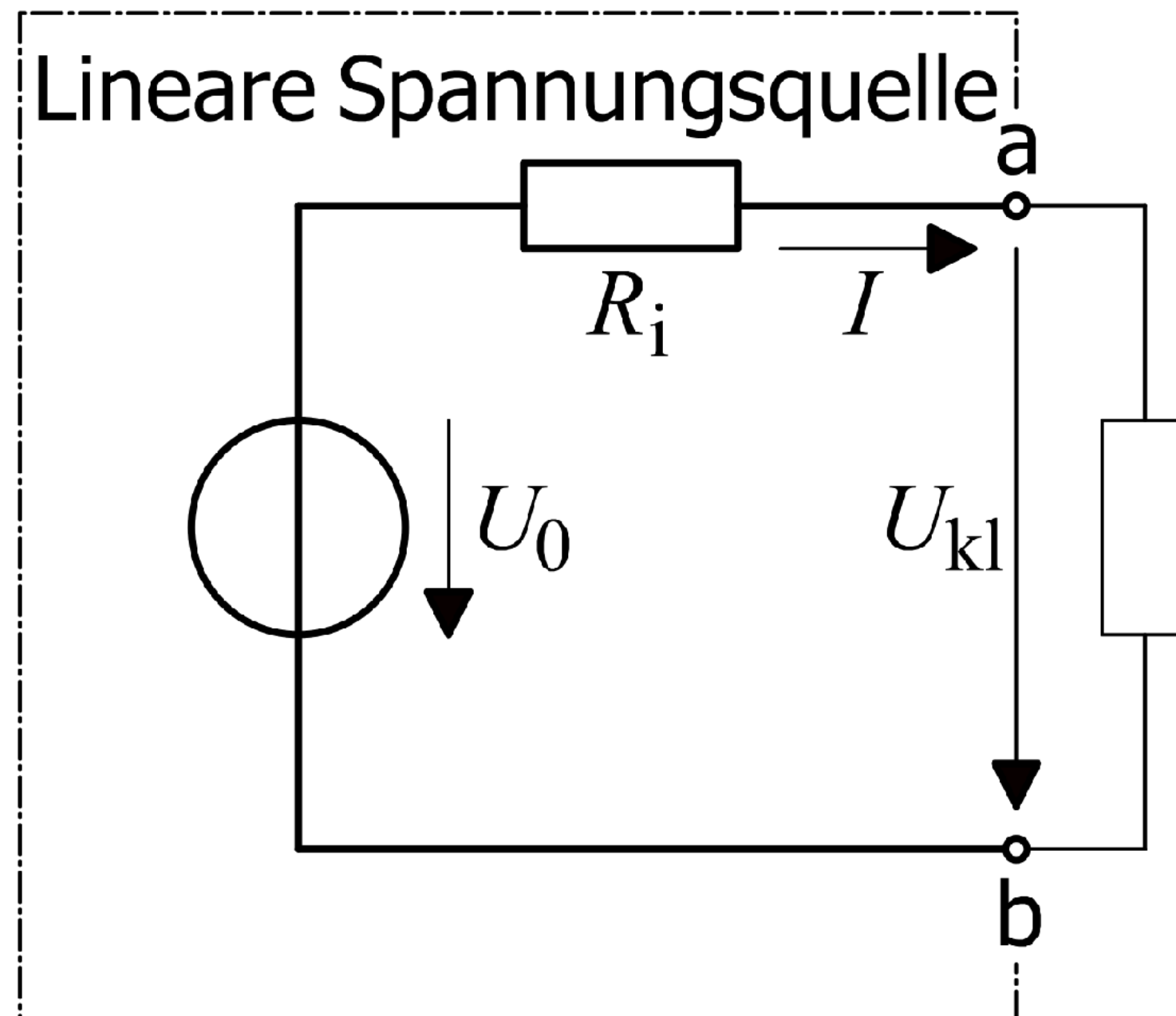- A net can be represented both by a Thévenin and a Northon equivalent




Source: Saure, CC-BY-SA-3.0; wikimedia commons

- Conversion:
 $R_{No} = R_{Th}$
 $I_{No} = U_{Th}/R_{No}$

Food for thought:

Seen from the outside both options are identical - where are the differences?

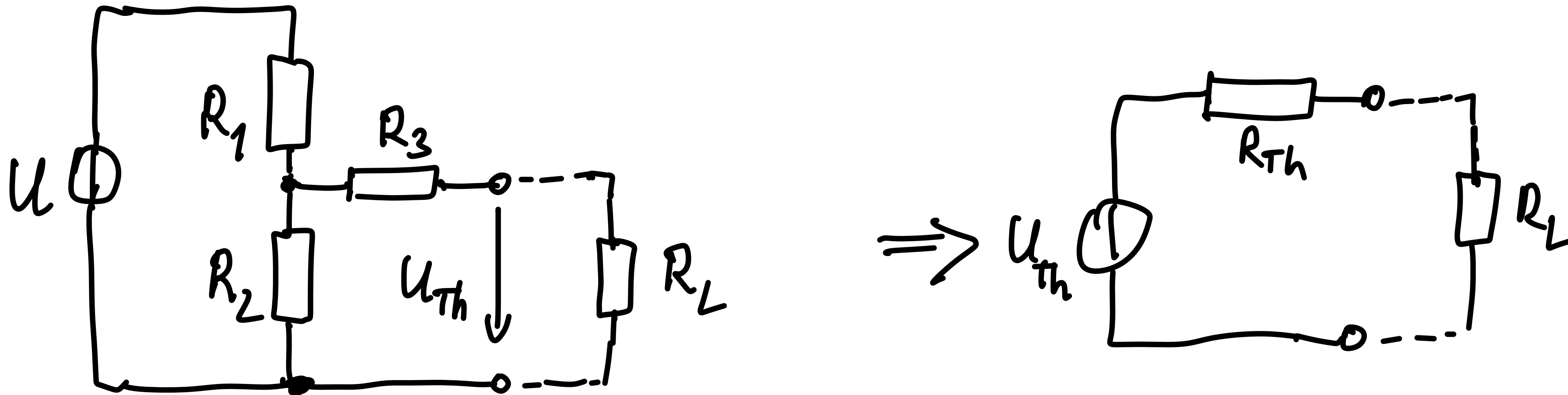- Slight increase in complexity: Additional resistor R_3 .
What happens to U_{Th} , R_{Th} ?




For U_{Th} : Without load this is identical to the “simple” voltage divider!

$$U_{Th} = \frac{UR_2}{R_1 + R_2}$$

For R_{Th} : In addition R_3 in series:

$$R_{Th} = R_1 + R_2 + R_3 = \frac{R_1 R_2}{R_1 + R_2} + R_3$$


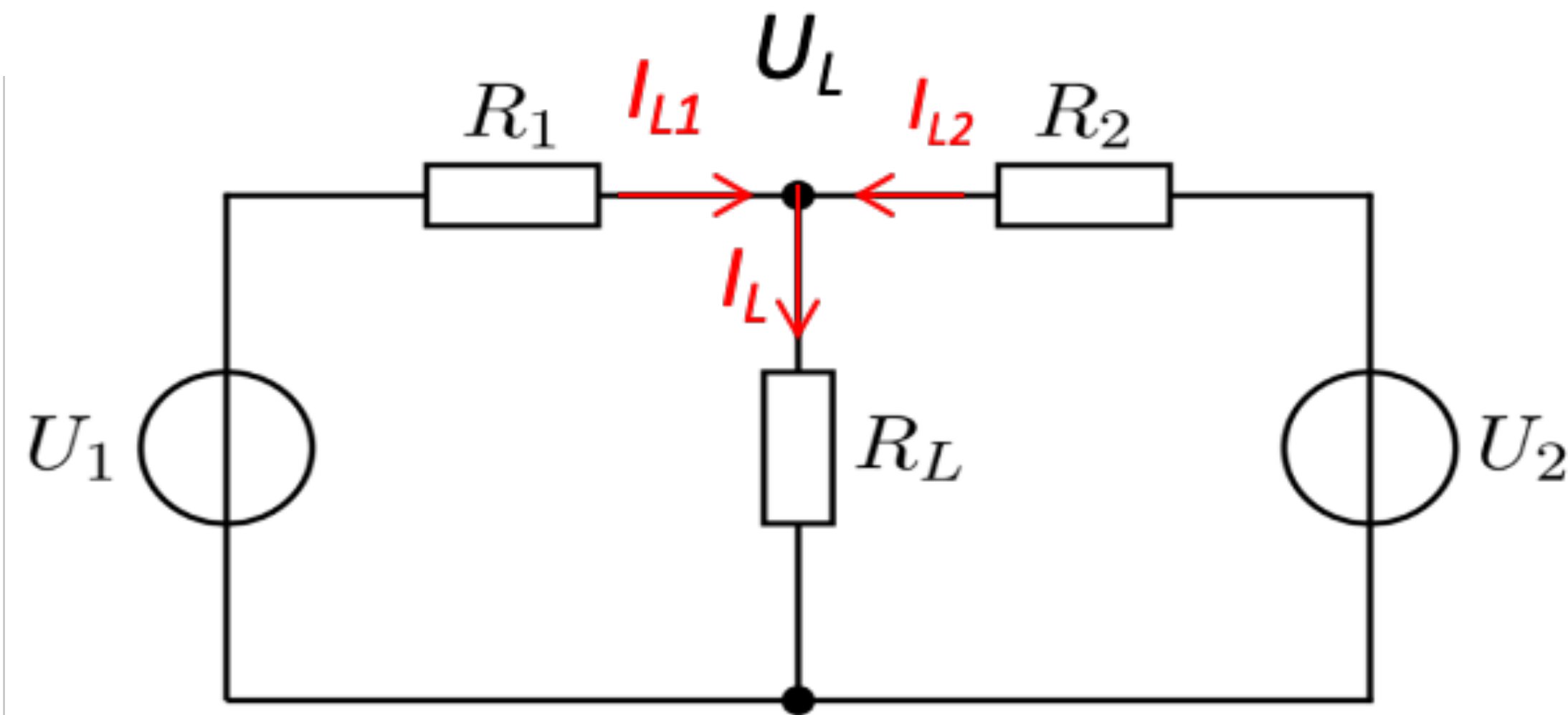
The Superposition Principle - for a simple example (“T-pad”):



Circuit with two voltage sources and 3 resistors.
What is the load current through R_L ?


A superposition of two circuits across R_L .
As usual Kirchhoff's laws are very helpful:
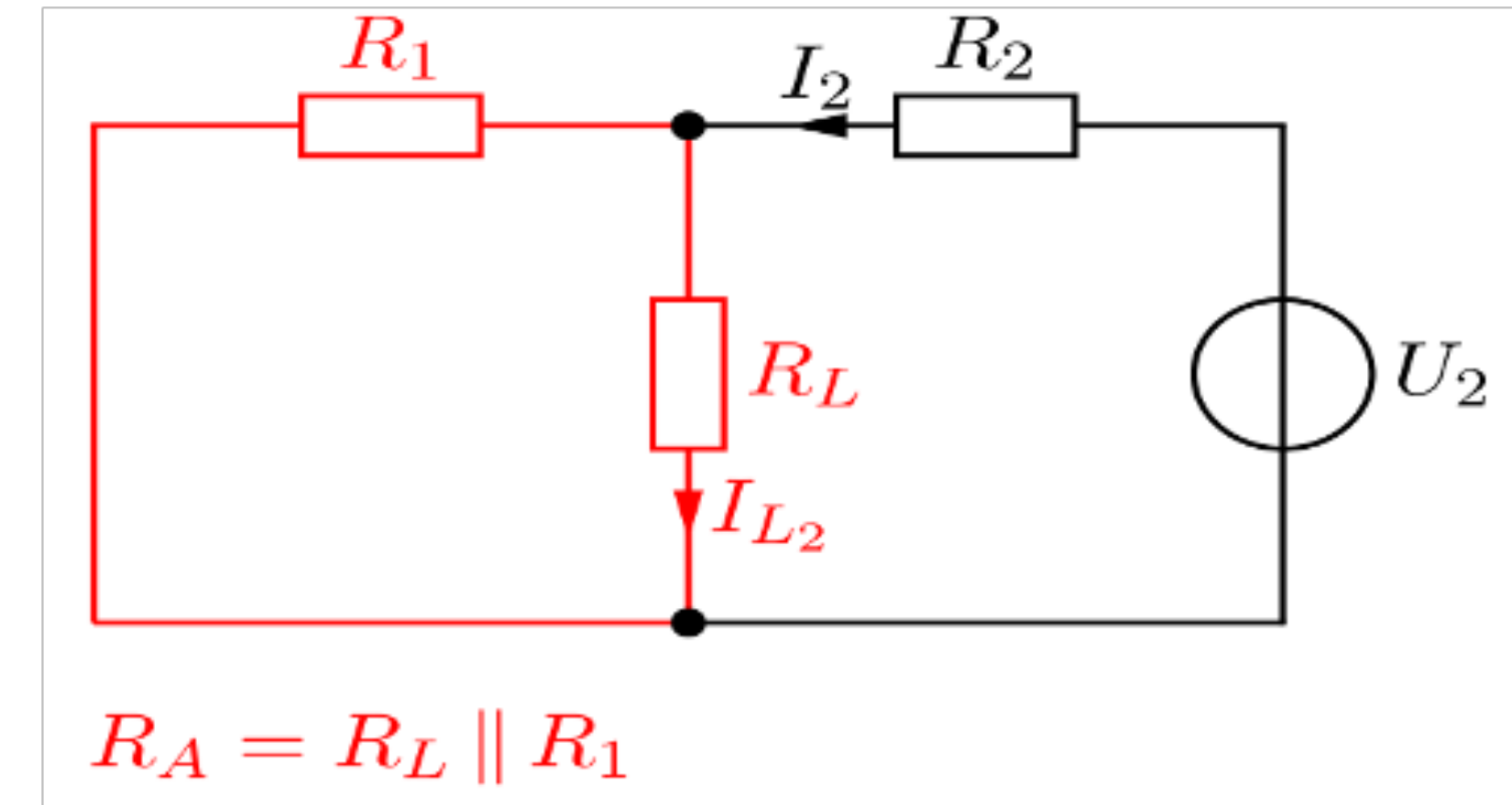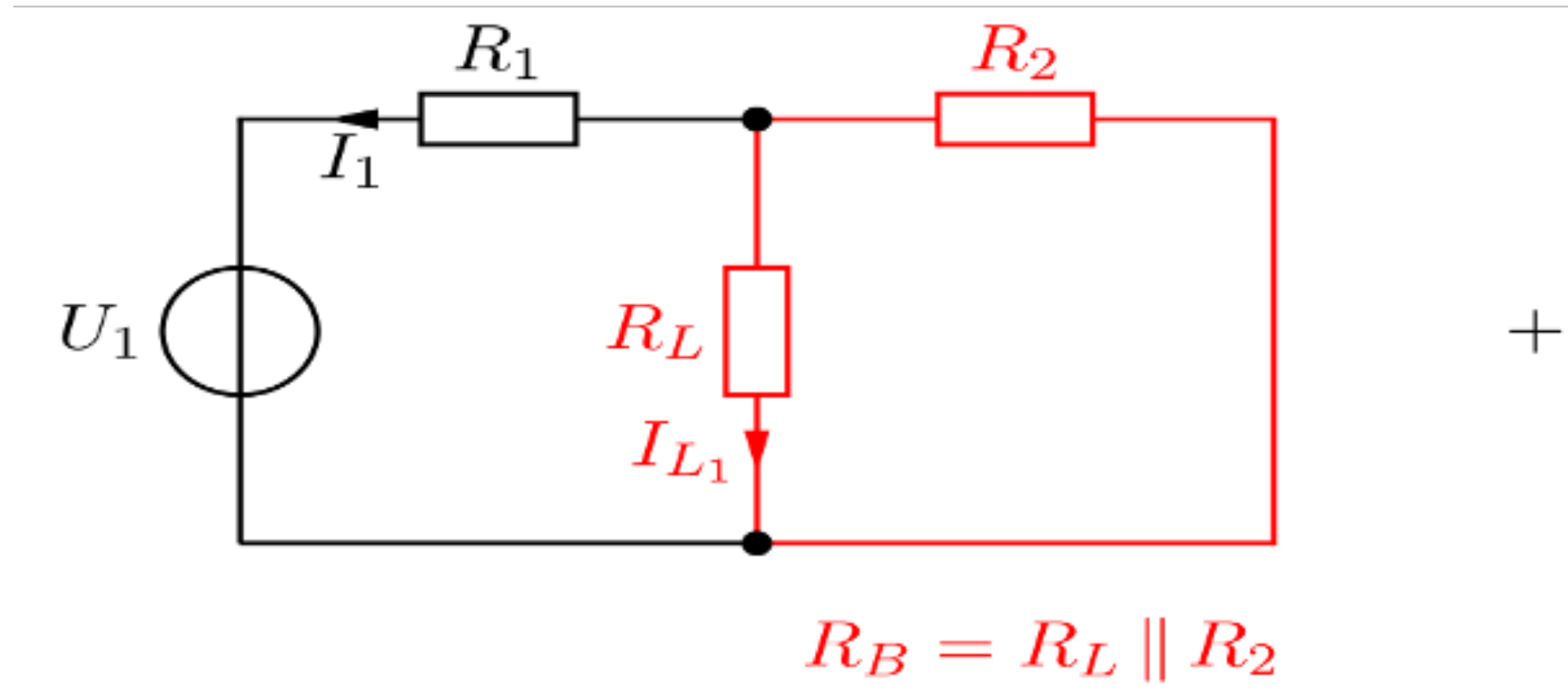
$$I_L = I_{L1} + I_{L2} \Rightarrow U_L = U_{L1} + U_{L2}$$



Analyzing Linear Networks

The Superposition Principle II

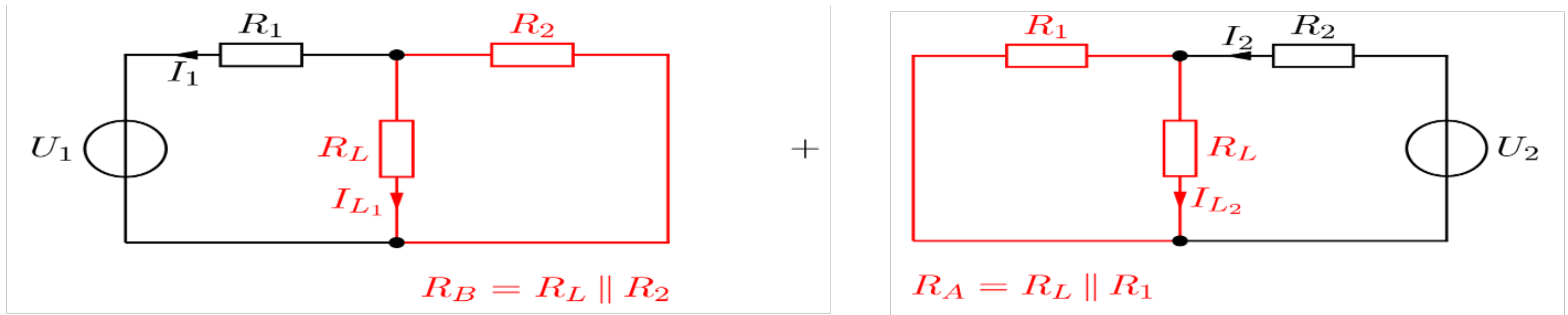

- To fully analyze the net, all but one current or voltage sources are replaced by the internal resistance in turn (here $R_i = 0$) and the resulting partial circuits are analyzed.

$$U_{L_1} = \frac{U_1 R_B}{R_1 + R_B} \quad R_B = \frac{R_L R_2}{R_L + R_2} \quad \text{and} \quad U_{L_2} = \frac{U_2 R_A}{R_1 + R_A} \quad R_A = \frac{R_L R_1}{R_L + R_1}$$


$$I_{L_1} = \frac{U_{L_1}}{R_L} \quad \text{and} \quad I_{L_2} = \frac{U_{L_2}}{R_L}$$

resulting in:

$$I_L = I_{L_1} + I_{L_2} = \frac{U_1 R_2 + U_2 R_1}{R_1 R_2 + R_L (R_1 + R_2)}$$

Solving Linear Networks

A system of linear equations

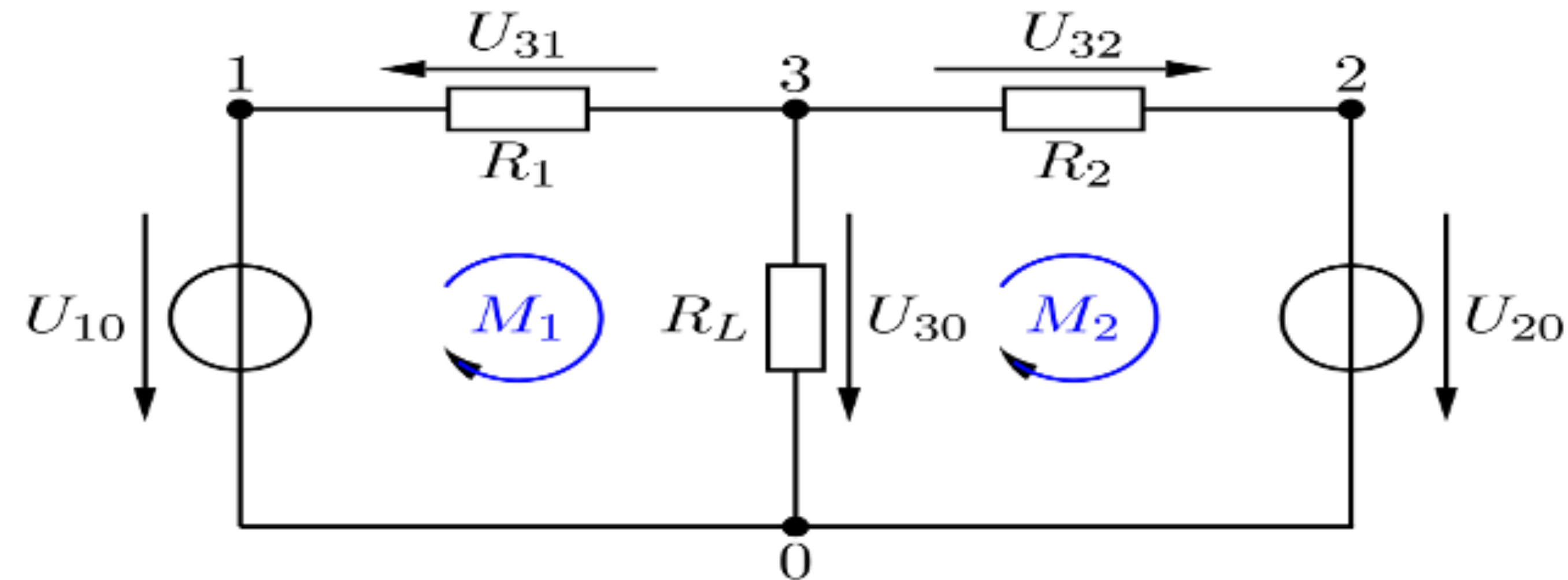

- The question: What is U_{30} , and what is the current through R_L ?

$$I_L = \frac{U_{30}}{R_L}$$

- Ansatz: Rigorous use of Kirchhoff's laws for all relevant nodes and loops.

Sum of currents in node 3 = 0:

$$\frac{U_{31}}{R_1} + \frac{U_{32}}{R_2} + \frac{U_{30}}{R_L} = 0$$

Sum of voltages over loops M 1 & 2 = 0:

$$\begin{aligned} -U_{31} + U_{30} - U_{10} &= 0 \quad (M_1) \\ -U_{30} + U_{32} + U_{20} &= 0 \quad (M_2) \end{aligned}$$

3 unknown voltages: U_{30} , U_{31} , U_{32} ; 3 independent equations: That can be solved!

- A compact way of writing and solving the system of equations:

As a matrix

$$\frac{U_{31}}{R_1} + \frac{U_{32}}{R_2} + \frac{U_{30}}{R_L} = 0$$

To simplify notation:

$$G_i = \frac{1}{R_i}$$

$$-U_{31} + U_{30} - U_{10} = 0$$

$$-U_{30} + U_{32} + U_{20} = 0$$

Can be solved using Cramer's rule:

$$\begin{pmatrix} G_L & G_1 & G_2 \\ 1 & -1 & 0 \\ 1 & 0 & -1 \end{pmatrix} \cdot \begin{pmatrix} U_{30} \\ U_{31} \\ U_{32} \end{pmatrix} = \begin{pmatrix} 0 \\ U_{10} \\ U_{20} \end{pmatrix}$$

$$U_{30} = \det \begin{pmatrix} 0 & G_1 & G_2 \\ U_1 & -1 & 0 \\ U_2 & 0 & -1 \end{pmatrix} \cdot \frac{1}{\det \begin{pmatrix} G_L & G_1 & G_2 \\ 1 & -1 & 0 \\ 1 & 0 & -1 \end{pmatrix}}$$

result:
$$U_{30} = \frac{G_1 U_{10} + G_2 U_{20}}{G_L + G_1 + G_2}$$

Next Lectures:

Digital - Thursday, November 2

Analog 04 - Chapter 02 - Tuesday, November 7

Electronics for Physicists

Analog Electronics

Frank Simon

Institute for Data Processing and Electronics

31.10.2023

KIT, Winter 2023/24