

Electronics for Physicists

Analog Electronics

Chapter 2; Lecture 04

Frank Simon

Institute for Data Processing and Electronics

07.11.2023

KIT, Winter 2023/24

Chapter 2

Circuits with R, C, L

- AC behavior of R, C, L
- Complex Voltages & Currents
- Filters
- Oscillators


Overview

1. Basics
2. **Circuits with R, C, L with Alternating Current**
3. Diodes
4. Operational Amplifiers
5. Transistors - Basics
6. 2-Transistor Circuits
7. Field Effect Transistors
8. Additional Topics
 - Filters
 - Voltage Regulators
 - Noise


Chapter 2

AC Behavior


In: Circuits with R , C , L

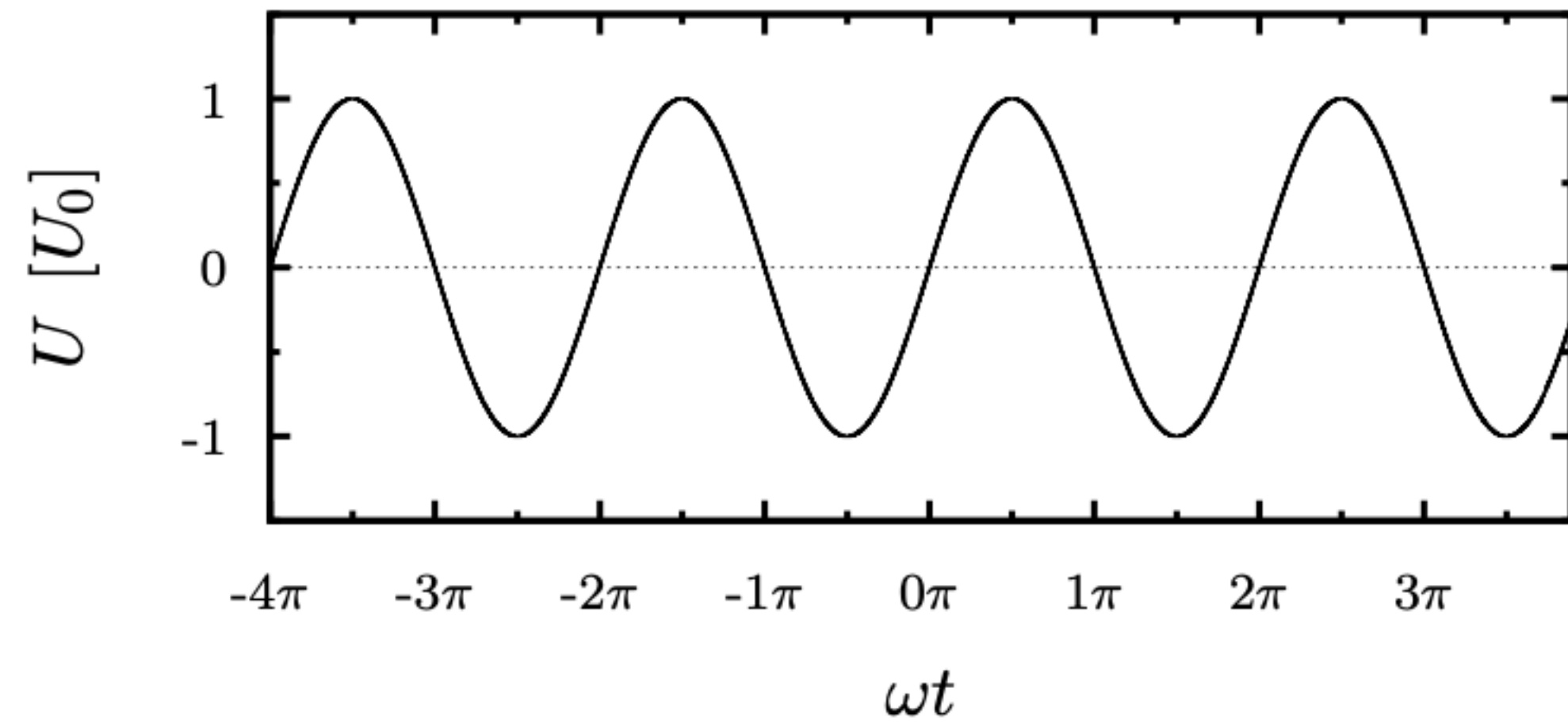


harmonic oscillation

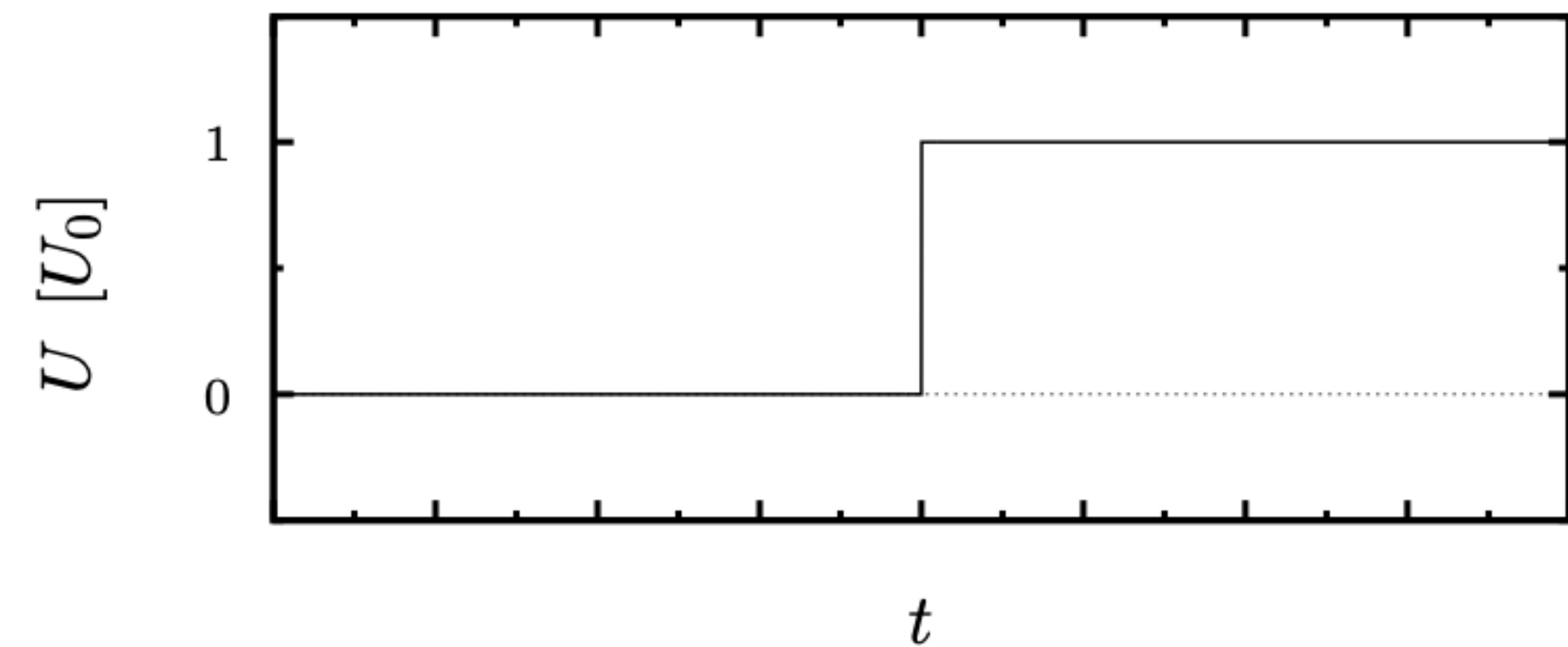

step function

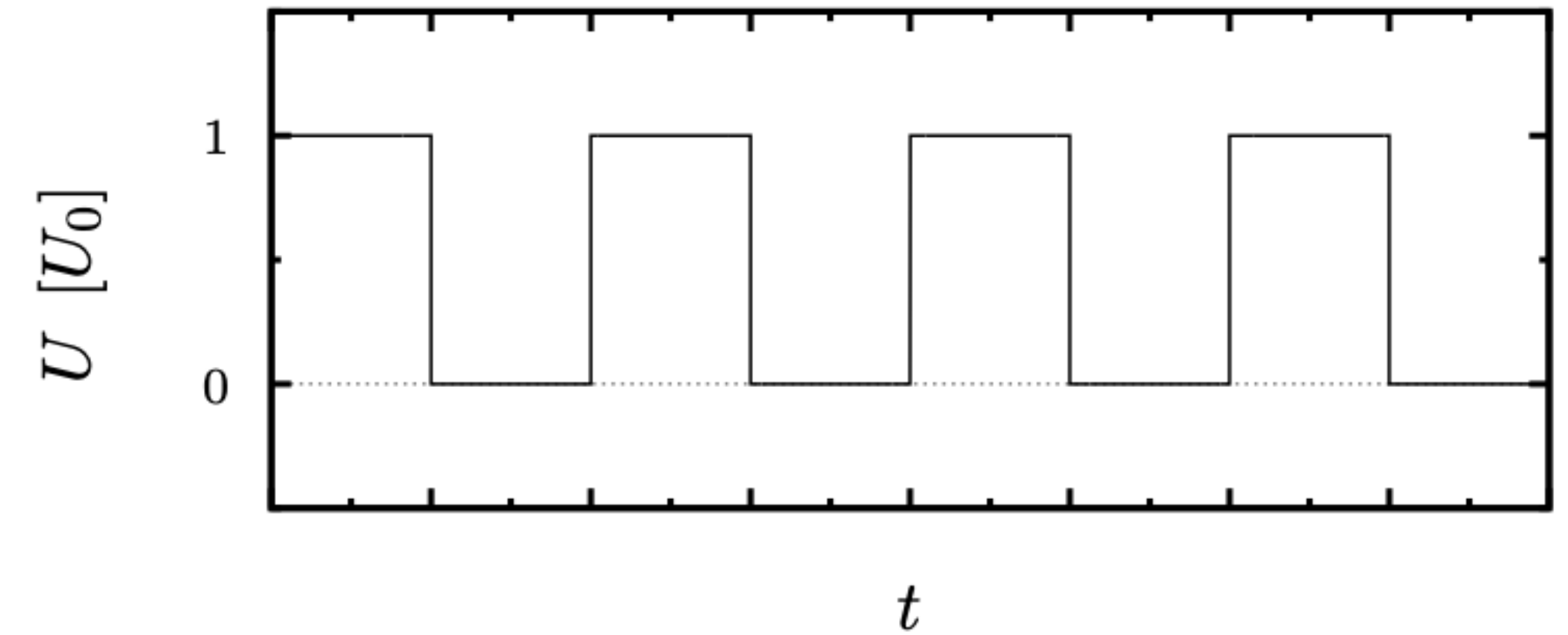

square wave

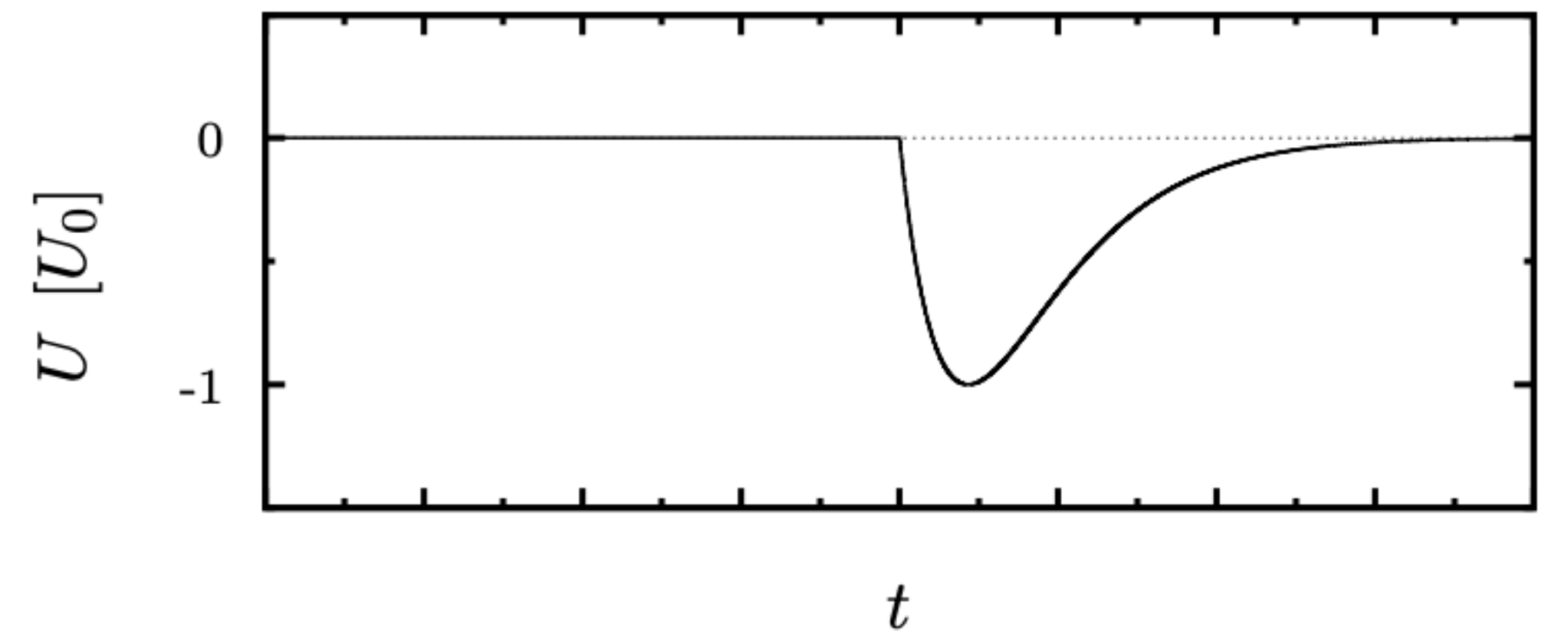


typical detector signal after RC-CR filtering

Behavior for harmonic Signals

Resistor


- Harmonic signal

$$U(t) = U_0 \sin(\omega t + \varphi)$$

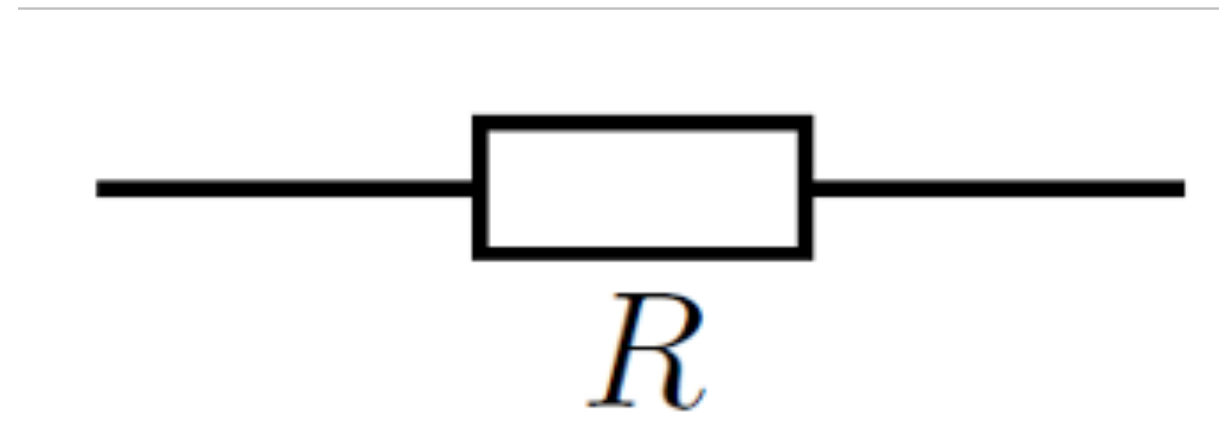

$$U(t) = R I(t)$$

Voltage and current are in phase.

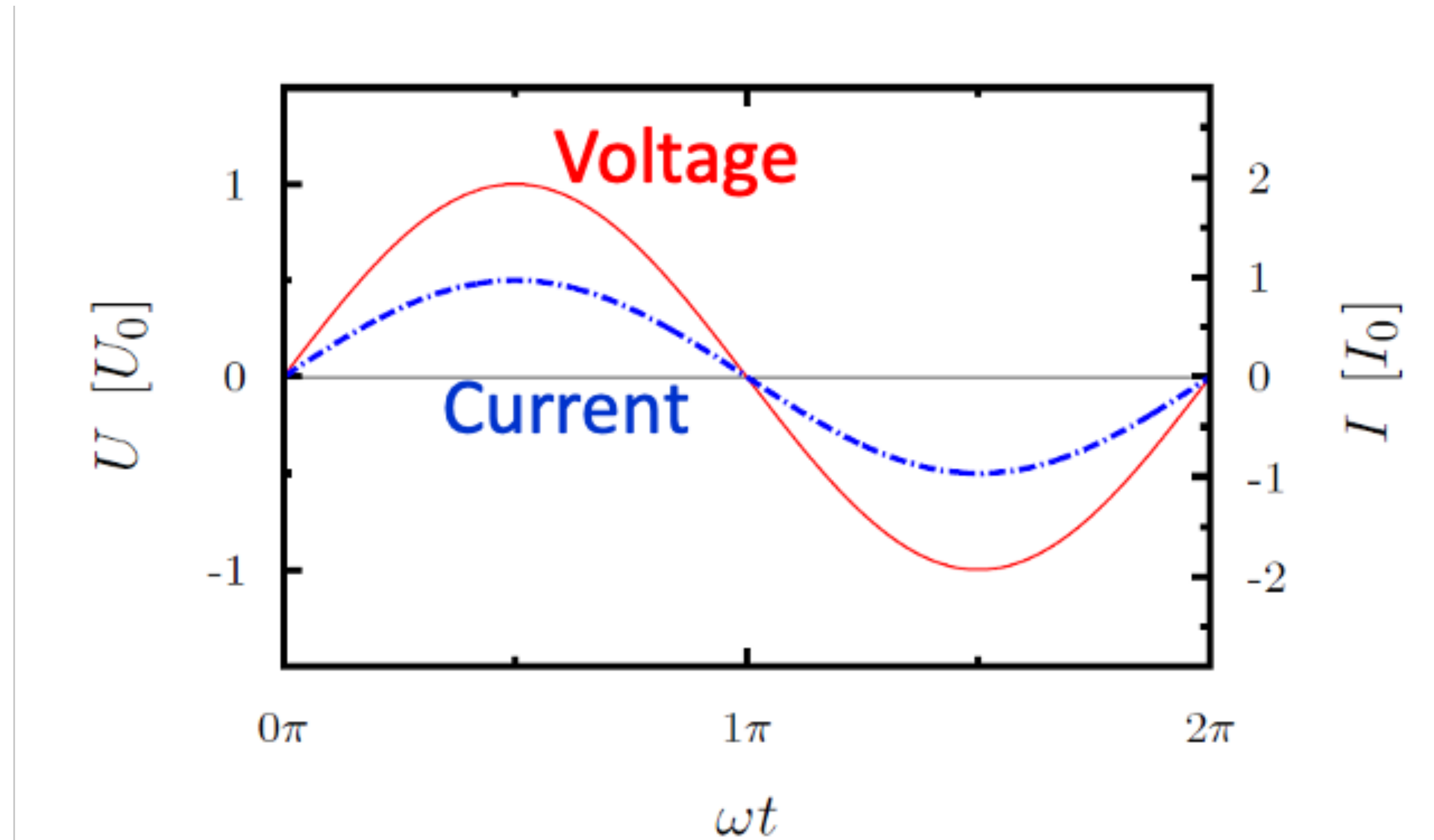

Behavior for harmonic Signals

Capacitor


- Harmonic signal

$$U(t) = U_0 \sin(\omega t + \varphi)$$



$$I = C \frac{dU}{dt} \Rightarrow I(t) = U_0 \omega C \cos(\omega t)$$

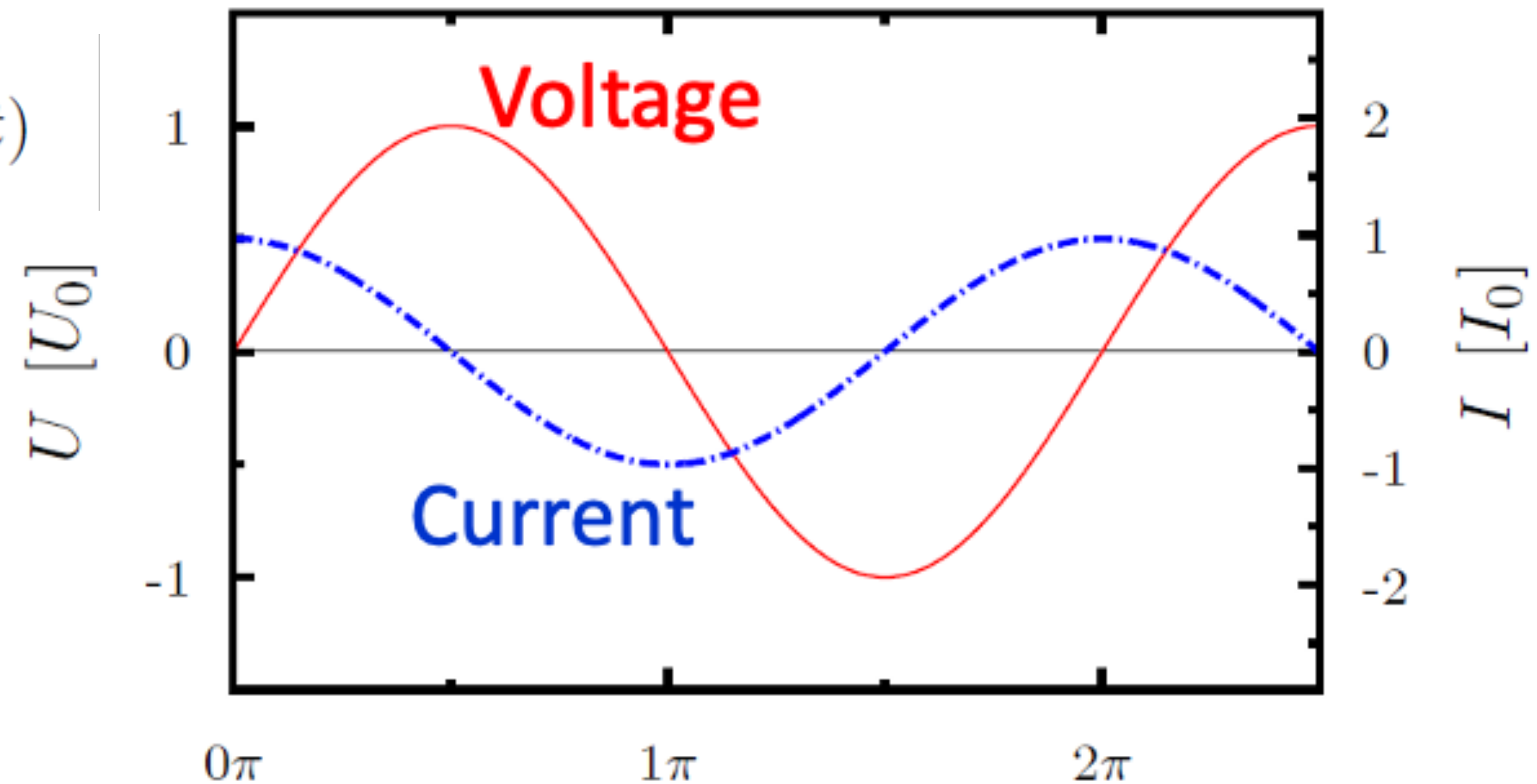90° phase shift:
Voltage follows current!




Behavior for harmonic Signals

Inductor

- Harmonic signal:

$$U(t) = U_0 \sin(\omega t + \varphi)$$

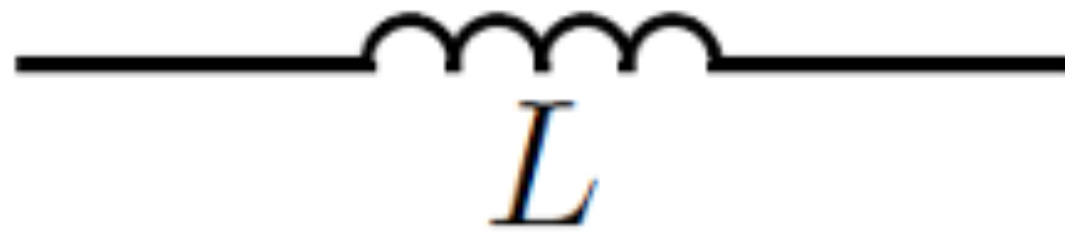


$$U = L \frac{dI}{dt}$$

$$I(t) = I_0 \sin(\omega t)$$

$$\Rightarrow U(t) = I_0 \omega L \cos(\omega t)$$

90° phase shift:

Current follows voltage.

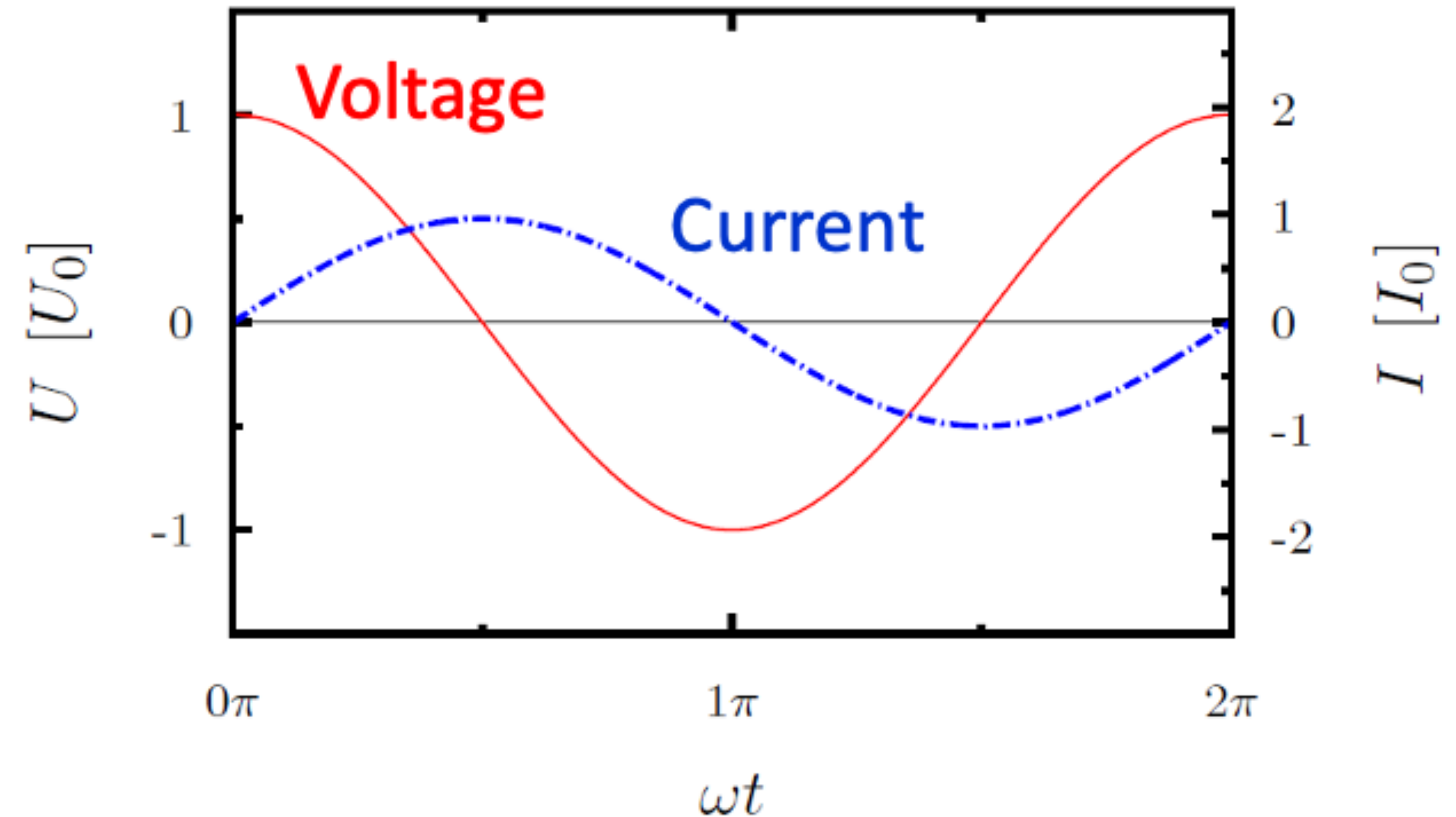

Chapter 2

Complex Currents and Voltages

In: Circuits with R , C , L

Representation via Complex Numbers


Time dependence via complex voltages and currents

- To describe the time dependence it is convenient to use complex numbers:

NB: in EE normally “j”
instead of “i” is used for $\sqrt{-1}$

$$\underline{z} = \operatorname{Re}(\underline{z}) + j \operatorname{Im}(\underline{z}) = a + j b$$

Graphical illustration in complex plane

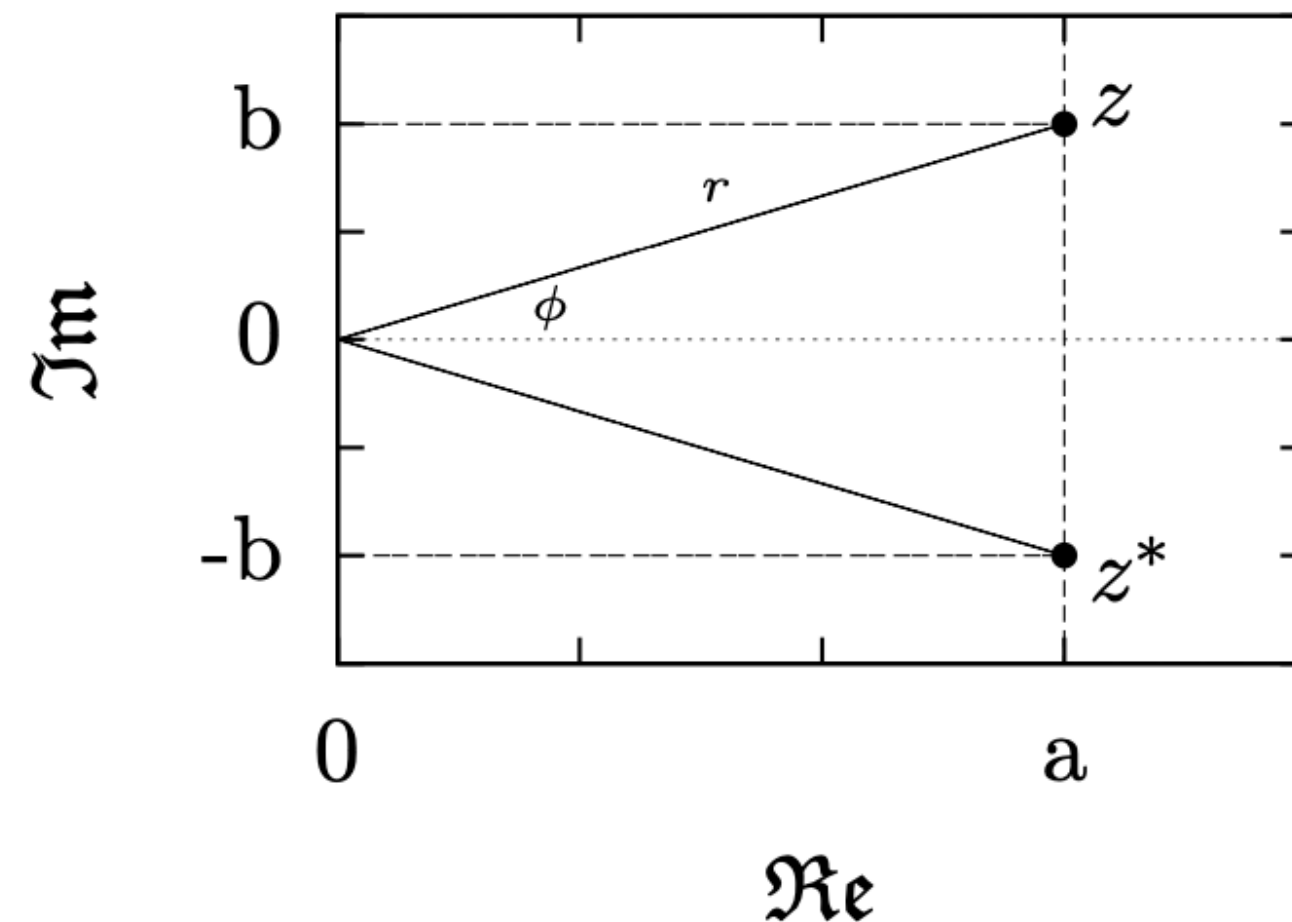

important relationship for harmonic signals: Euler's formula

$$e^{j\varphi} = \cos \varphi + j \sin \varphi$$

Complex voltage:

$$\underline{U} = U_0 e^{j\omega t}$$

In the time domain (*Zeitbereich*):

Differentiation becomes a multiplication by frequency $j\omega$

$$\frac{dF}{dt} \rightarrow j\omega \underline{F}$$

Integration becomes a division by $j\omega$

$$\int F dt \rightarrow \frac{1}{j\omega} \underline{F} \qquad \omega = 2\pi f$$

	time domain	complex plane
Resistor	$U = RI$	$\underline{U} = R\underline{I}$
Capacitor	$I = C \frac{dU}{dt}$	$\underline{I} = j\omega C \underline{U}$
Inductor	$U = L \frac{dI}{dt}$	$\underline{U} = j\omega L \underline{I}$

Generalized Ohm's Law

Verallgemeinertes Ohmsches Gesetz

- (Complex) impedance $\underline{Z}$ describing the relationship between complex voltages $\underline{U}$ and complex currents $\underline{I}$

$$\underline{U} = \underline{Z} \underline{I} \quad \text{Impedanz}$$

Resistor: $\underline{Z}_R = R$

Capacitor: $\underline{Z}_C = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$

Inductor: $\underline{Z}_L = j\omega L$

Circuits with impedances:

series: $\underline{Z} = \underline{Z}_1 + \underline{Z}_2$

parallel: $\underline{Z} = \left(\frac{1}{\underline{Z}_1} + \frac{1}{\underline{Z}_2} \right)^{-1}$

The opposition to alternating currents by capacitors and inductors is also referred to as **reactance**: No power dissipation (in contrast to resistance)


Blindwiderstand

Representation in the Complex Plane

Darstellung in der komplexen Ebene

- General remark: The impedance of an ohmic resistor is real, the impedance of capacitors and inductors is imaginary.

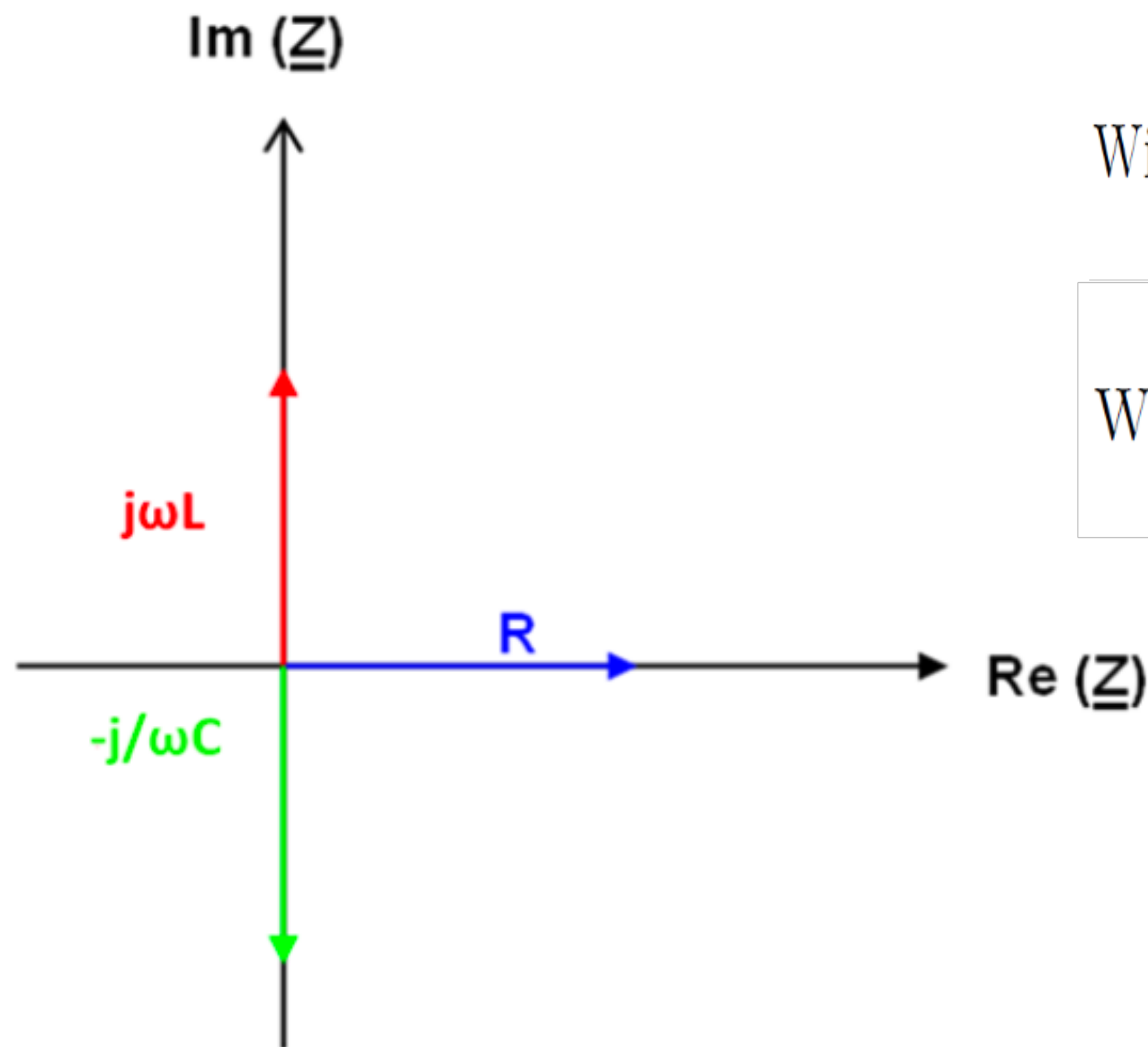Representation of $\underline{Z}$ in the complex plane:



$$\text{With } \underline{U} = U_0 e^{j\omega t} \text{ and } \underline{I} = C \frac{d\underline{U}}{dt} \Leftrightarrow \underline{I} = j\omega C U_0 e^{j\omega t} \text{ and } Z_C = \frac{\underline{U}}{\underline{I}} = \frac{1}{j\omega C}$$

$$\text{With } \underline{U} = L \frac{d\underline{I}}{dt} \Leftrightarrow L \underline{I} = \int \underline{U} dt = \frac{1}{j\omega} U_0 e^{j\omega t} \text{ and } Z_L = \frac{\underline{U}}{\underline{I}} = j\omega L$$


Frequency Behaviour: Summary

Frequenzverhalten

	$\omega \sim 0$	$\omega \rightarrow \infty$
Resistor	$\underline{U} = R\underline{I}$ frequency independent	
Capacitor $\underline{I} = j\omega C\underline{U}$	$I = 0$ open circuit	$U \rightarrow 0$ short circuit
Inductor $\underline{U} = j\omega L\underline{I}$	$U = 0$ short circuit	$I \rightarrow 0$ open circuit

Concrete Example: Generalized Ohm's Law

Resistor and Inductor

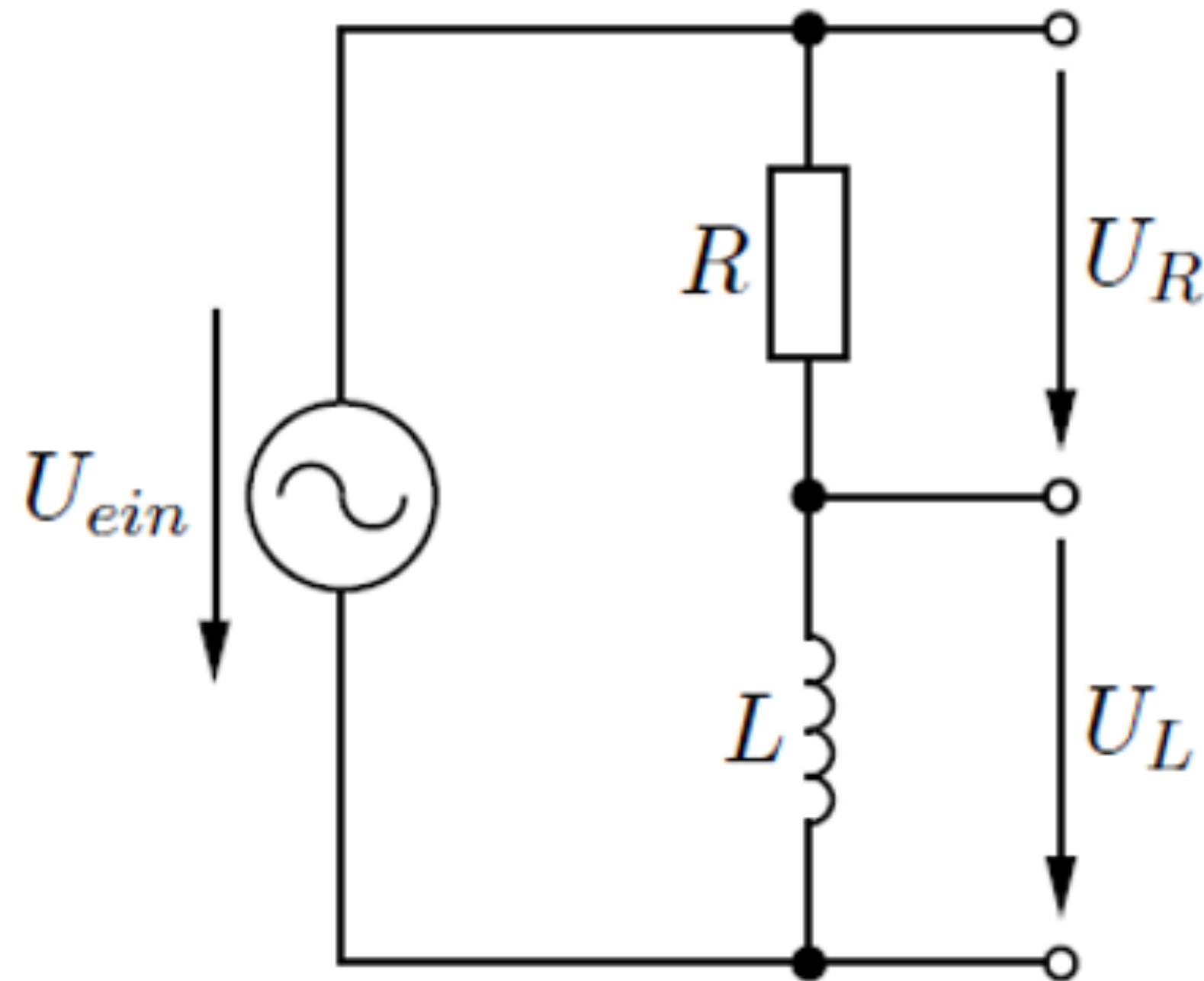

Input voltage


$$\underline{U}_{ein} = U_0 e^{j\omega t}$$

The problem:

What are $\underline{U}_R$ and $\underline{U}_L$?

and: What are the real voltages?

Ansatz: Voltage divider

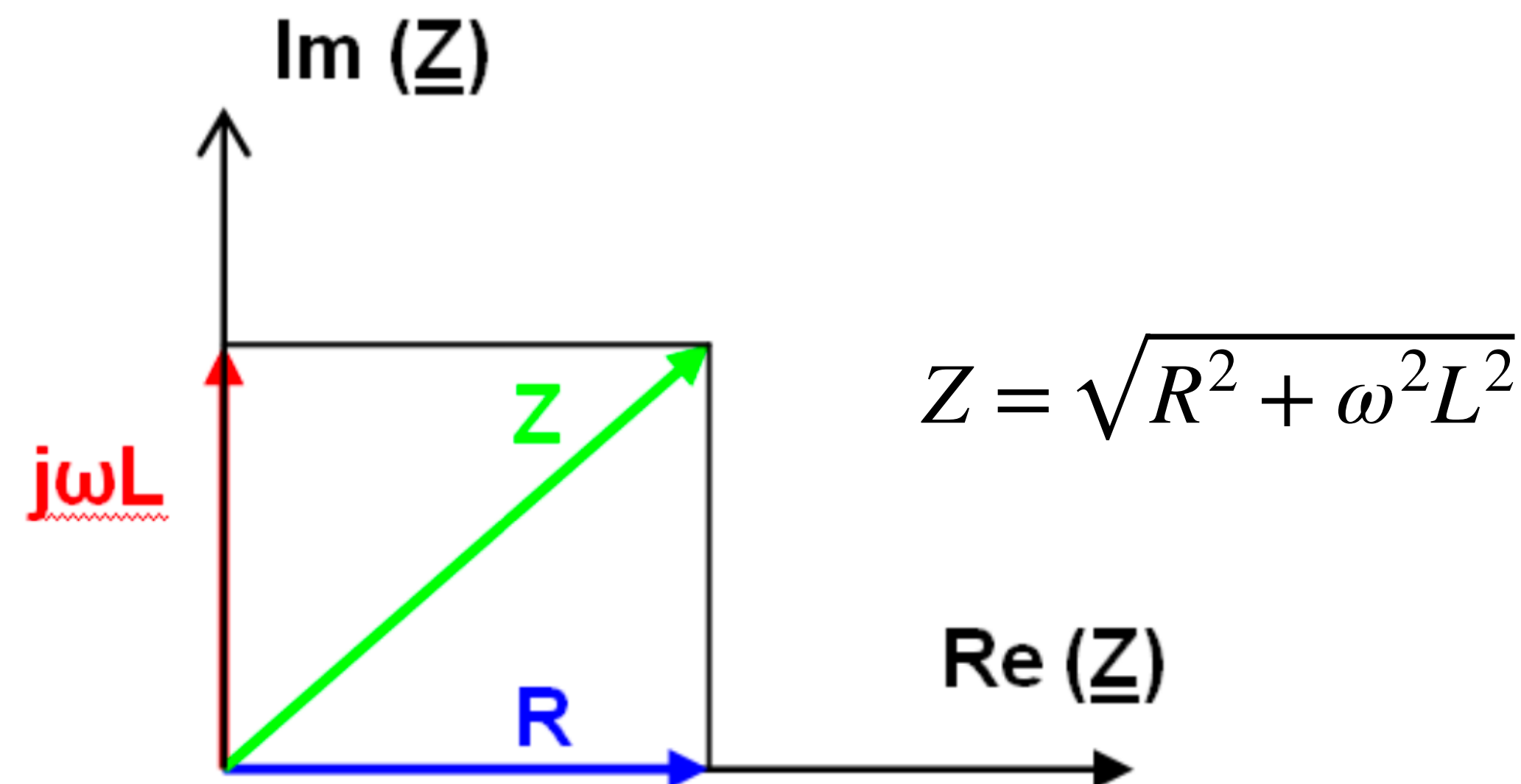

Concrete Example: Generalized Ohm's Law

Solution

$$\underline{U}_L = \underline{U}_{\text{ein}} \frac{\underline{Z}_L}{\underline{Z}_R + \underline{Z}_L} \quad \underline{U}_R = \underline{U}_{\text{ein}} \frac{\underline{Z}_R}{\underline{Z}_R + \underline{Z}_L}$$

↳ Given by generalized Ohm's Law

Solution:

$$\underline{Z} \equiv \underline{Z}_R + \underline{Z}_L = R + j\omega L \Rightarrow |\underline{Z}| = Z = \sqrt{R^2 + \omega^2 L^2}$$

Impedance / "Scheinwiderstand"

$$\Rightarrow \varphi = \arctan\left(\frac{\omega L}{R}\right)$$



$$\underline{Z} = \sqrt{R^2 + \omega^2 L^2} \cdot e^{j \arctan\left(\frac{\omega L}{R}\right)}$$

$$\Rightarrow \underline{U}_R = U_0 \cdot e^{j\omega t} \cdot \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \cdot e^{-j\varphi}$$

$$= U_0 \cdot \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \cdot e^{j(\omega t - \varphi)}$$

Info complex numbers


$$\underline{x} = a + jb$$

$$\underline{x} = x \cdot e^{j\varphi}$$

↑ real amplitude

$$x = \sqrt{a^2 + b^2}$$

$$\tan \varphi = \frac{b}{a}$$

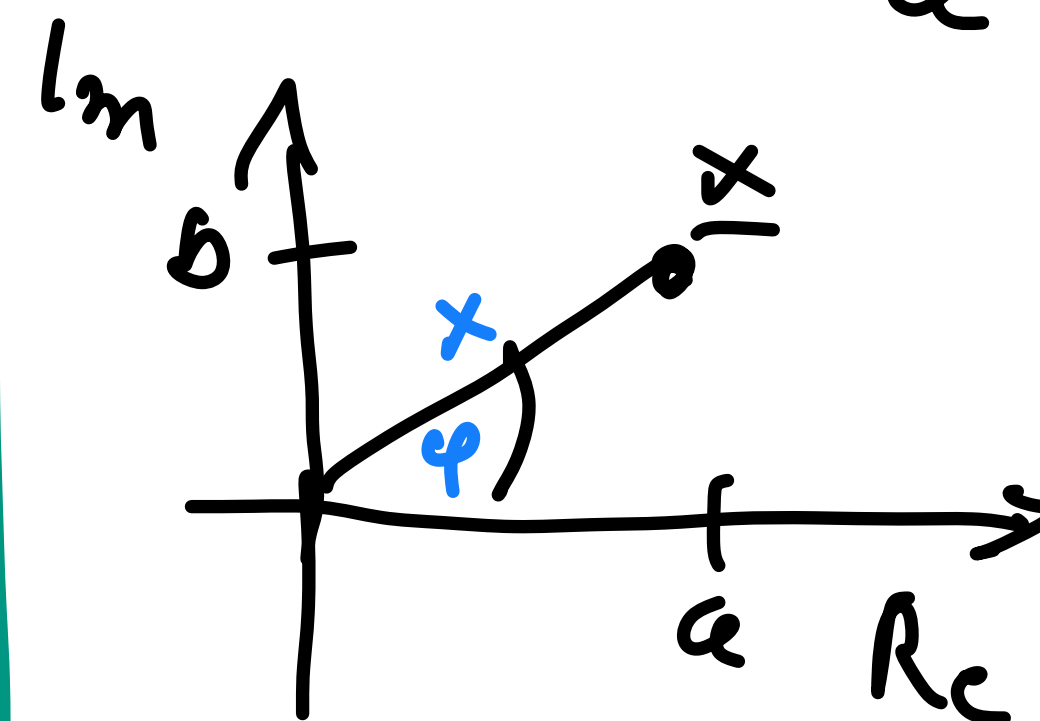

Euler's formula

$$e^{j\varphi} = \cos \varphi + j \sin \varphi$$

Concrete Example: Generalized Ohm's Law

Solution

$$\underline{U}_R = \underline{U}_0 \cdot \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \cdot e^{j(\omega t - \varphi)}$$

Real voltage given by real part of $\underline{U}_R$

$$\Rightarrow U_R = U_0 \cdot \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \cdot \cos(\omega t - \varphi) \\ = \quad \quad \quad \quad \quad \cos(\omega t - \arctan(\frac{\omega L}{R}))$$

Same for $\underline{U}_L$:

$$\underline{U}_L = \underline{U}_0 \cdot e^{j\omega t} \cdot \frac{j\omega L}{\sqrt{R^2 + \omega^2 L^2}} \cdot e^{-j\varphi} \\ = \underline{U}_0 \cdot e^{j\omega t} \cdot \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \cdot e^{-j\varphi + \frac{\pi}{2}}$$

NB: Multiplication with $j \hat{=}$ Phase shift by $\frac{\pi}{2}$ in complex plane


$$= \underline{U}_0 \cdot \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \cdot e^{j(\omega t - \varphi + \frac{\pi}{2})}$$

$$\text{results in: } U_L = U_0 \cdot \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \cdot \cos(\omega t - \arctan(\frac{\omega L}{R}) + \frac{\pi}{2})$$

$\Rightarrow U_L$ 90° ahead of U_R !


Concrete Example: Generalized Ohm's Law

Resistor and Inductor: Result

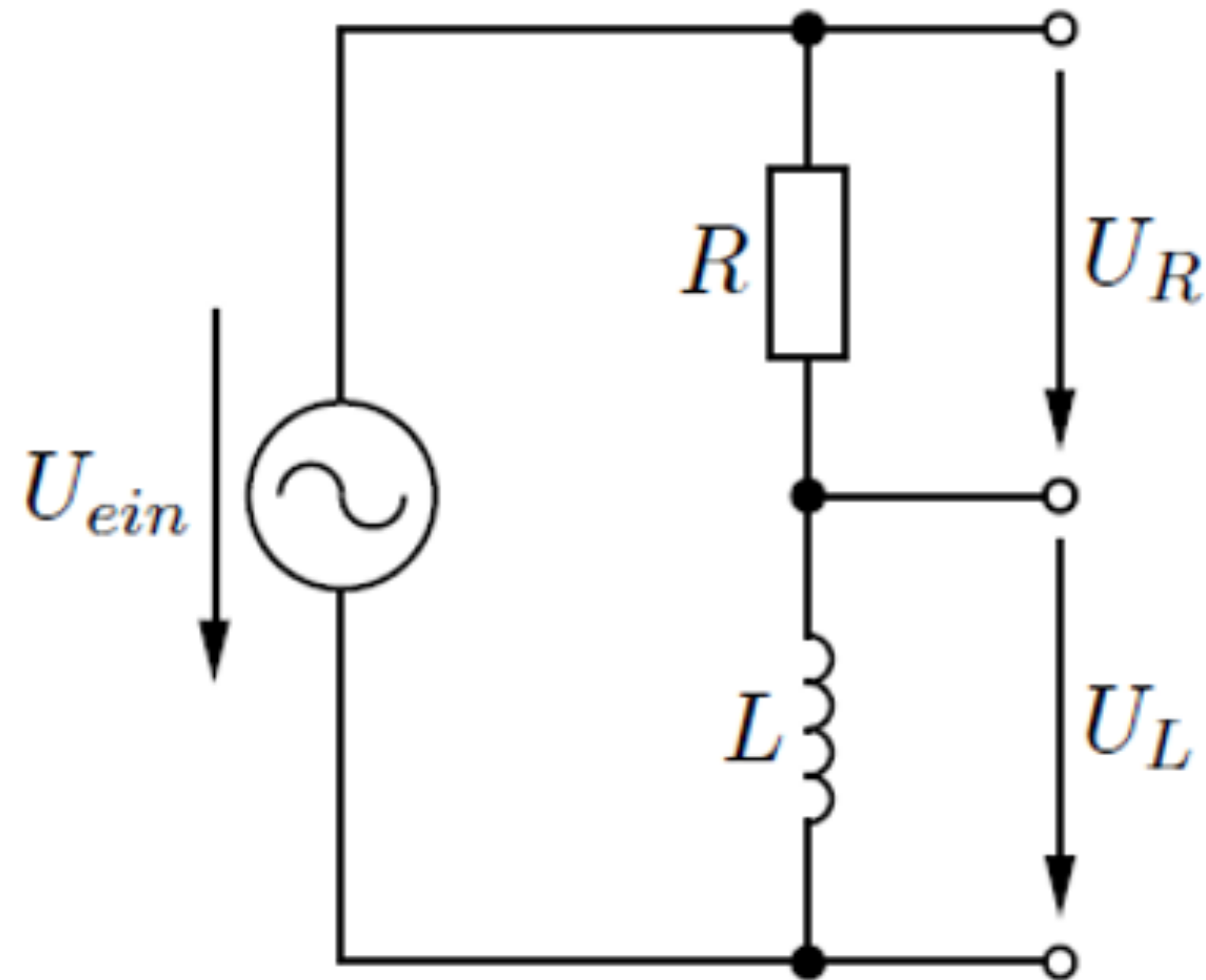

$$U_R = U_0 \frac{R}{Z} \cos \left[\omega t - \arctan \left(\frac{\omega L}{R} \right) \right]$$
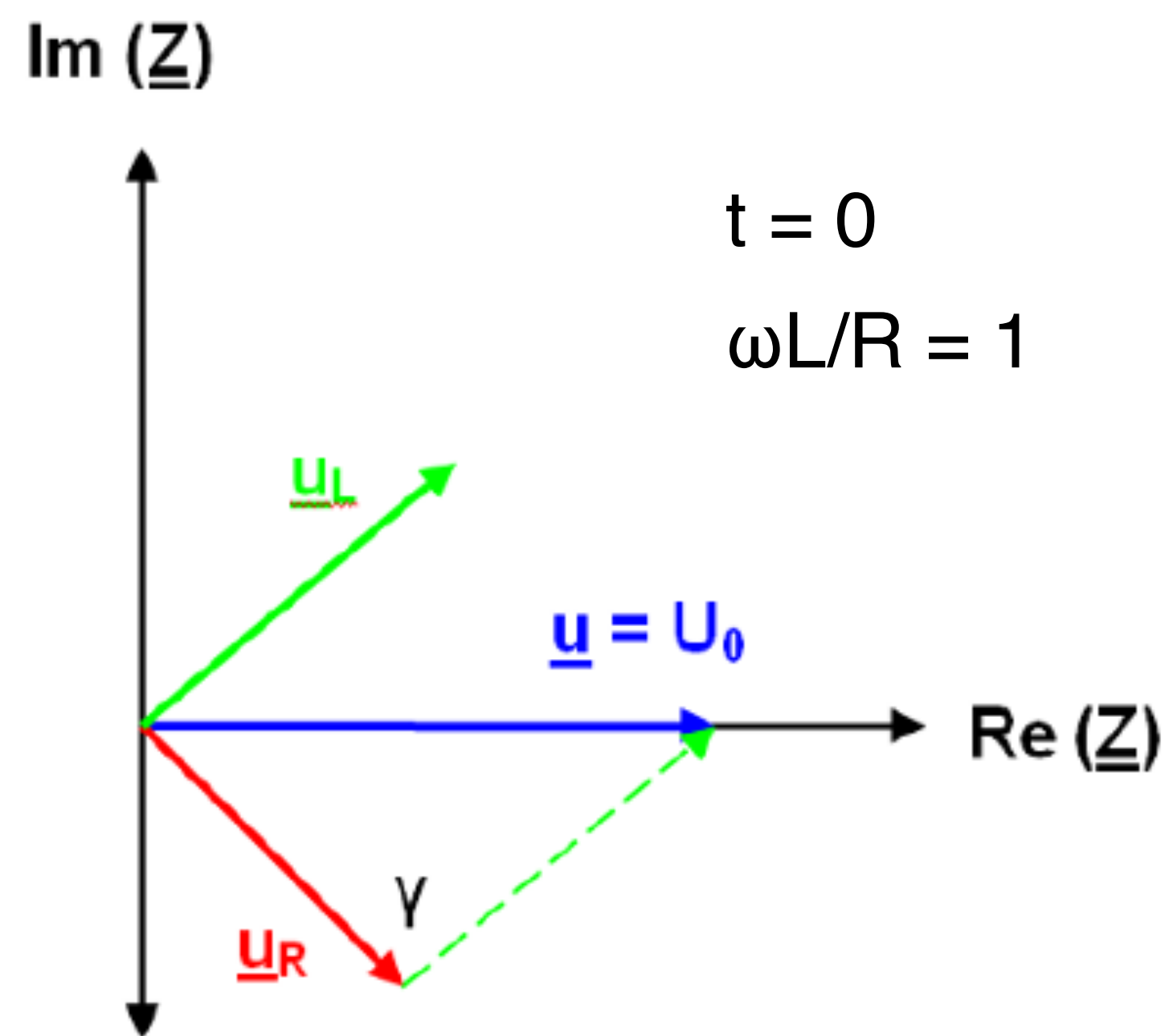
$$U_L = U_0 \omega \frac{L}{Z} \cos \left[\omega t - \arctan \left(\frac{\omega L}{R} \right) + \frac{\pi}{2} \right]$$




Why this matters: Real Components

Short overview


- Real components never behave like ideal elements:

Example resistor:

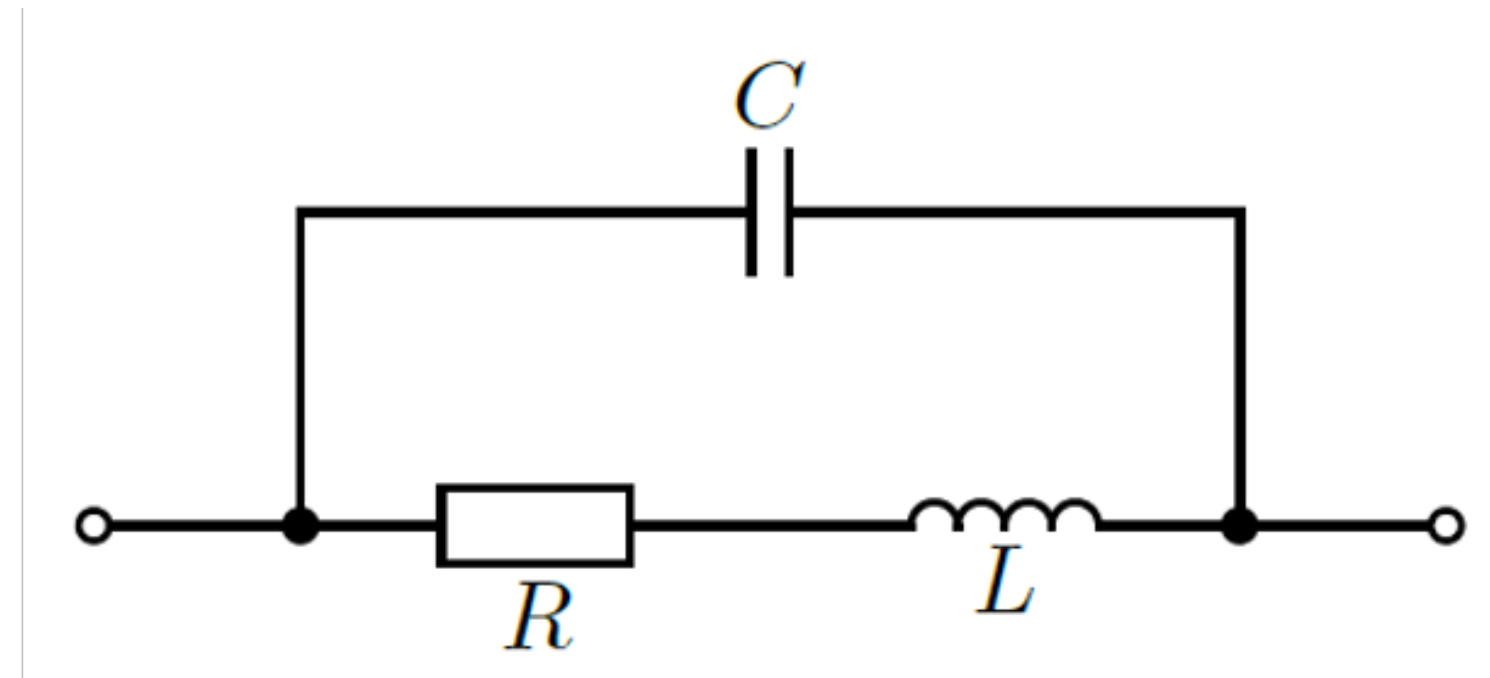

equivalent circuit
(*Ersatzschaltbild*)

Example capacitor:

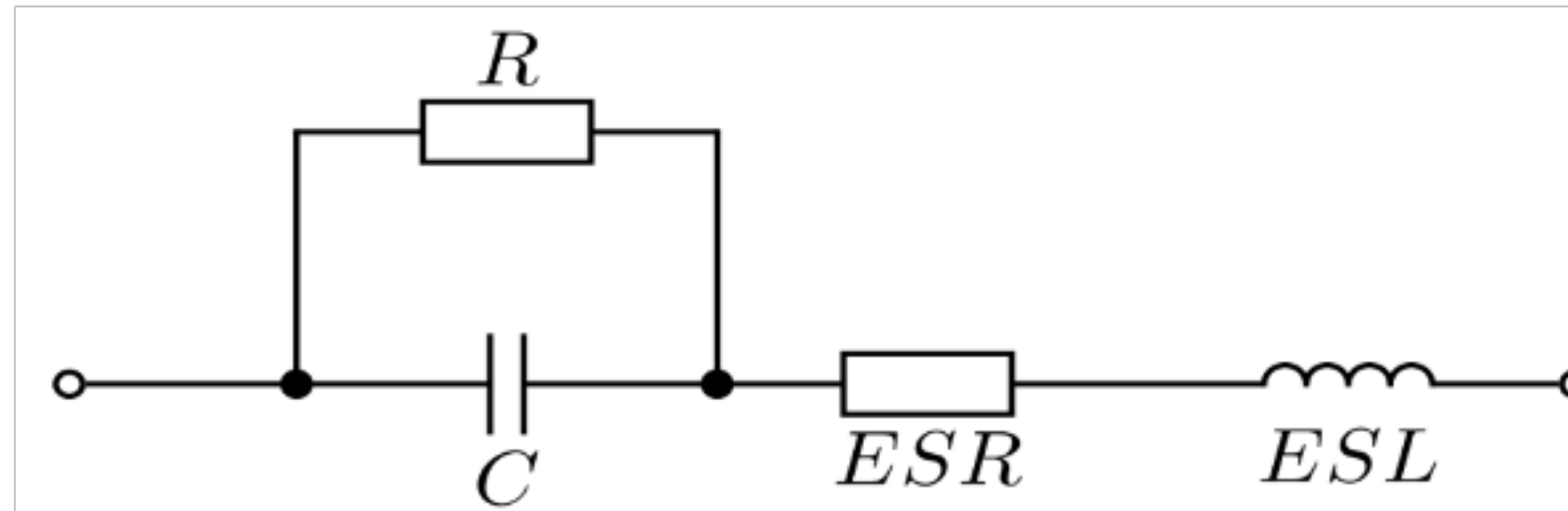

ESR: equivalent series resistance
ESL: equivalent series inductance

Consequence: frequency dependent
behavior of real electronics components
beyond naive expectation.

Example: Compensated Voltage Divider

Oscilloscope Probe


- Typical application: Oscilloscope to extend the measurement range

Practical Course!



Naive approach: 10:1 Voltage divider with two resistors:
x10 in dynamic range. (One of the resistors is the input resistor of the oscilloscope, typ. 1 M Ω or 50 Ω , depending on use case.)

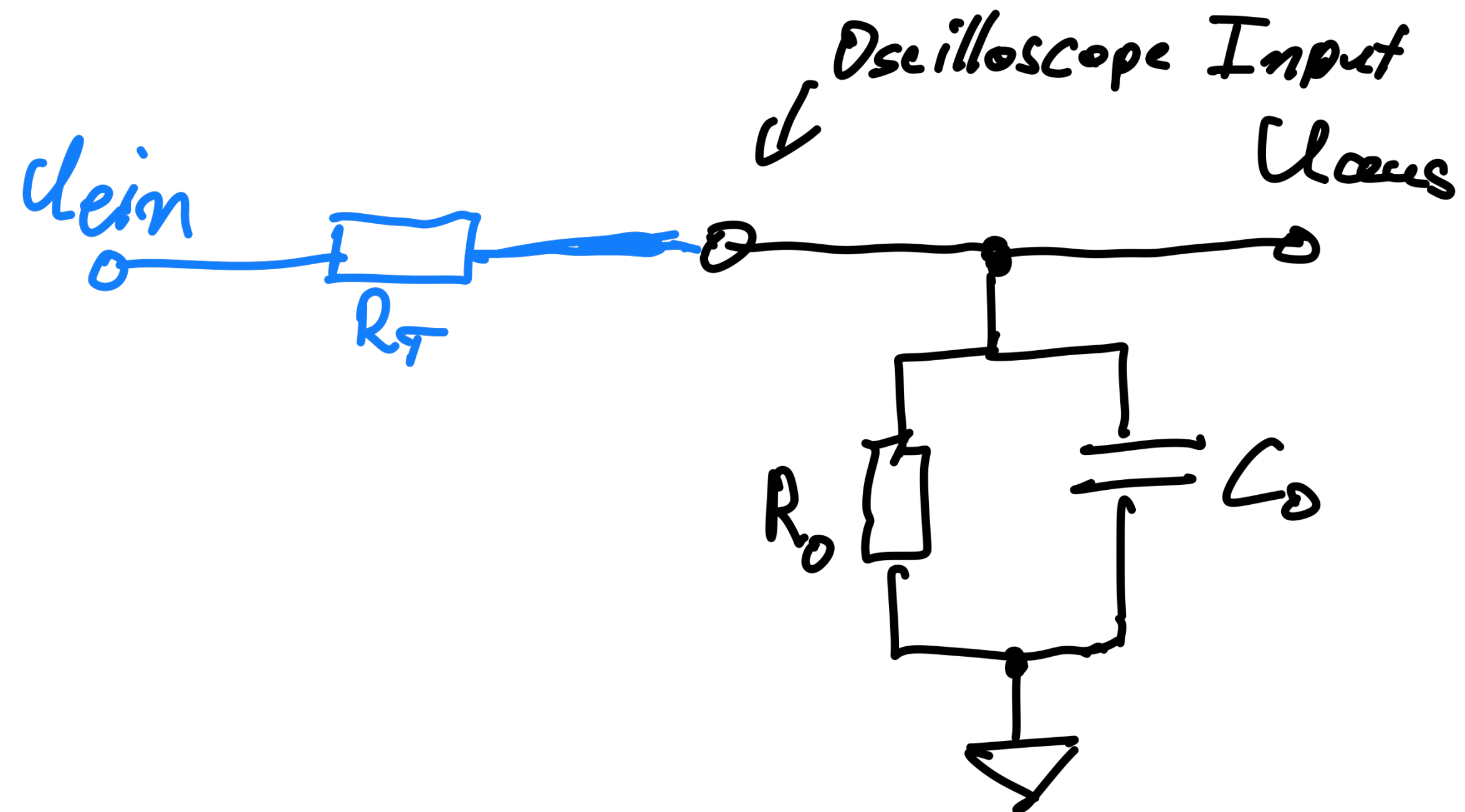But: Capacitance (typ. ~ 100 pF) results in a frequency dependence, which is modified by the additional resistor: Distortion of the signal!



Example: Compensated Voltage Divider

Oscilloscope Probe

- Typical application: Oscilloscope to extend the measurement range

Practical Course!



Die solution: Probe with a parallel circuit of resistor and capacitance, which is chosen based on the input impedance of the oscilloscope.


C_T has to be chosen such that $U_{\text{ein}}/U_{\text{aus}}$ is frequency independent.

Result:

$R_O C_O = R_T C_T$, and with that $C_T = 1/9 * C_O$

Provides 10:1 voltage division independent of frequency:



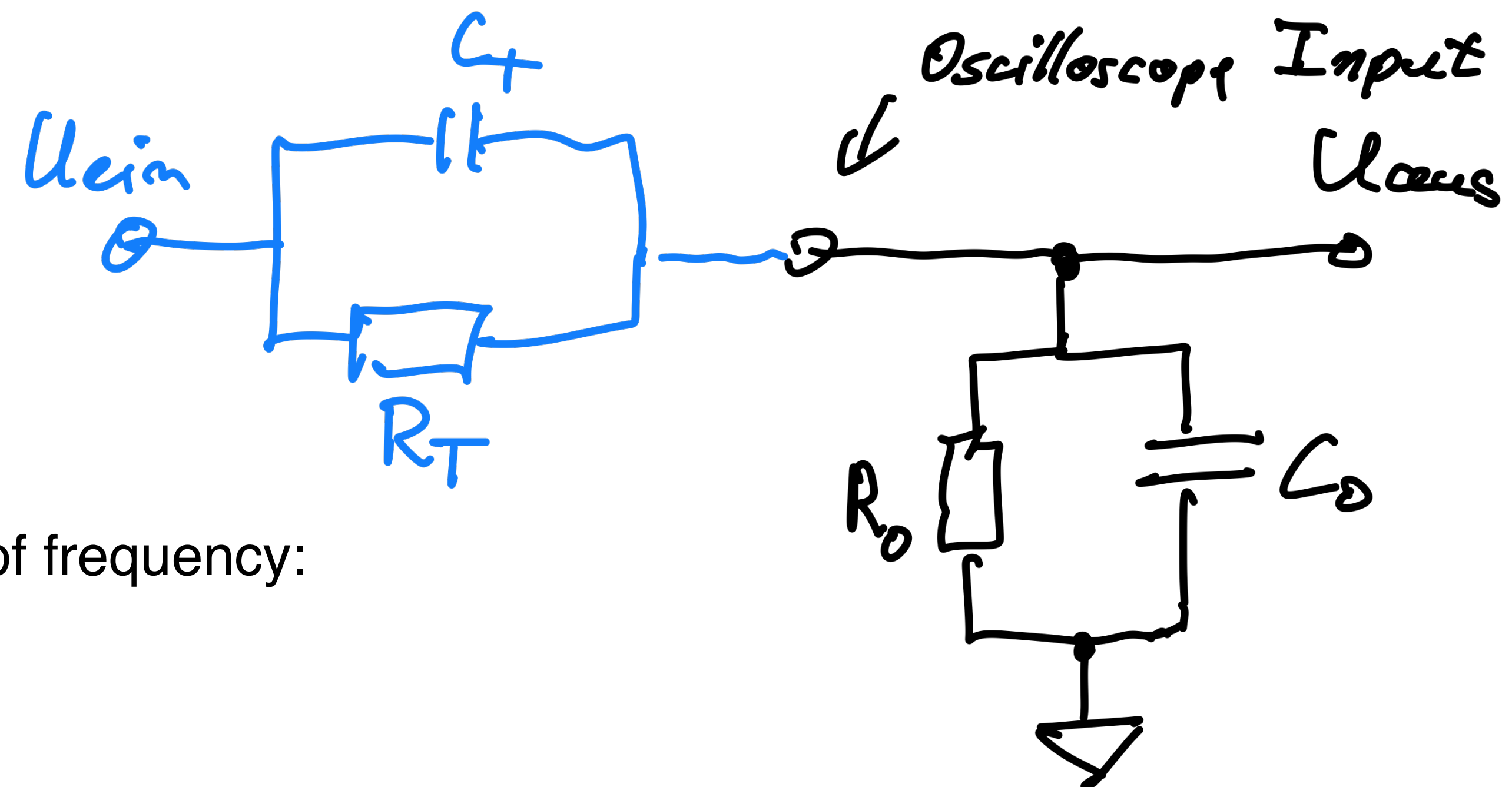
$$\frac{U_{\text{ein}}}{U_{\text{aus}}} = \frac{U_{\text{ein}}}{U_{\text{aus}}} = 1 + \frac{R_T}{R_O}$$



Real Components: Resistors

Some more details

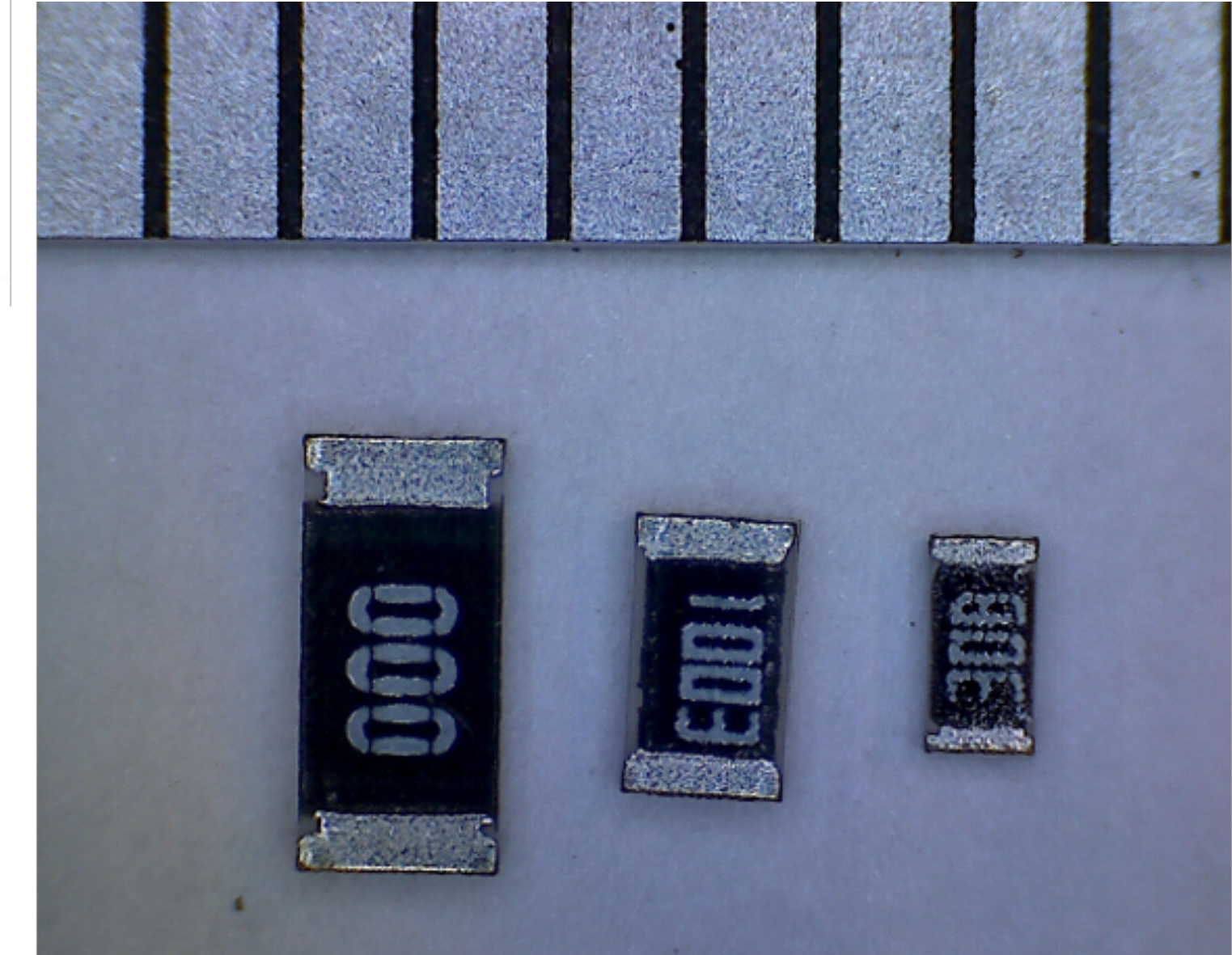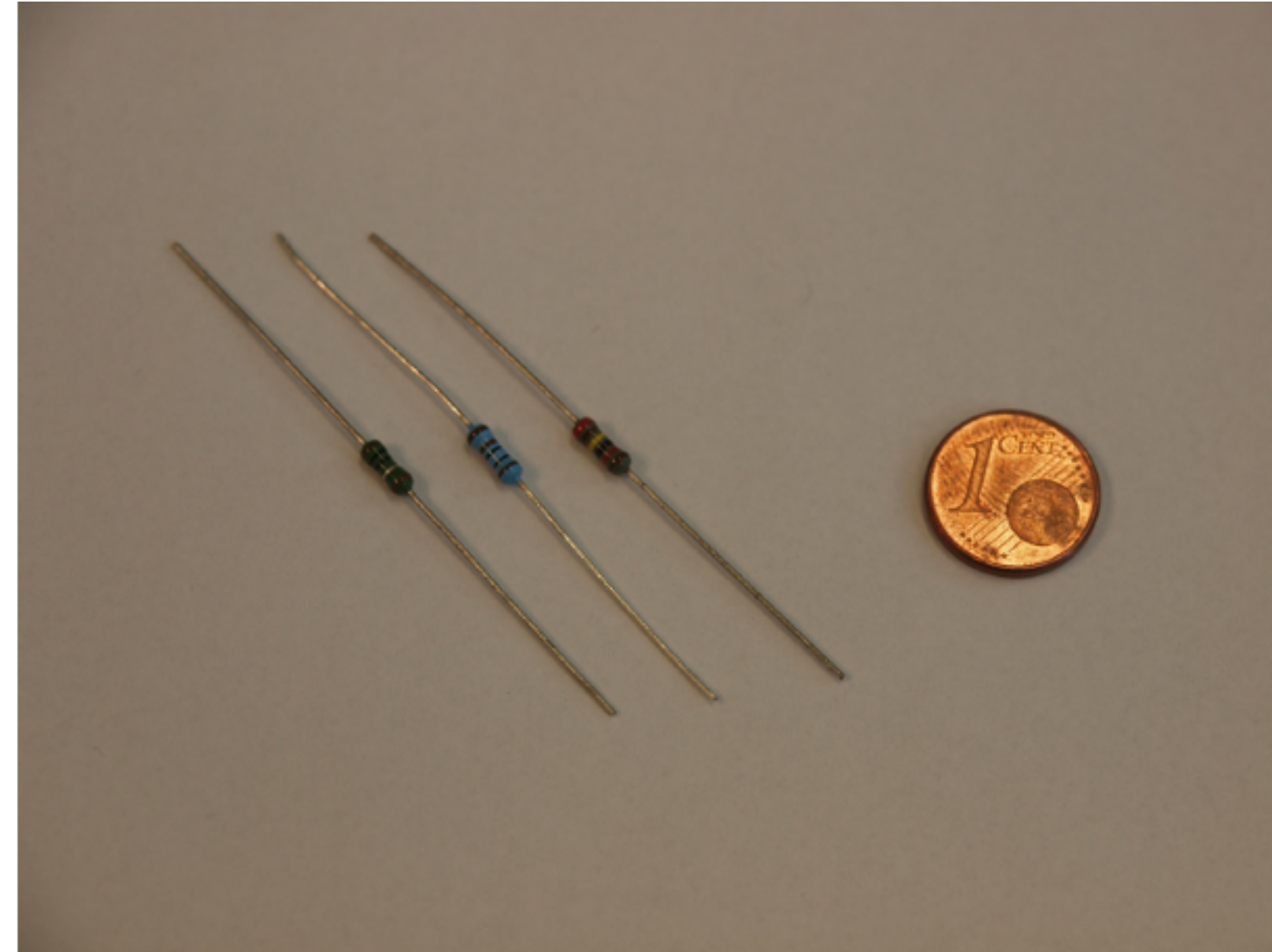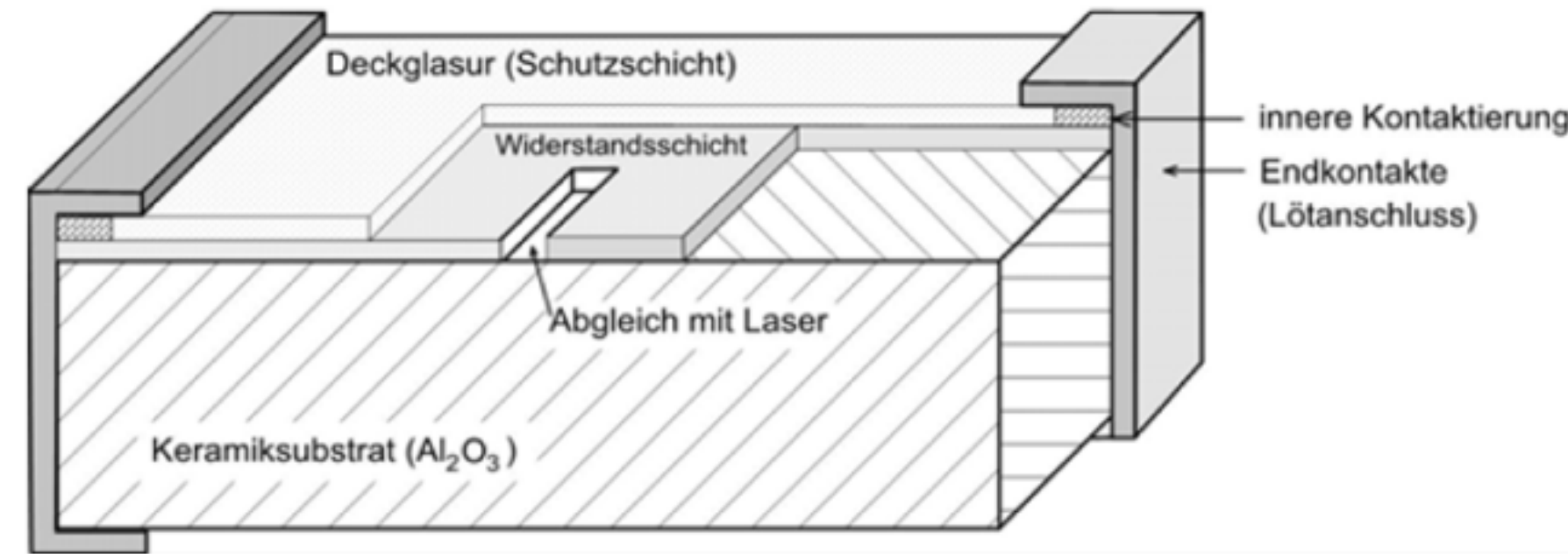- Typical parameters to consider:
 - Maximum ratings
 - Precision
 - Temperature stability
 - Types and sizes
 - HF properties
 - Costs




SMD components


“**s**urface **m**ounted **d**evice”

Real Components: Resistors

Some more details

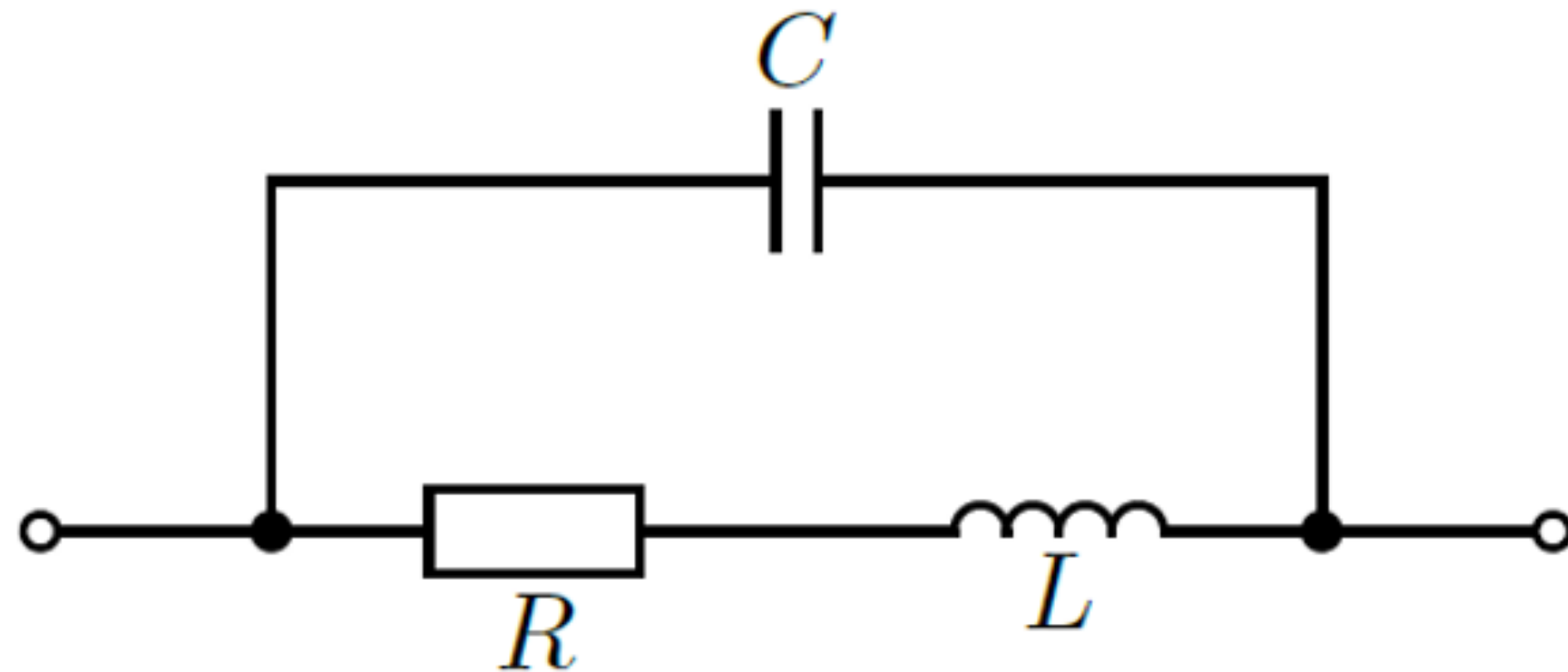

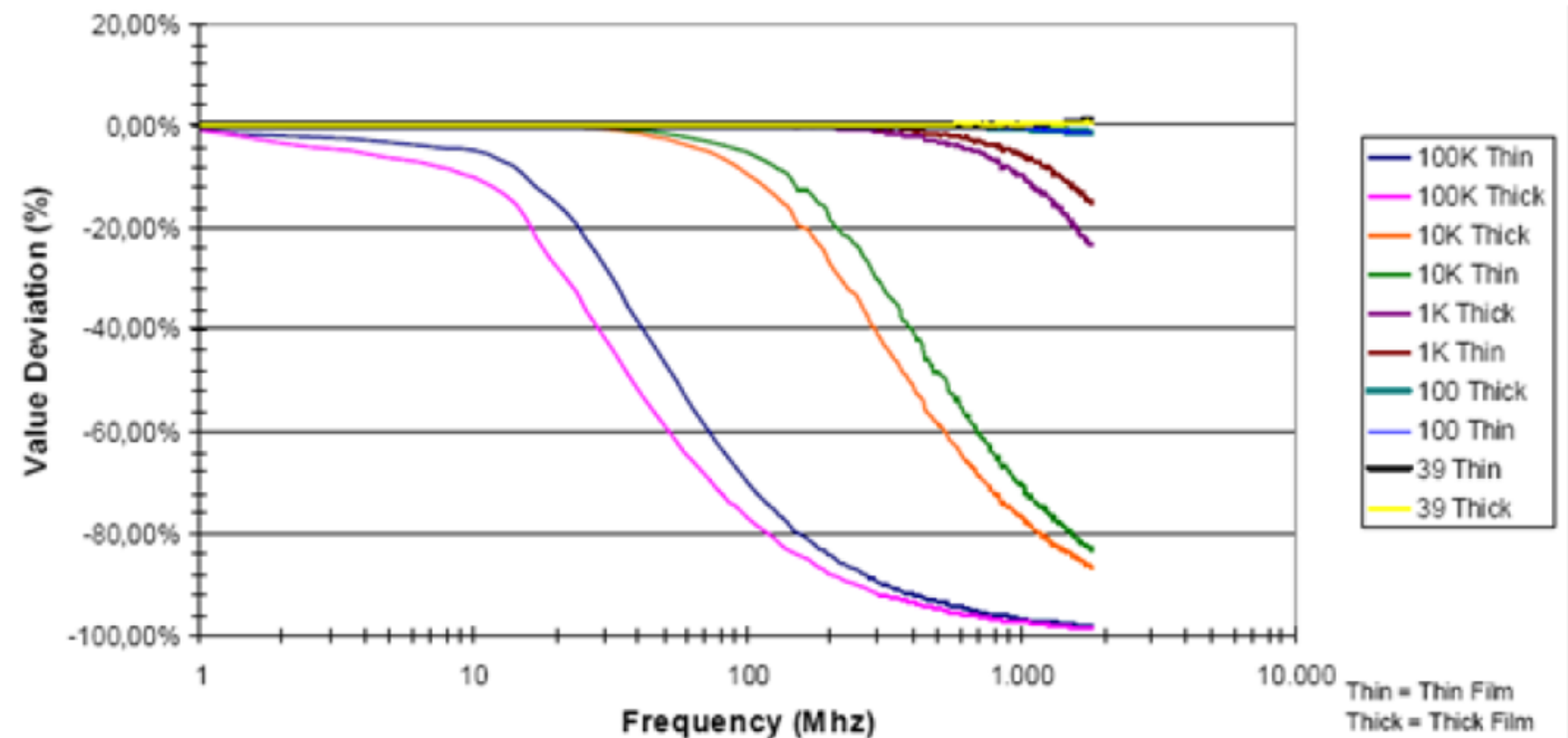
frequency behavior -
some random examples



Real Components: Capacitors

Some more details

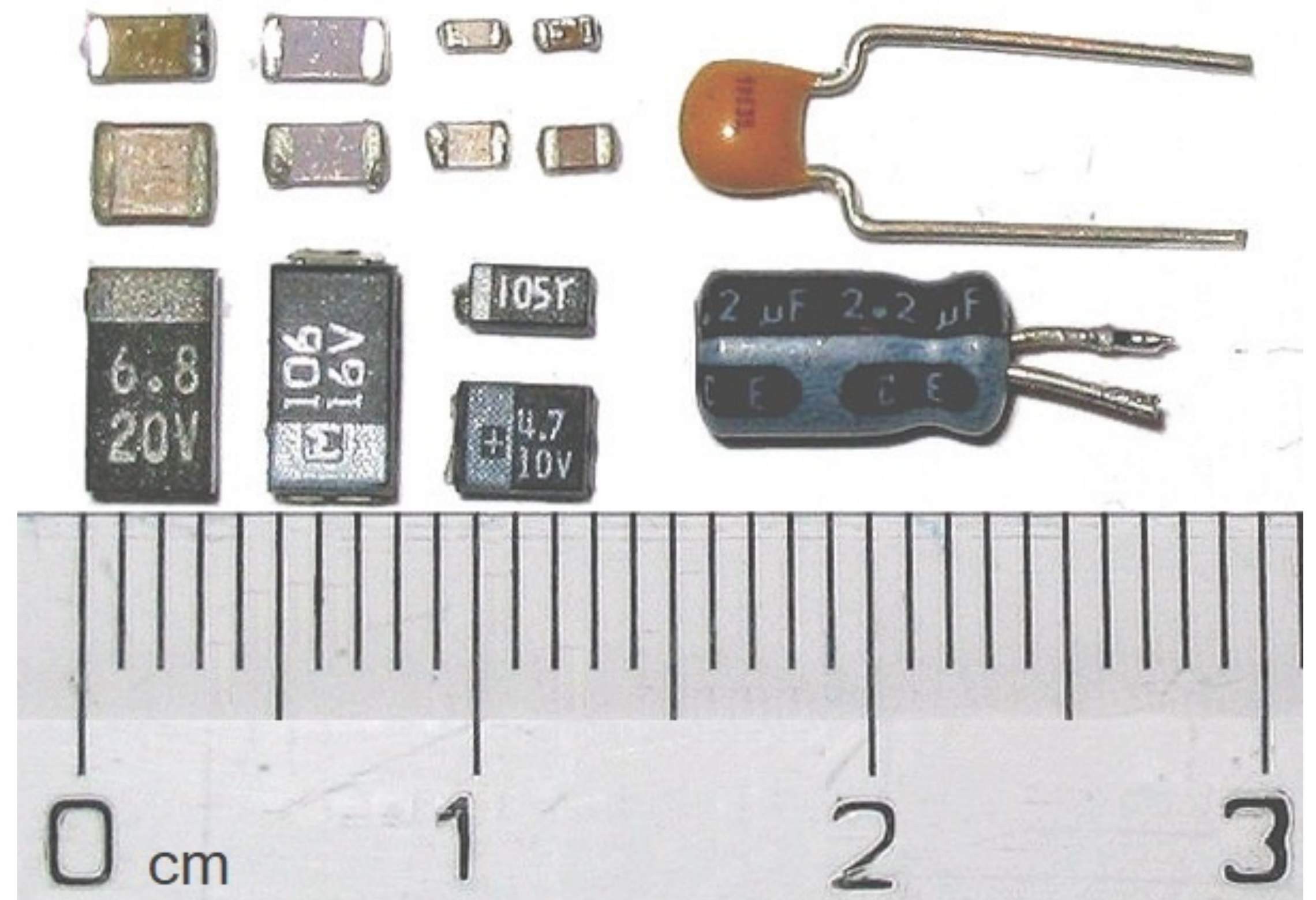
- Different types and form factors
 - Different dielectrics in use - ceramics, liquid,... with dielectric constants ranging typically from a few 10 to a few 100




Real Components: Capacitors

Some more details

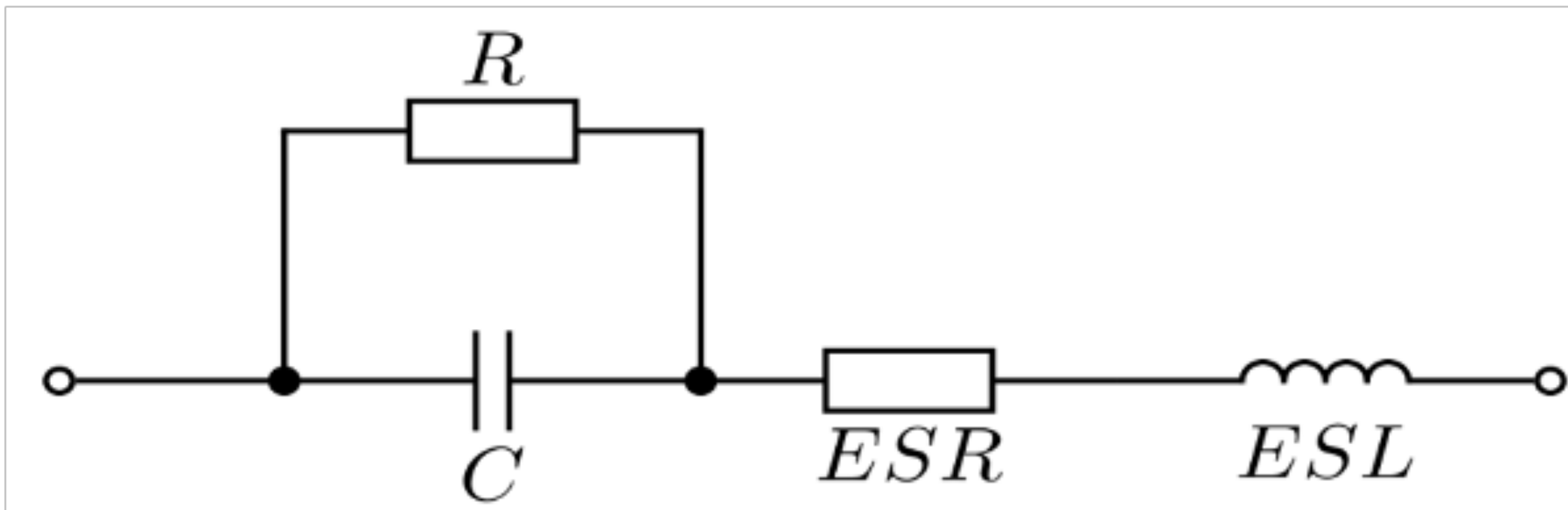Frequency behavior - can be understood via equivalent circuit



- For small ω , the capacitive term $1/\omega C$ dominates.
- For large ω , the term ωL dominates.
- Around the natural frequency behavior primarily resistive ($\omega_0 = 1 / \text{Sqrt}(ESL C)$).
- The frequency response of a capacitor is often more important than the exact value of its capacitance.

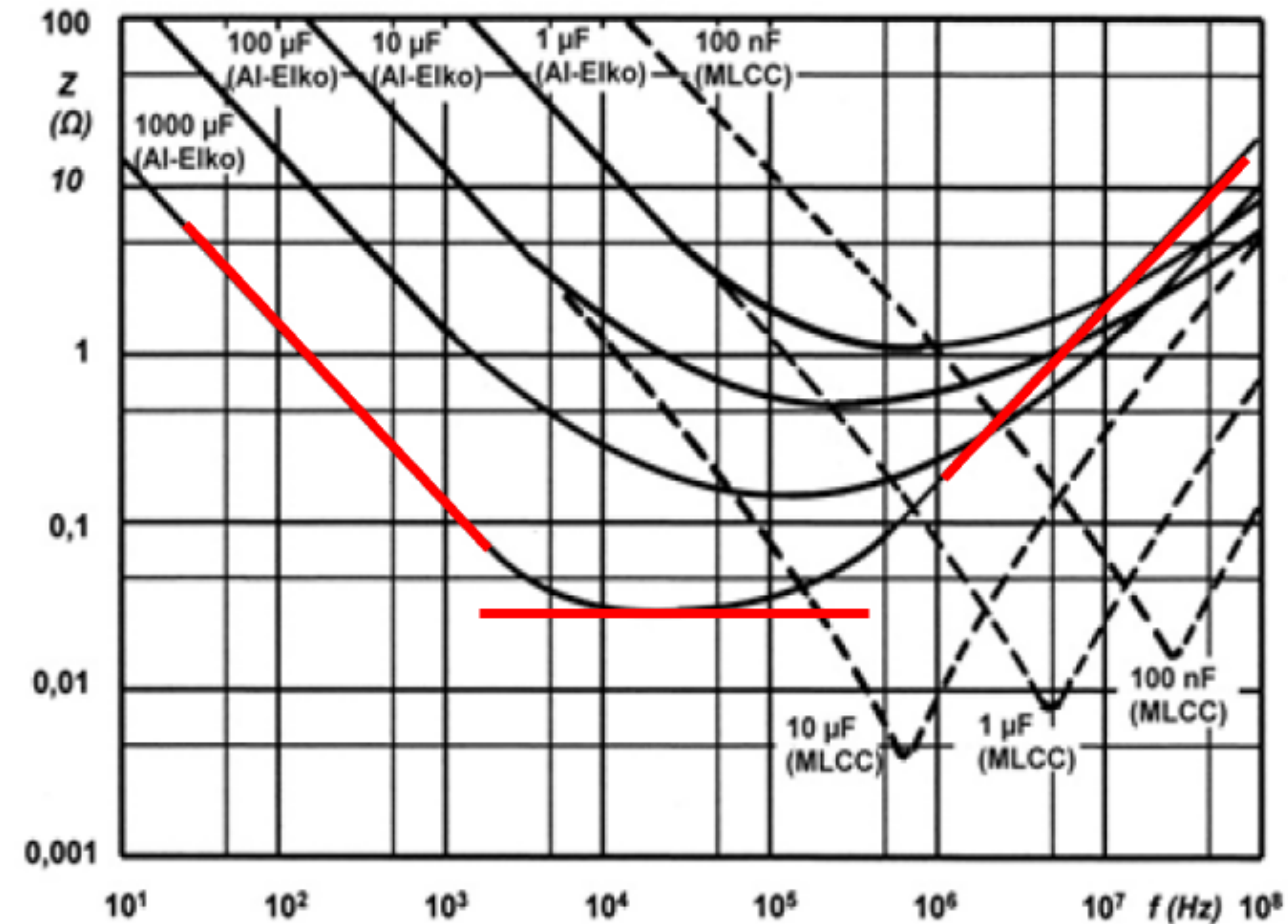





Chapter 2


Filters

In: Circuits with R , C , L

High- and Low Pass Filters

Reminder / Summary

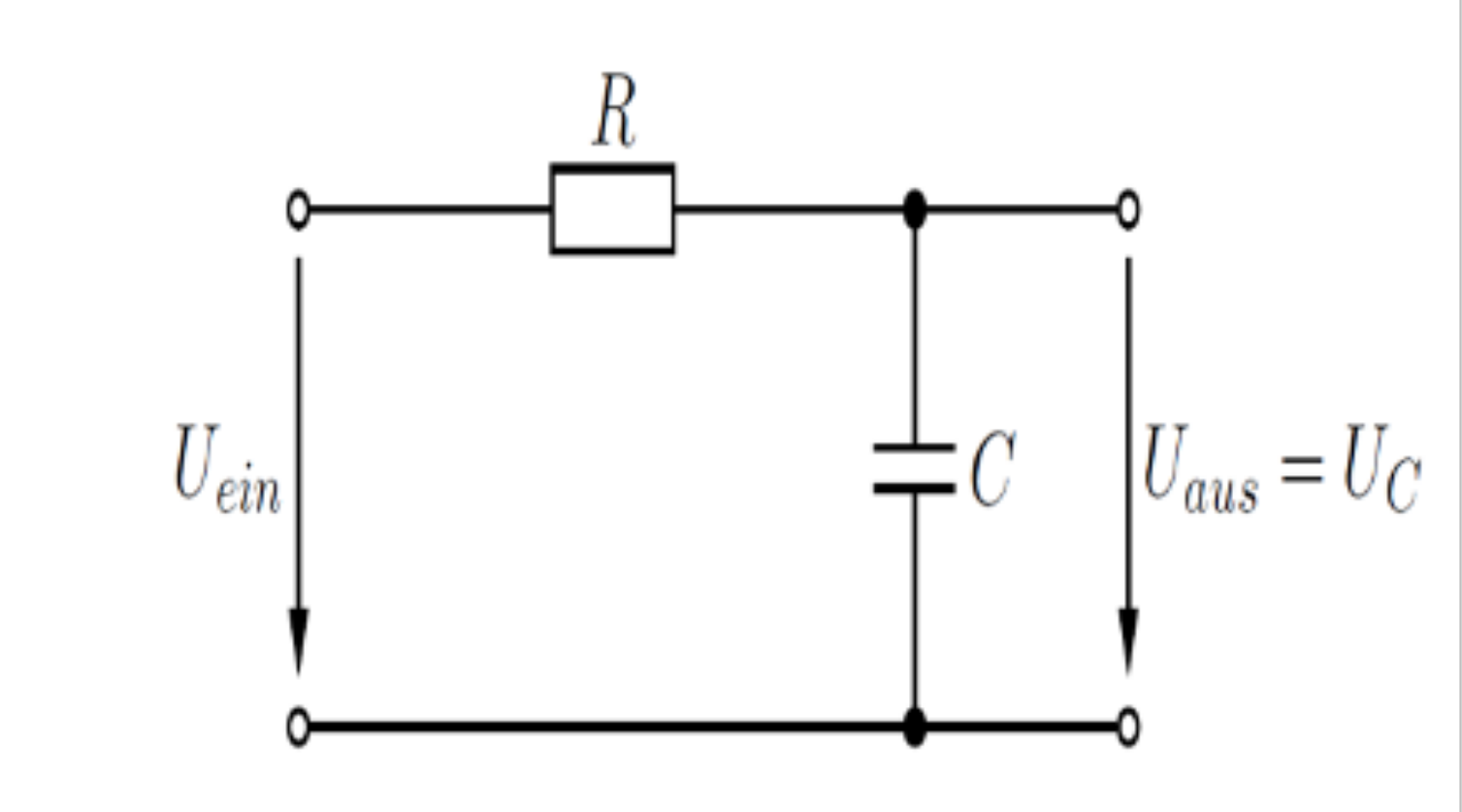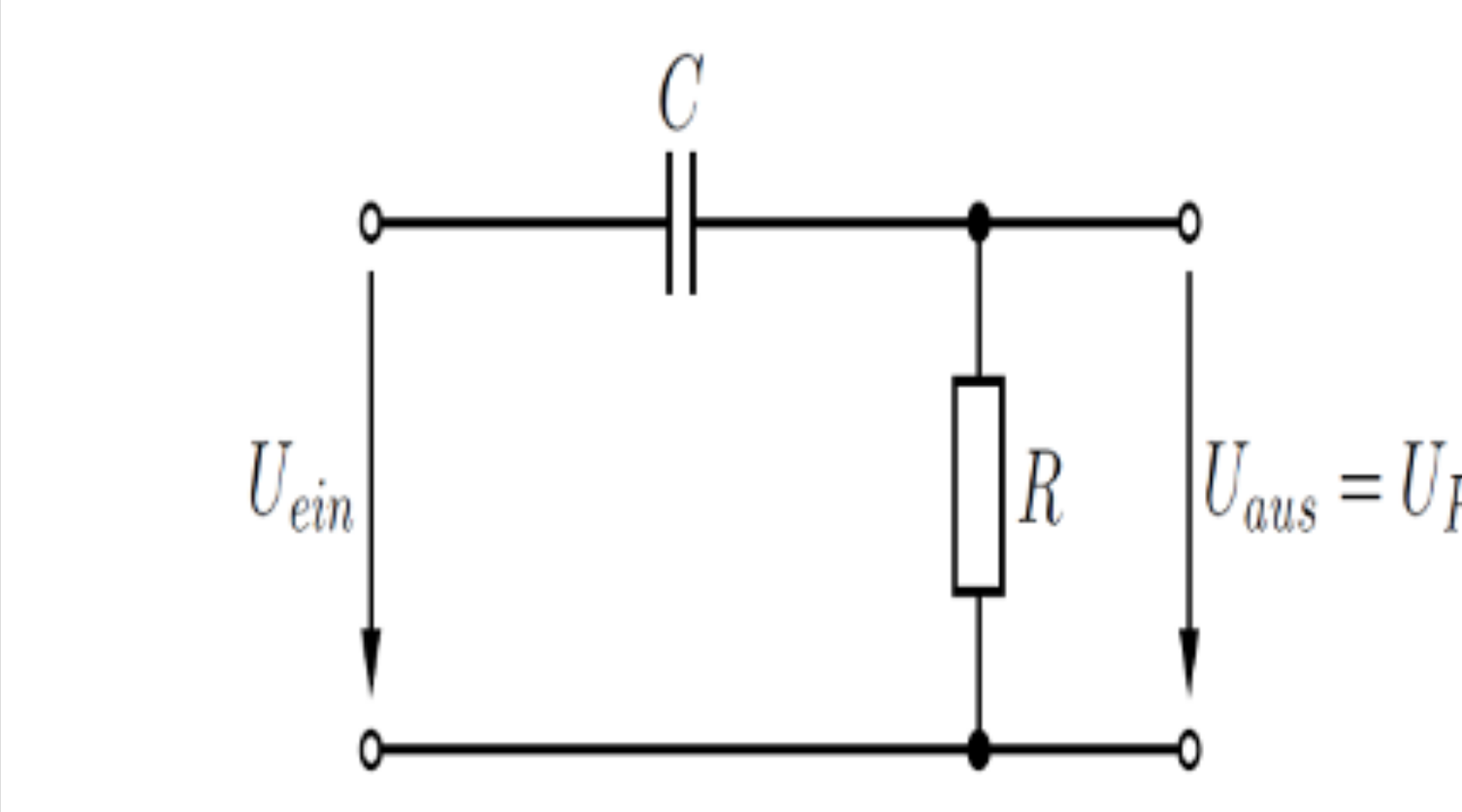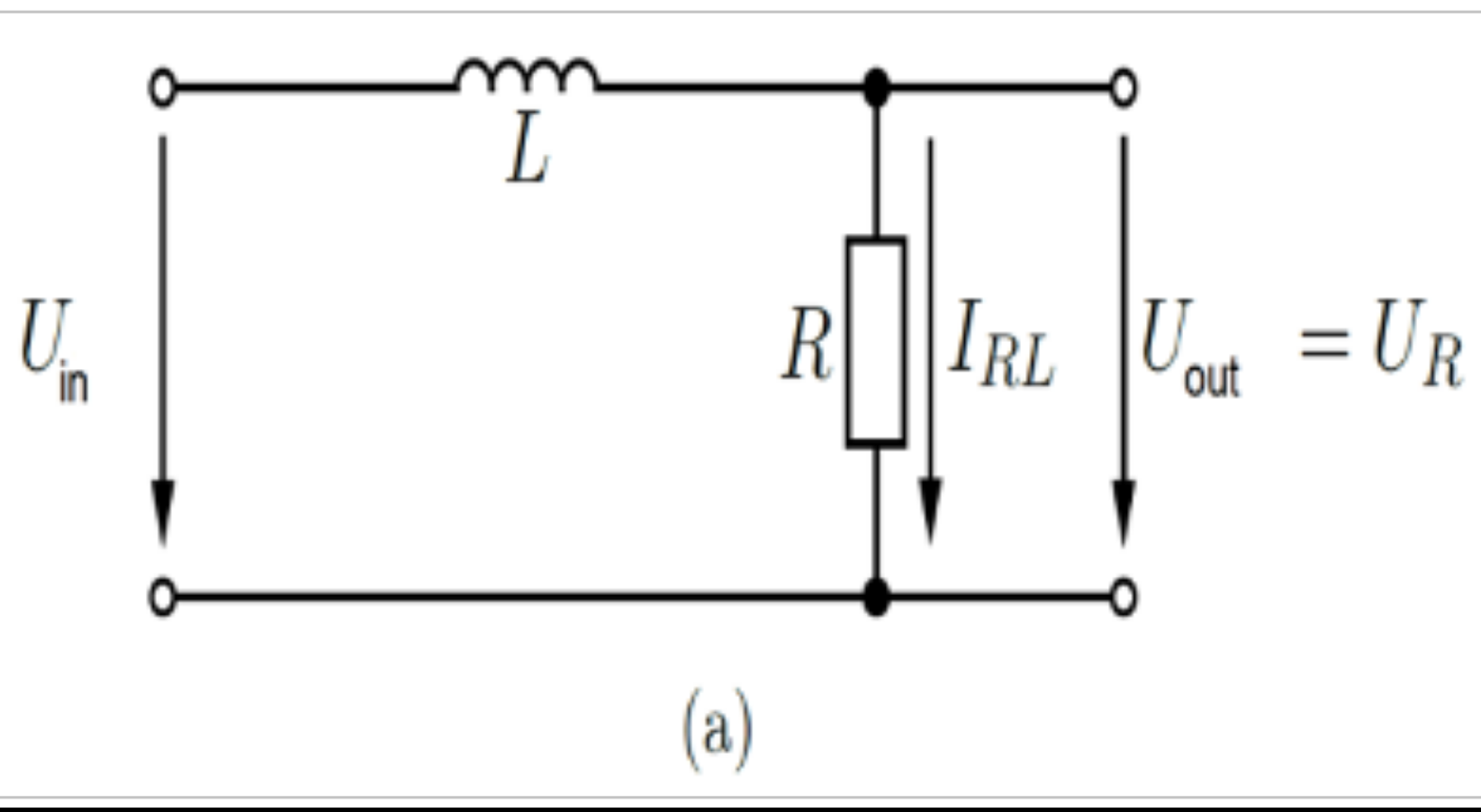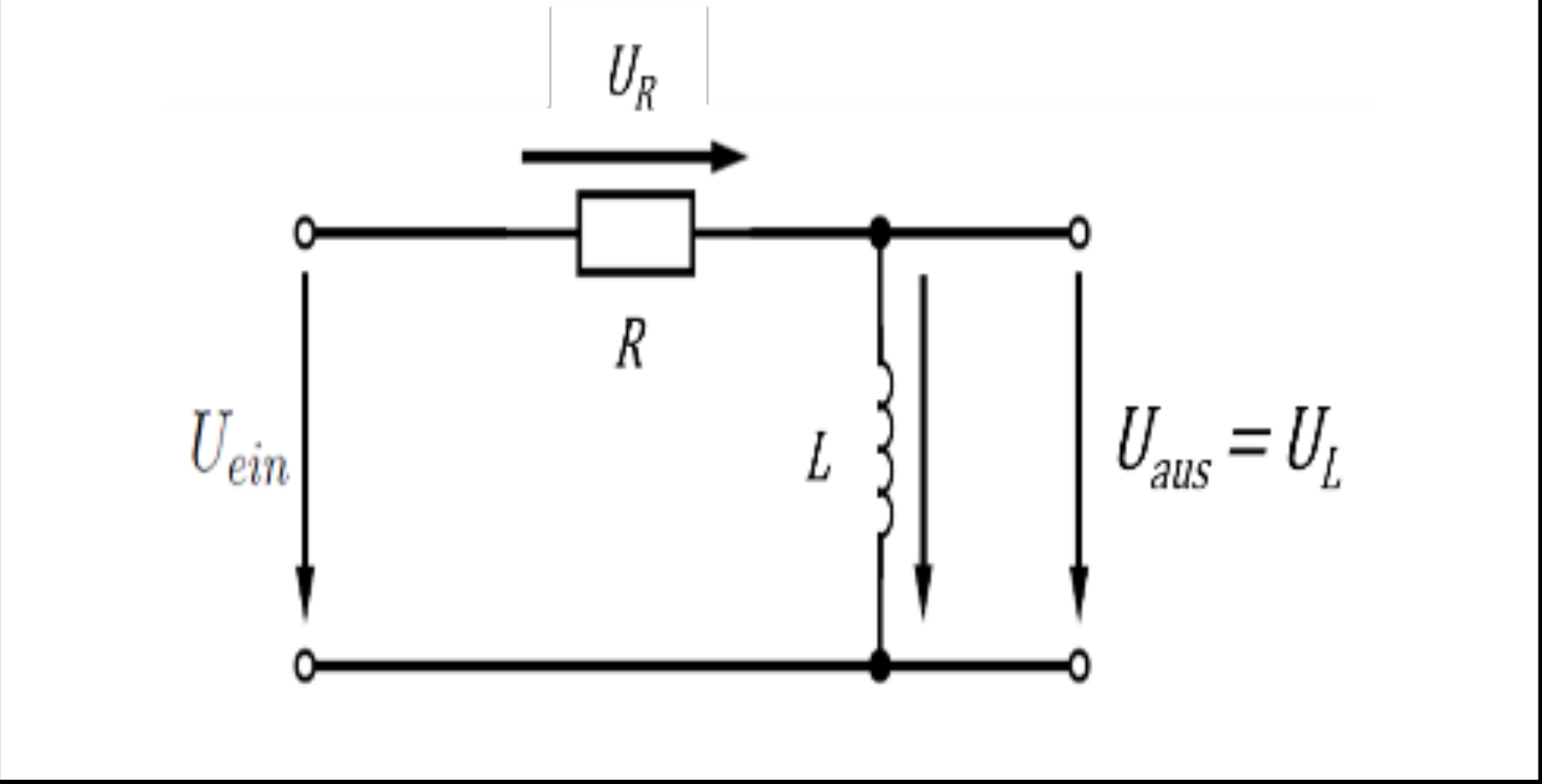Type	low pass	high pass
RC	 Circuit diagram of an RC low pass filter. The input voltage is U_{ein}. A resistor R is in series with the input, followed by a capacitor C connected to ground. The output voltage is $U_{aus} = U_C$.	 Circuit diagram of an RC high pass filter. The input voltage is U_{ein}. A capacitor C is in series with the input, followed by a resistor R connected to ground. The output voltage is $U_{aus} = U_R$.
RL	 Circuit diagram of an RL low pass filter. The input voltage is U_{in}. An inductor L is in series with the input, followed by a resistor R connected to ground. The output voltage is $U_{out} = U_R$. The current through the resistor is I_{RL}. The diagram is labeled (a).	 Circuit diagram of an RL high pass filter. The input voltage is U_{ein}. A resistor R is in series with the input, followed by an inductor L connected to ground. The output voltage is $U_{aus} = U_L$. The voltage across the resistor is U_R.

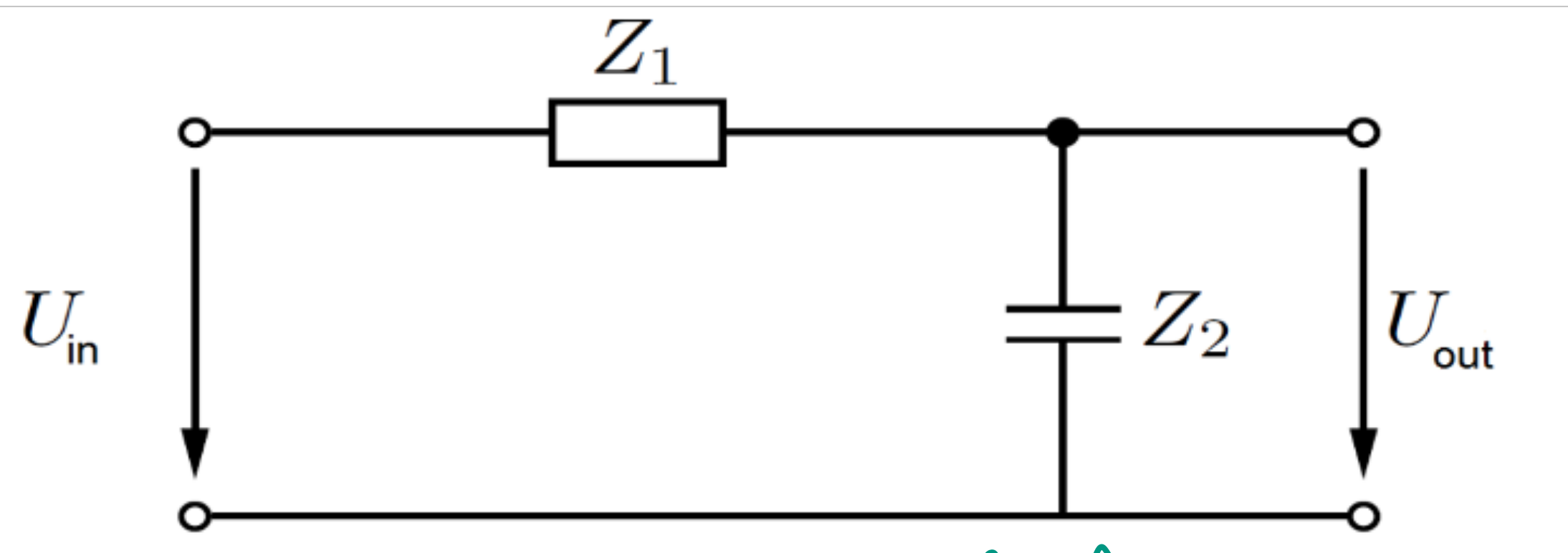

Integrator / low pass filter

$$\underline{U}_{out} = \underline{U}_{in} \frac{\underline{Z}_2}{\underline{Z}_1 + \underline{Z}_2} \quad (\text{voltage divider!})$$

complex transfer function

$$\frac{\underline{U}_{out}}{\underline{U}_{in}} = \underline{Z} = \frac{\underline{Z}_2}{\underline{Z}_1 + \underline{Z}_2} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC} = \frac{1 - j\omega RC}{1 + (\omega RC)^2}$$

with $\underline{Z} = Z e^{j\varphi}$:


$$Z = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad \text{and} \quad \tan \varphi = \frac{\text{Im}(\underline{Z})}{\text{Re}(\underline{Z})} = -\omega RC$$

$$Z \approx 1 \text{ for } \omega \approx 0$$

$$\text{and } Z \approx 0 \text{ for } \omega \gg 1/(RC)$$

Low Pass

Impact on Signals

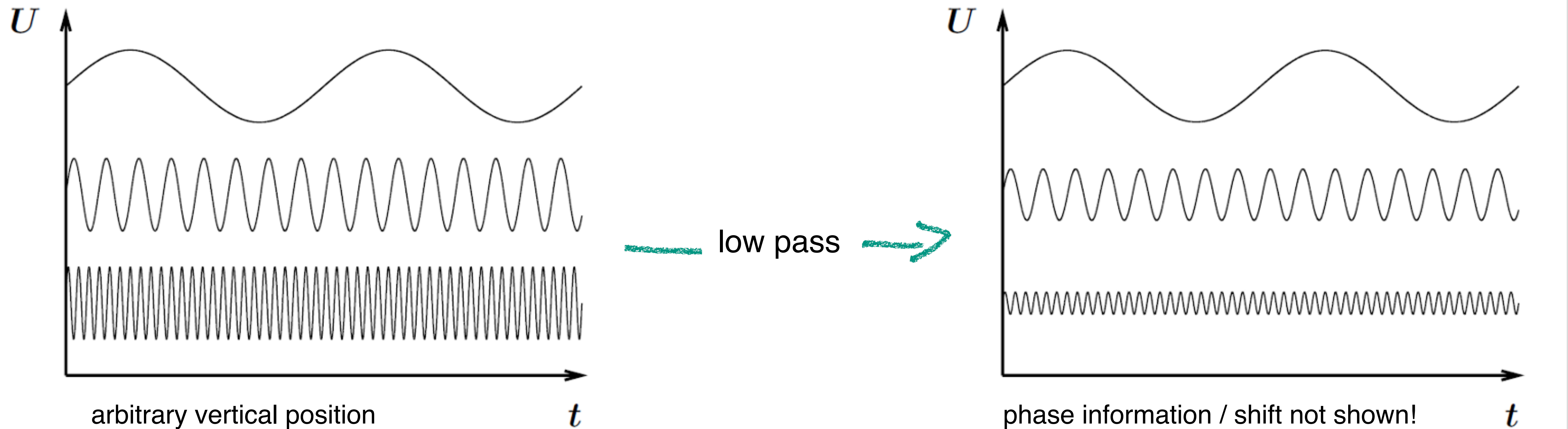


- Low frequency signals pass unchanged
- High frequency signals are damped
- For high frequencies the output signal is delayed in time with respect to the input signal

Low Pass

Frequency Dependence

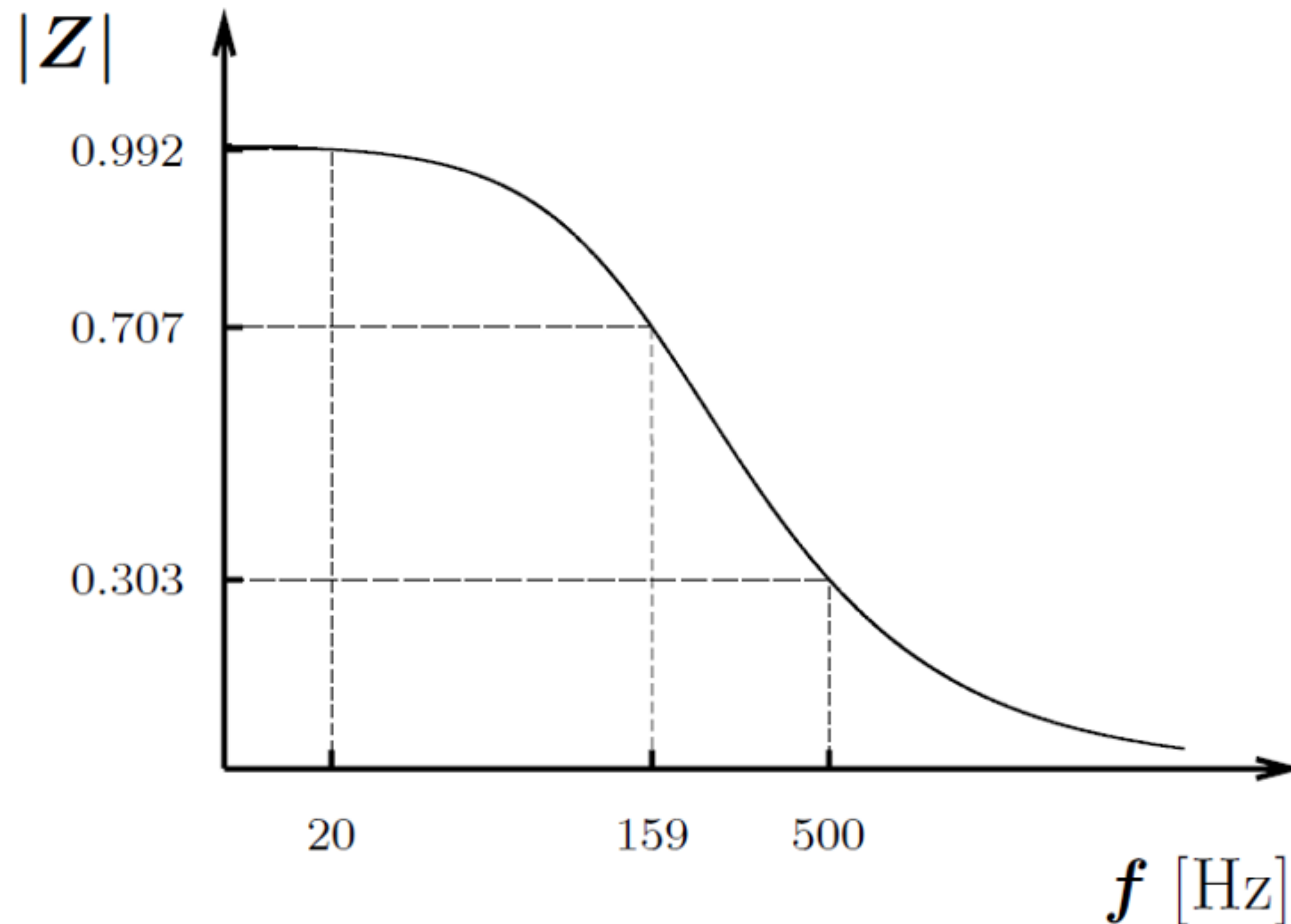- Amplitude of output signal depends on frequency.
- Phase depends on frequency.
- The frequency of input and output signal is identical.



$$Z = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

Brief Excursion: Decibel

Characterizing Filter Properties

Definitions: $10 \log \frac{P_{in}}{P_{out}}$ for power $20 \log \frac{U_{in}}{U_{out}}$ or $20 \log \frac{I_{in}}{I_{out}}$ for current / voltage

dB	voltage ratio $20 \log \frac{U_{aus}}{U_{ein}}$	power ratio $10 \log \frac{P_{aus}}{P_{ein}}$
100	10^5	10^{10}
40	100	10^4
20	10	100
6,02	2	4
3,01	$\sqrt{2}$	2
0	1	1
- 3,01	$\frac{1}{\sqrt{2}}$	$\frac{1}{2}$
- 6,02	$\frac{1}{2}$	$\frac{1}{4}$
- 20	0,1	10^{-2}
- 40	0,01	10^{-4}
- 100	10^{-5}	10^{-10}

NB: log = base 10 logarithm

Reminder:
 $\log(ab) = \log(a) + \log(b)$:
dB values can be added!

Additional terms:
dBm: dB relative to 1 mW: $10 \log \frac{P[W]}{1 \text{ mW}}$

dBmA: dB relative to 1 mA: $20 \log \frac{I[A]}{1 \text{ mA}}$

Bode Plot: Introduction, Low Pass


Bodediagramm

- A commonly used representation of the transfer function (*komplexe Übertragungsfunktion*) $Z e^{j\varphi}$

- Two plots:

- Amplitude of transfer function Z in dB vs $\log(f)$
- Phase ϕ vs $\log(f)$

$$f = \frac{\omega}{2\pi}$$

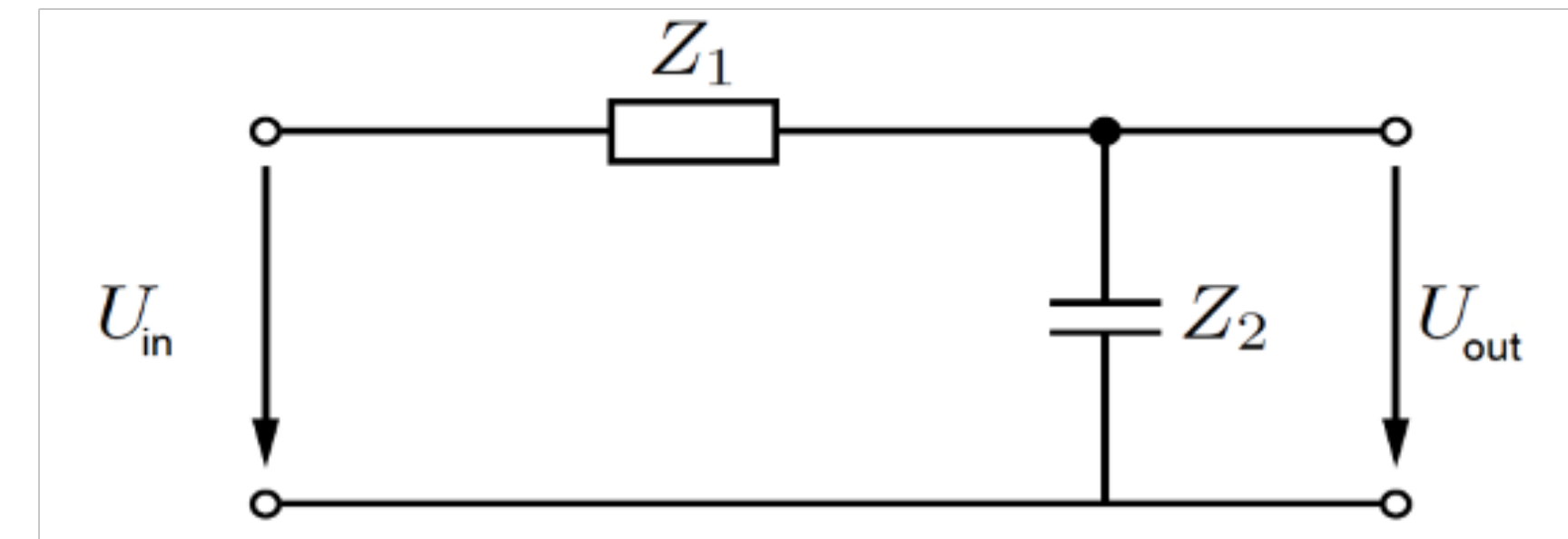



$$Z = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\tan \varphi = -\omega RC$$

here:


$$R = 10 \text{ k}\Omega$$

$$C = 100 \text{ nF}$$

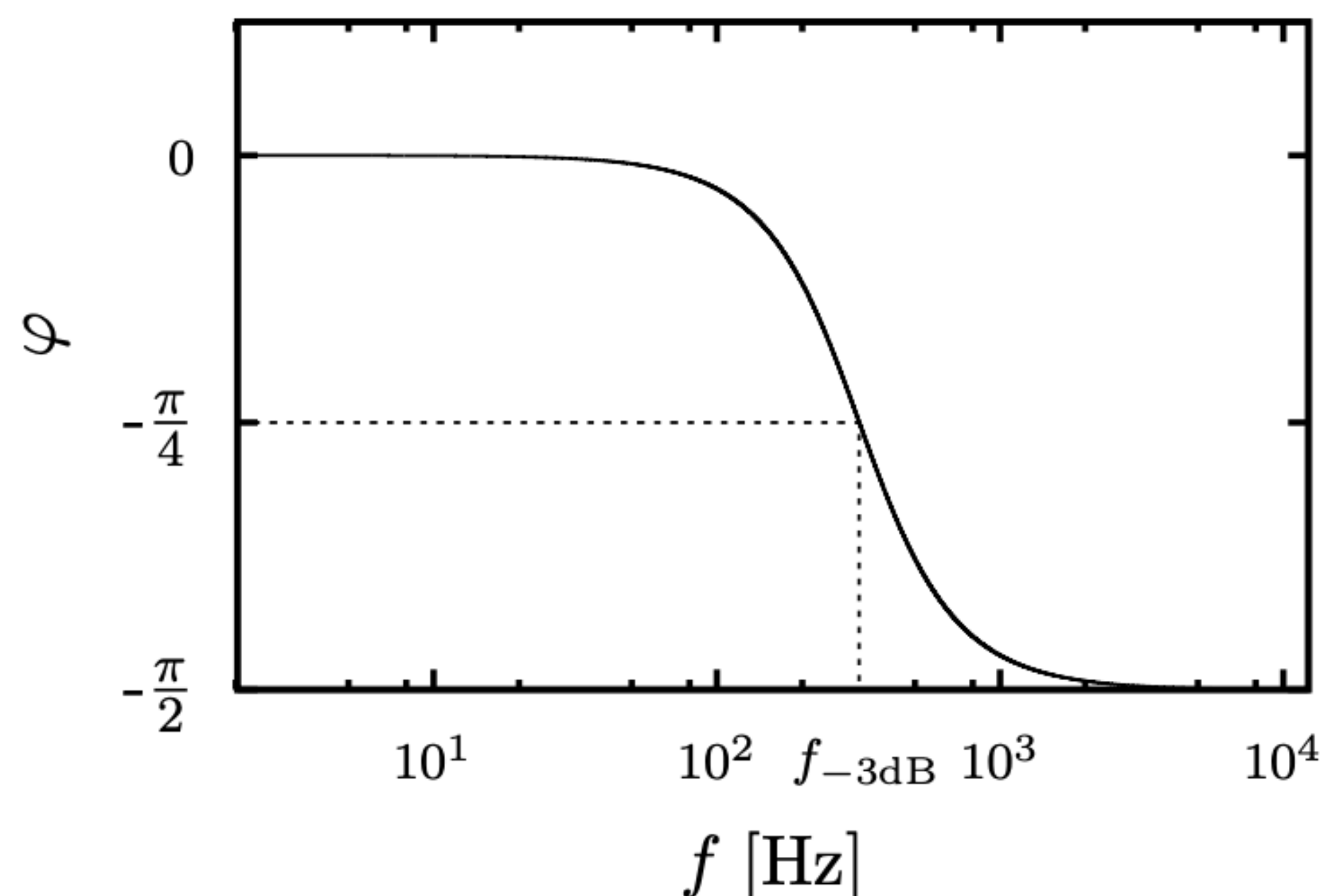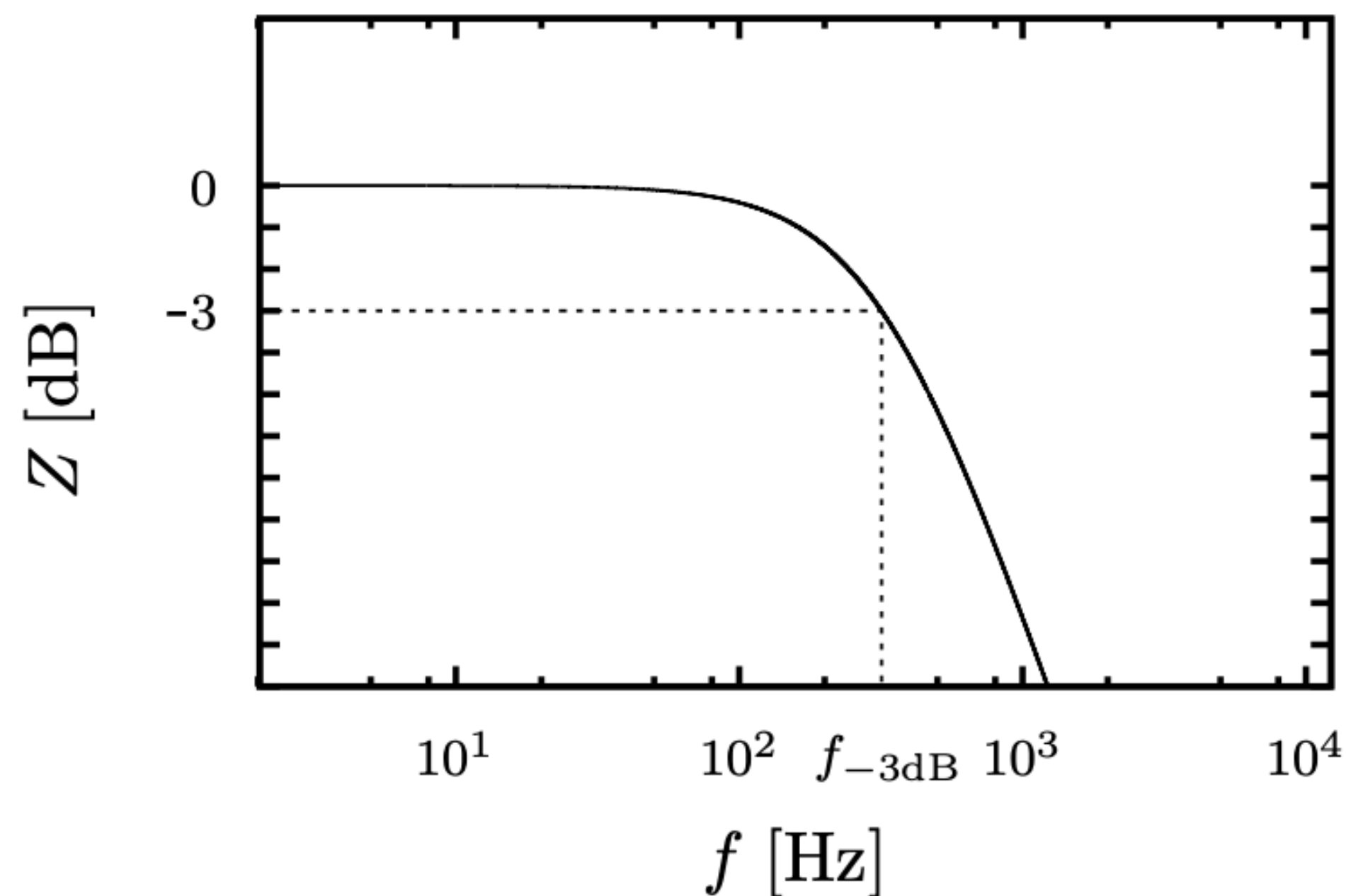

Bode Plot: Low Pass


Closer Look

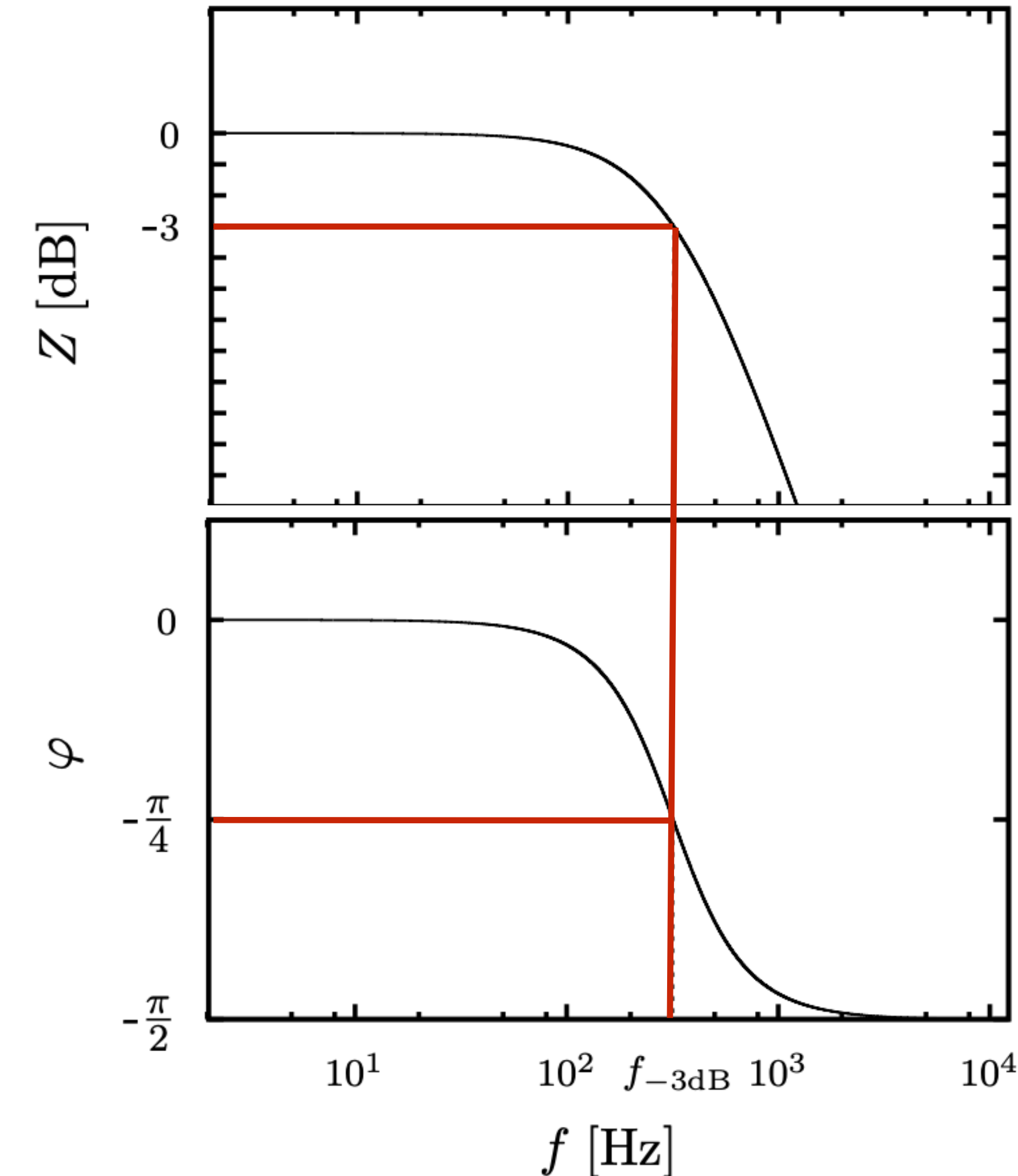

Cutoff frequency: Z has dropped by $1/\sqrt{2}$ (-3 dB)

$$f_{-3\text{ dB}} = \frac{1}{2\pi RC} \quad \omega_{-3\text{ dB}} = \frac{1}{RC}$$

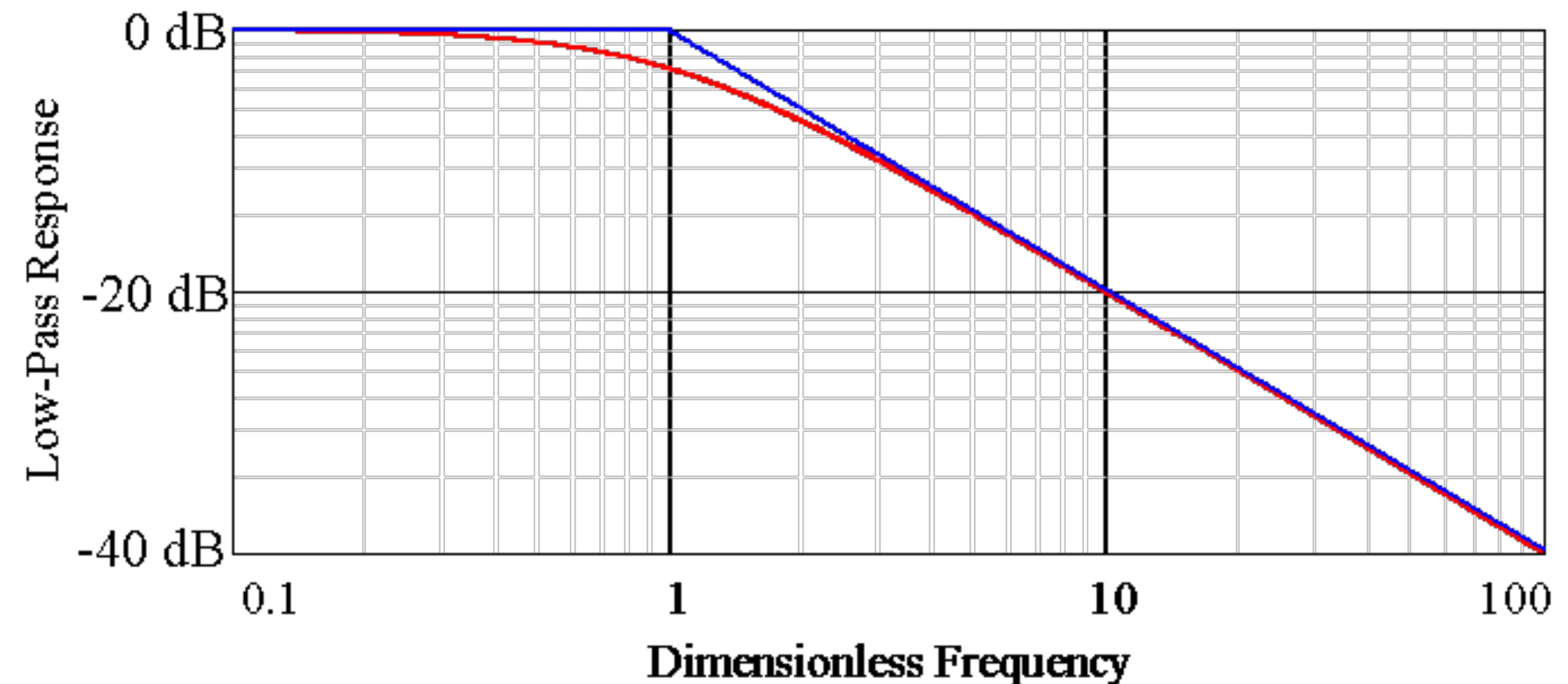Since $\tan \varphi = -\omega RC$: for critical frequency: -1; $\rightarrow \varphi = -\pi/4$



At high frequencies Z drops by 20 dB per frequency decade.
Corresponds to 6 dB / Octave (frequency doubling / halving)

Next Lectures:

Digital - Thursday, November 9

Analog 05 - Chapters 02, 03 - Tuesday, November 14

Time Plan for Next Lectures

A few Changes coming up!

Calender Week	Tuesday	Thursday
45	07.11. Analog	09.11. Digital
46	14.11. Analog	09.11. Digital
47	21.11. Digital	23.11. Analog
48	28.11. Digital	30.11. Digital
49	05.12. Digital	07.12. Analog
50	12.12. Digital	14.12. Analog
51	19.12. Analog	21.12. Digital
2	09.01. Analog	11.01. Analog
3	16.01. Digital	18.01. Digital
4	23.01. Analog	25.01. Digital
5	30.01. Analog	01.02. Digital
6	06.02. Analog	08.02. Digital
7	13.02. Analog	15.02. Digital

Electronics for Physicists

Analog Electronics

Chapter 2; Lecture 04

Frank Simon

Institute for Data Processing and Electronics

07.11.2023

KIT, Winter 2023/24