
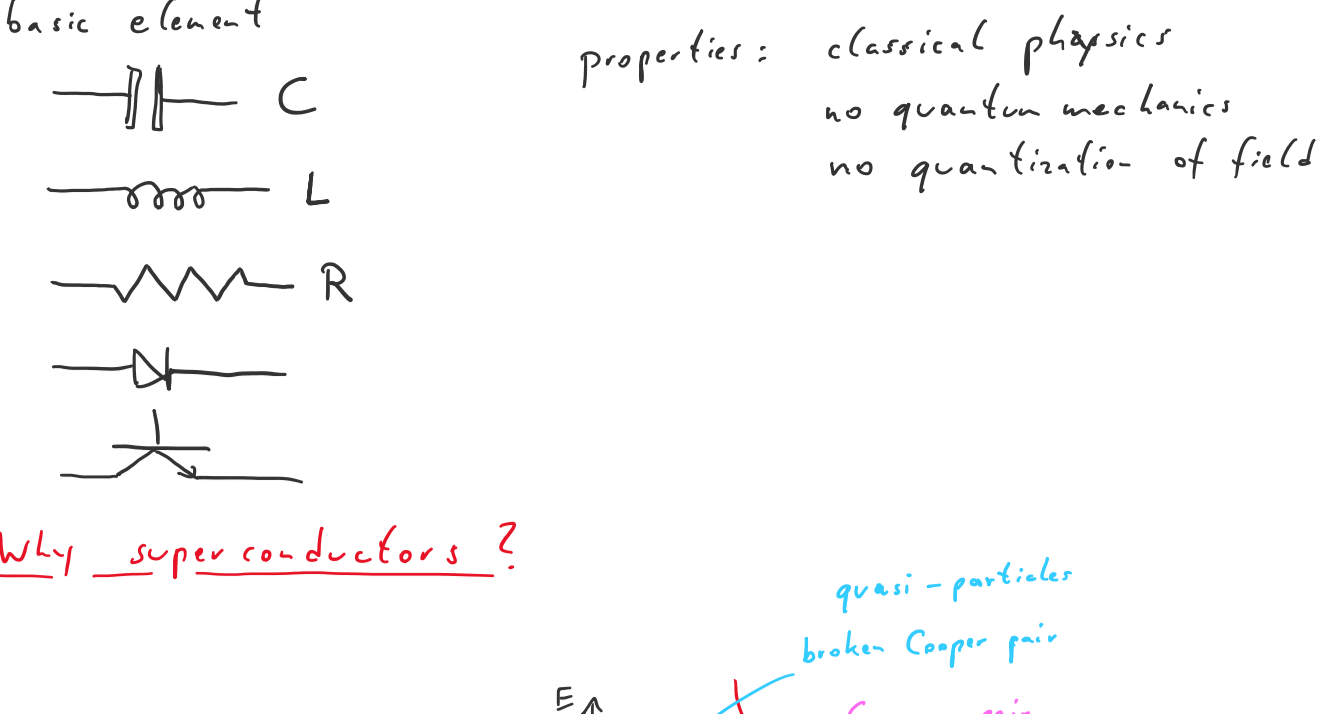


2. Introduction to superconducting quantum circuits

conventional electronic circuits

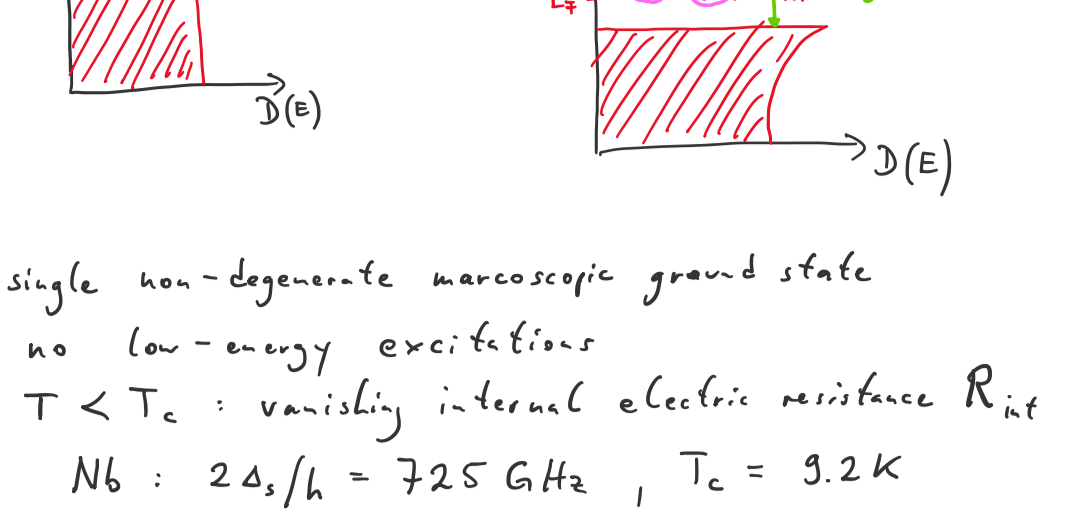

Why superconductors?



- single non-degenerate macroscopic ground state
- no low-energy excitations
- $T < T_c$: vanishing internal electric resistance R_{int}
- Nb: $2\Delta_0/\hbar = 725 \text{ GHz}$, $T_c = 9.2 \text{ K}$
- Al: $2\Delta_0/\hbar = 100 \text{ GHz}$, $T_c = 1.2 \text{ K}$

Quantum electronic circuit elements

$\frac{1}{\sqrt{2}} \left(\frac{1}{C} + \frac{1}{C} \right)$ charge on a capacitor

$\frac{1}{\sqrt{2}} \left(\frac{1}{L} + \frac{1}{L} \right)$ current or magnetic flux in an inductor

- charge Q and flux ϕ are conjugated variables
- quantum uncertainty relation $\Delta\phi\Delta Q > \hbar$

harmonic LC oscillator

$\omega = \frac{1}{\sqrt{LC}} \sim 5 \text{ GHz}$

typical inductor: $L = 1 \mu\text{H}$
wire in vacuum $L \sim 1 \text{ nH/mm}$

typical capacitor: $C = 1 \text{ pF}$
size $10 \times 10 \mu\text{m}^2$ and dielectric AlO_x ($\epsilon = 10$) of 10 nm thickness

classical physics \rightarrow quantum mechanics

$H = \frac{p^2}{2L} + \frac{Q^2}{2C}$ $\hat{H} = \frac{\hat{p}^2}{2L} + \frac{\hat{Q}^2}{2C} = \hbar\omega \left(\hat{a}^\dagger \hat{a} + \frac{1}{2} \right)$


$[\hat{p}, \hat{Q}] = i\hbar$

$\hat{Q} = \sqrt{\frac{\hbar}{2\omega C}} (\hat{a}^\dagger + \hat{a})$ $\hat{a}^\dagger |n\rangle = \sqrt{n+1} |n+1\rangle$

$\hat{p} = i\sqrt{\frac{\hbar}{2L\omega}} (\hat{a}^\dagger - \hat{a})$ $\hat{a} |n\rangle = \sqrt{n} |n-1\rangle$



$\hat{a}^\dagger |0\rangle = |1\rangle$ $\hat{a} |1\rangle = |0\rangle$

$Z_c = \sqrt{\frac{L}{C}}$ impedance

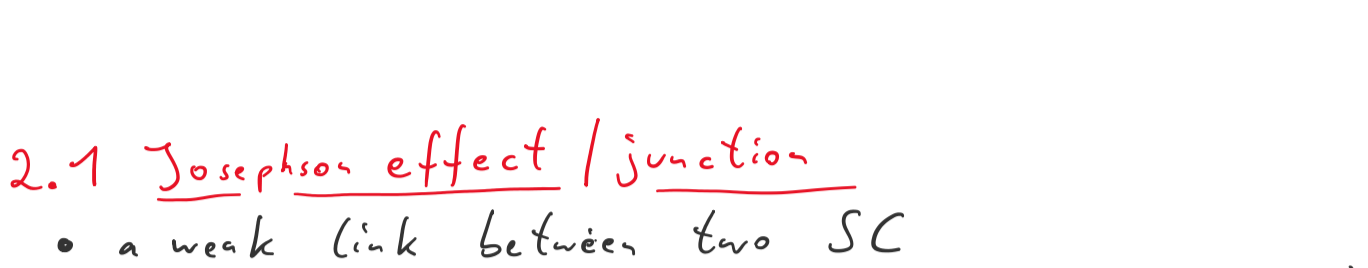

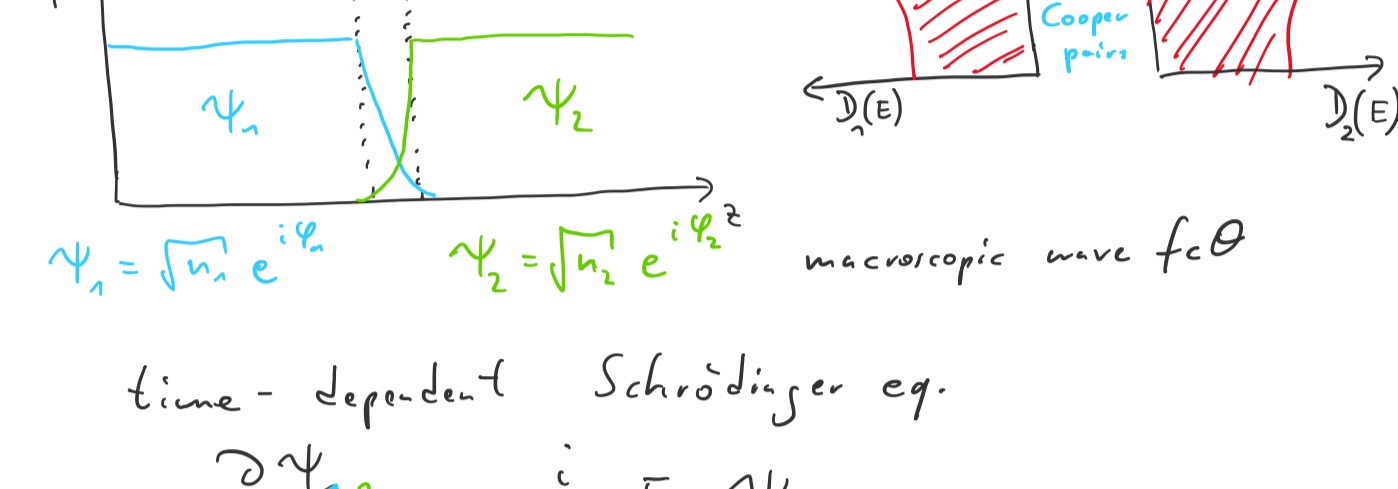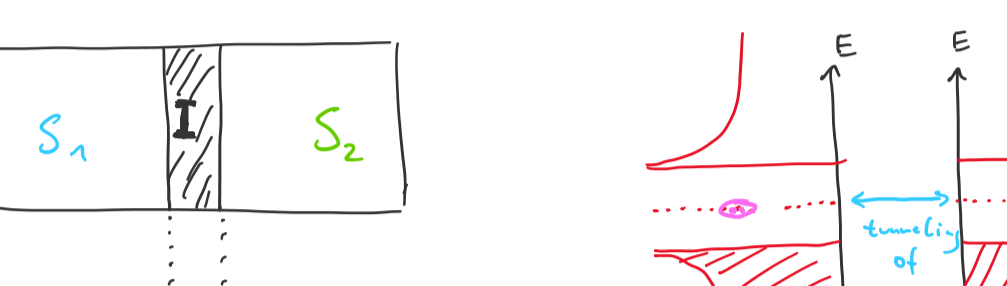2.1 Josephson effect / junction

- a weak link between two SC
- point contact - constriction (micro-bridge)



$\psi_n = \sqrt{V_n} e^{i\varphi_n}$ $\psi_2 = \sqrt{V_2} e^{i\varphi_2}$ macroscopic wave fct

time-dependent Schrödinger eq.

$\frac{\partial \psi_{1,2}}{\partial t} = -\frac{i}{\hbar} E_{1,2} \psi_{1,2}$

weak coupling between both SC

$\frac{\partial \psi_{1,2}}{\partial t} = -\frac{i}{\hbar} (E_{1,2} \psi_{1,2} + K \psi_{2,1})$

K: coupling constant

separating the real and imaginary part gives the two Josephson equations


$I_3 = I_c \sin \varphi$ $E_1 - E_2 = 2eU$

$\frac{d\varphi}{dt} = \frac{2\pi}{\Phi_0} U$ $n_1 = n_2$

V : Voltage $I_c = \frac{4e\hbar^2 K}{\Phi_0} V_n$

$\varphi = \varphi_2 - \varphi_1$ $\Phi_0 = h/2e$

for $\varphi = 0 \rightarrow I_3 = 0$

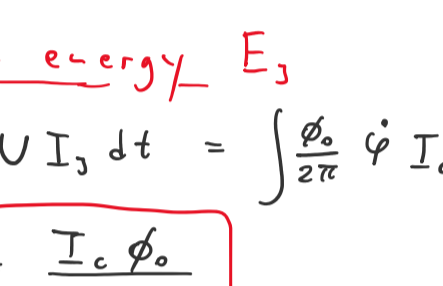

for $U = \text{const} \Rightarrow$ phase difference increases linearly with time

$\varphi_2 - \varphi_1 = \frac{2\pi}{\Phi_0} U t + \varphi(t=0)$

substitution into the first J eq.

$I_3 = I_c \sin \left(\frac{2\pi}{\Phi_0} U t + \varphi_0 \right)$ $f = \frac{1}{\Phi_0} U = \frac{2e}{h} U$

$486.6 \text{ MHz}/\mu\text{V}$

Josephson energy E_J

$E_J = \int U I_3 dt = \int \frac{\Phi_0}{2\pi} \dot{\varphi} I_c \sin \varphi dt = -\frac{I_c \Phi_0}{2\pi} \cos \varphi$

$E_J = -\frac{I_c \Phi_0}{2\pi}$


non-linear inductance

(a) $I_3 = I_c \sin \varphi \sim \dot{\varphi} = \frac{2\pi}{\Phi_0} U \sim U = \frac{\Phi_0}{2\pi} \dot{\varphi} = \frac{\Phi_0}{2\pi I_c \cos \varphi} \dot{\varphi}$

classical inductance: $U = -L \dot{I}$

$\sim L_J = -\frac{\Phi_0}{2\pi I_c \cos \varphi} \sim$ non-linear inductance

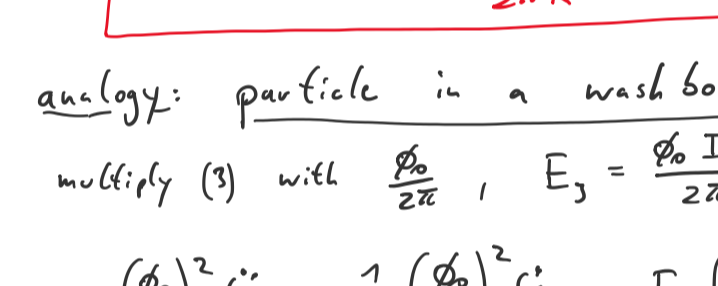2.2 Resistively capacitively shunted junction model RCSJ-Model



Kirchoff's law $I = I_3 + I_1 + I_2$ I_3 : Josephson current

I_1 : quasi-particle current I_2 : displacement current

quasi-particle current depends in a complicated way on the voltage U

no approx: $I_1 = \frac{U}{R}$

frequently, an artificial parallel resistance is attached "shunted JJ"

$I = I_c \sin \varphi + \frac{U}{R} + C \dot{U}$

$I = I_c \sin \varphi + \frac{\Phi_0}{2\pi R} \dot{\varphi} + \frac{C \Phi_0}{2\pi} \ddot{\varphi}$ (9)


analyze: particle in a wash board potential

multiply (9) with $\frac{\Phi_0}{2\pi}$, $E_J = \frac{\Phi_0 I_c}{2\pi}$ Josephson energy

$C \left(\frac{\Phi_0}{2\pi} \right)^2 \ddot{\varphi} + \frac{1}{R} \left(\frac{\Phi_0}{2\pi} \right)^2 \dot{\varphi} - E_J \left(\frac{I}{I_c} - \sin \varphi \right) = 0$

$\varphi \hat{=} \text{position}$

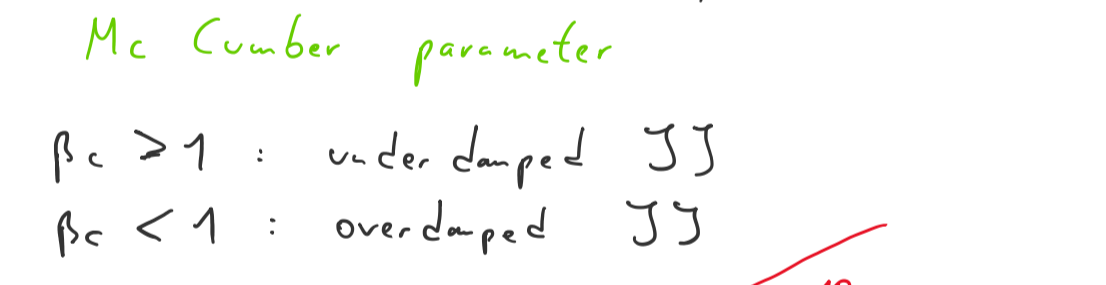$U(\varphi) = -E_J \left(\cos \varphi + \varphi \frac{I}{I_c} \right)$



- depending on the damping, the particle will move very non-uniformly
- at high current \Rightarrow particle very fast ($486.6 \text{ MHz}/\mu\text{V}$)

Josephson plasma oscillation at $I=0$

$\omega_{pl} = \sqrt{\frac{2\pi I_c}{\Phi_0 C}}$

$\omega_{pl}(I) = \omega_{pl} \left[1 - \frac{I}{I_c} \right]^{1/4}$


Dimensionless unit: $i = \frac{I}{I_c}$ $\tau = t \sqrt{\frac{2\pi I_c}{\Phi_0 C}} = t \omega_{pl}$

$\ddot{\varphi} + \beta_C^{-1/2} \dot{\varphi} - (i - \sin \varphi) = 0$

$\beta_C = \frac{2\pi I_c R^2 C}{\Phi_0} = \left(\frac{\omega_{pl}}{\omega_{RC}} \right)^2$ $\omega_{RC} = \frac{1}{RC}$

Mc Cumber parameter

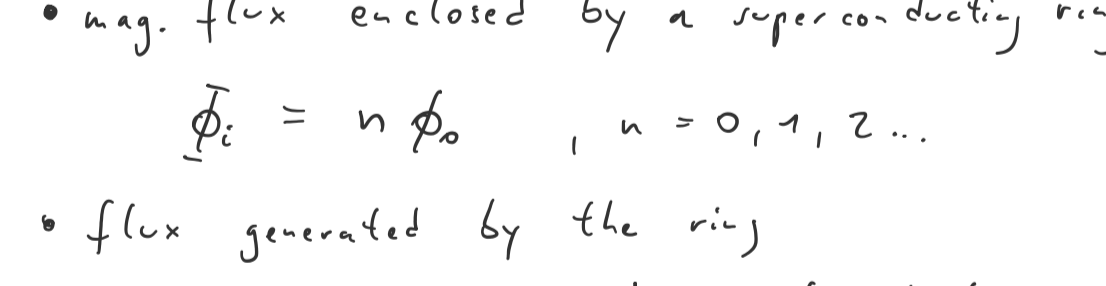- $\beta_C > 1$: underdamped JJ
- $\beta_C < 1$: overdamped JJ



for $\beta_C = 0$ $U = 0$ for $|I| < I_c$


$U = R_n \sqrt{I^2 - I_c^2}$ for $|I| > I_c$

Ambegaokar - Baraoff relation

$I_c R_n = \frac{\pi}{2e} \Delta_0(T) \tanh \left(\frac{\Delta_0(T)}{2k_B T} \right)$


for $T=0$ $I_c R_n = \frac{\pi}{2e} \Delta_0$

Thermal effects

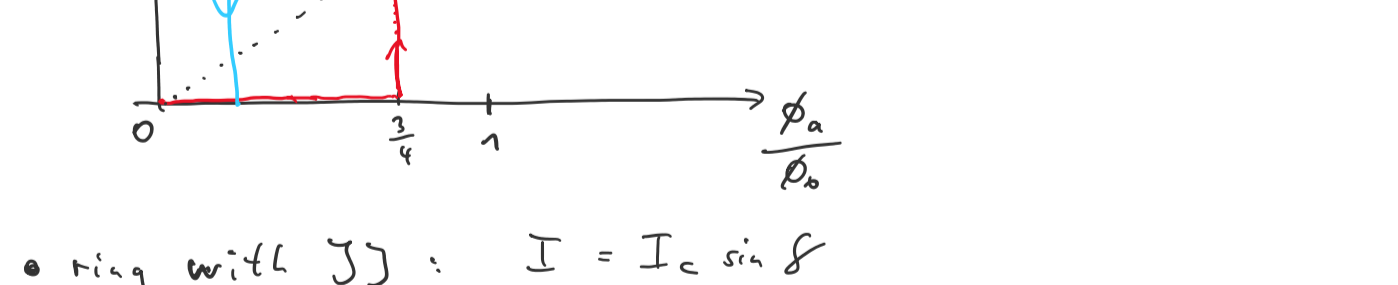

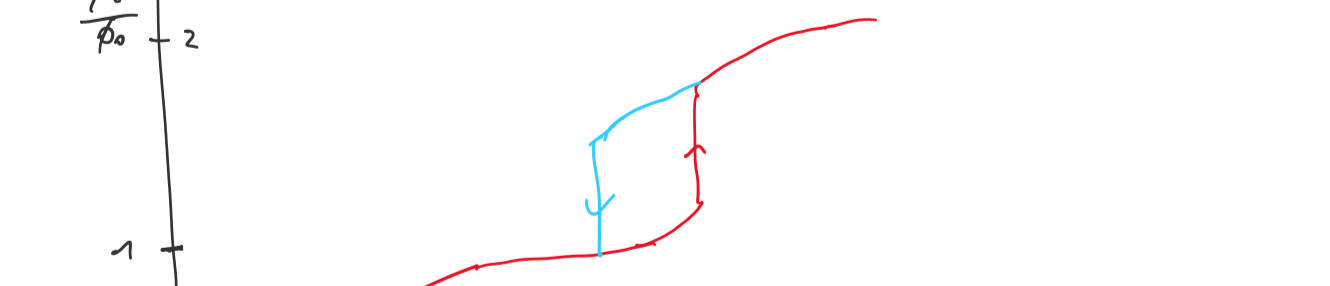2.3 RF-SQUID $\hat{=} \text{flux qubit}$

Superconducting QUantum Interference Device



magn. flux enclosed by a superconducting ring is quantized

$\Phi_i = n \Phi_0$, $n = 0, 1, 2, \dots$

flux generated by the ring


$\Phi_s = L I_s$ L : self-inductance of ring

I_c : supercurrent of the ring

assume the critical current

$L I_c = \frac{1}{4} \Phi_0$

$\Phi_a = B_a A$

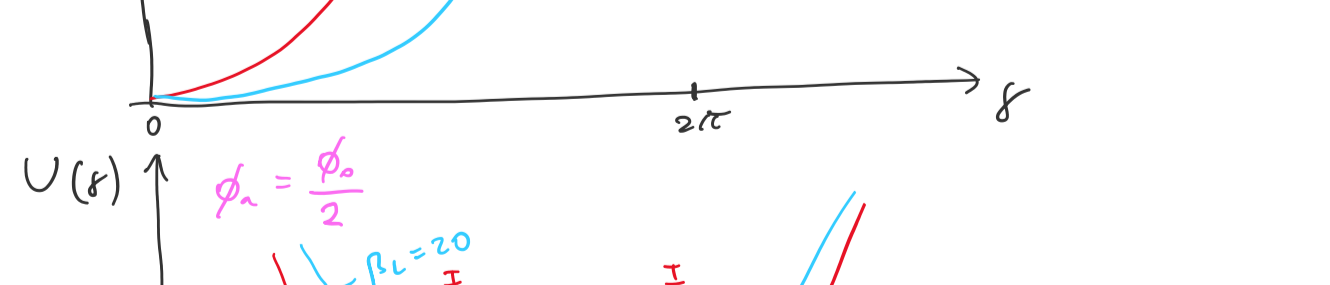

ring with JJ: $I = I_c \sin \varphi$

$\varphi + 2\pi \frac{\Phi_i}{\Phi_0} = 2\pi n$


$\Phi_i = \Phi_a + L I_s = \Phi_a + L I_c \sin \left(2\pi \frac{\Phi_i}{\Phi_0} \right)$

$U(\varphi) = \frac{1}{2L} \left(\frac{\Phi}{2\pi} - \Phi_i \right)^2 - E_J \cos \varphi$


inductive energy Josephson energy

$U(\varphi) = E_J \left[\frac{1}{2\beta_L} \left(\varphi - 2\pi \frac{\Phi_a}{\Phi_0} \right)^2 - \cos \varphi \right]$

$\beta_L = \frac{2\pi L I_c}{\Phi_0}$

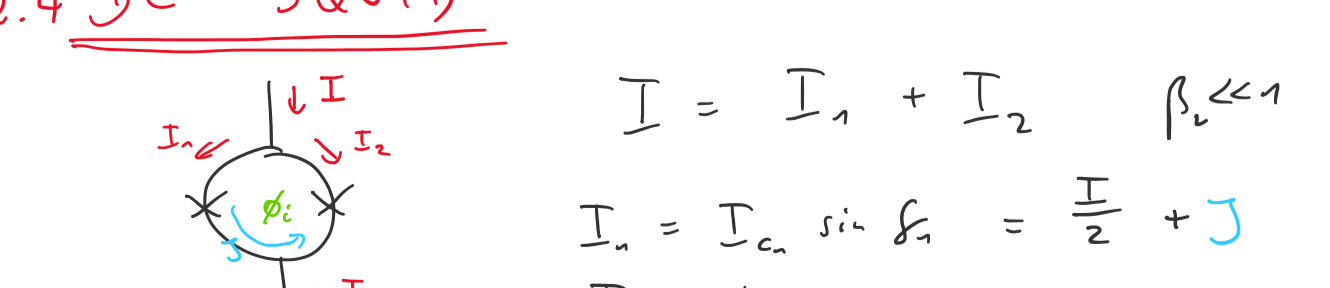

Why RF-SQUID?

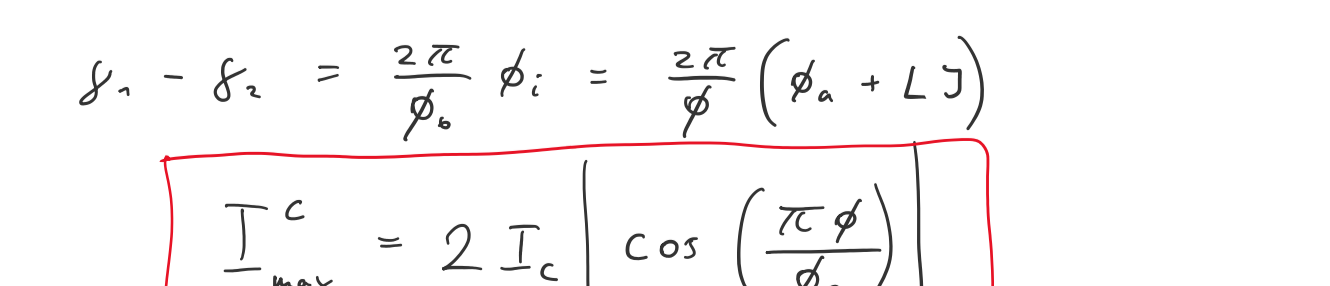

2.4 JC-SQUID

$I = I_1 + I_2$ $\beta_C \ll 1$

$I_1 = I_c \sin \varphi_1 = \frac{I}{2} + J$

$I_2 = I_c \sin \varphi_2 = \frac{I}{2} - J$

$\varphi_1 - \varphi_2 = \frac{2\pi}{\Phi_0} \Phi_i = \frac{2\pi}{\Phi_0} (\Phi_a + L I)$

$I_{c, \text{max}}^c = 2 I_c \left| \cos \left(\frac{\pi \Phi_a}{\Phi_0} \right) \right|$

